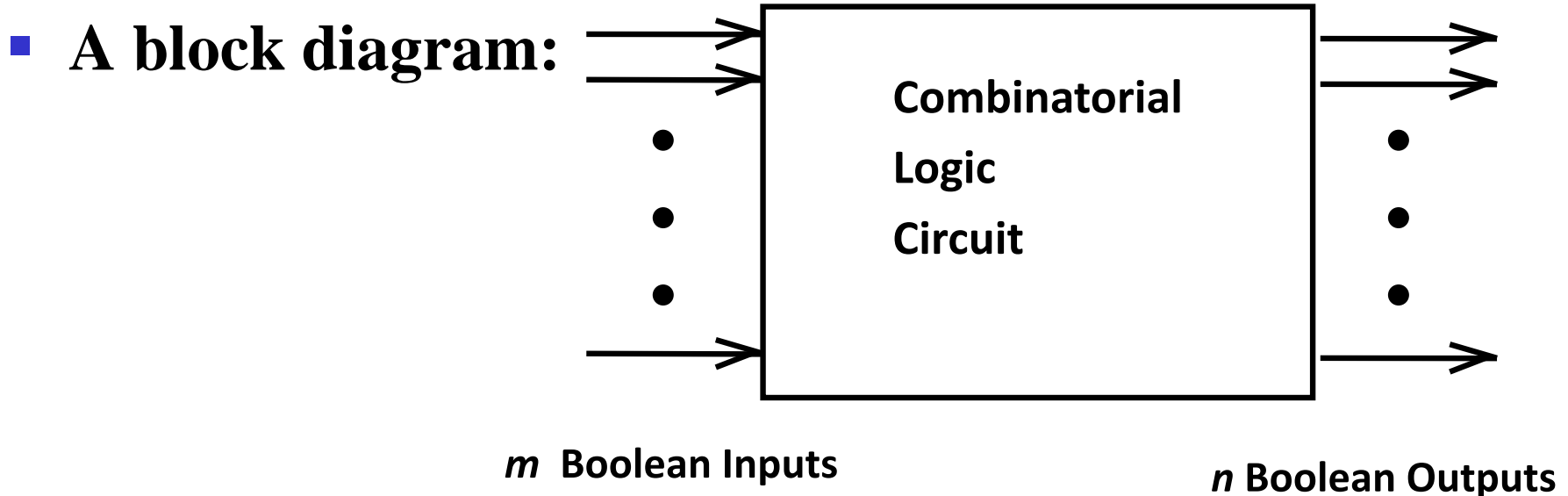


Chapter 3 – Combinational Digital Circuit Design

Part 1 – Implementation Technology and Logic Design

Combinational Circuits

- A combinational logic circuit has:
 - A set of m Boolean inputs,
 - A set of n Boolean outputs, and
 - n switching functions, each mapping the 2^m input combinations to an output such that the current output depends only on the current input values



Addition of Positive Numbers

Carry	00000		01100	
X	01100	12	10110	22
Y	<u>+10001</u>	<u>+17</u>	<u>+10111</u>	<u>+23</u>
Sum	11101	29	101101	45

Note:

- 1. The carry input to the LSB is always '0'.**
- 2. The sum of two n-bit numbers has n+1-bits.**

Addition Circuit

- Addition of two 2-bit numbers

- $S = X + Y$
- $X = (x_1 \ x_0)$ and $Y = (y_1 \ y_0)$
- $S = (s_2 \ s_1 \ s_0)$

- Addition of bits

1. $s_0 = x_0 \oplus y_0$
 $c_1 = x_0 y_0$ (carry)
2. $s_1 = x_1 \oplus y_1 \oplus c_1$
 $c_2 = x_1 y_1 + x_1 c_1 + y_1 c_1$
3. $s_2 = c_2$

x_i	y_i	c_i	s_i	c_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


Addition Circuit

$$s_1 = x_1 \oplus y_1 \oplus c_1$$

$$s_2 = c_2 \quad c_2 = x_1 y_1 + x_1 c_1 + y_1 c_1$$

$$s_0 = x_0 \oplus y_0$$

$$c_1 = x_0 y_0$$

 

Full Adder


Half Adder

Integer Adder 1/2


■ n-bit Binary Adder:

- $A = (a_{n-1}, a_{n-2}, \dots, a_1, a_0)$
- $B = (b_{n-1}, b_{n-2}, \dots, b_1, b_0)$
- $A + B = S = (s_n, s_{n-1}, s_{n-2}, \dots, s_1, s_0)$

■ 4-bit Binary Adder:

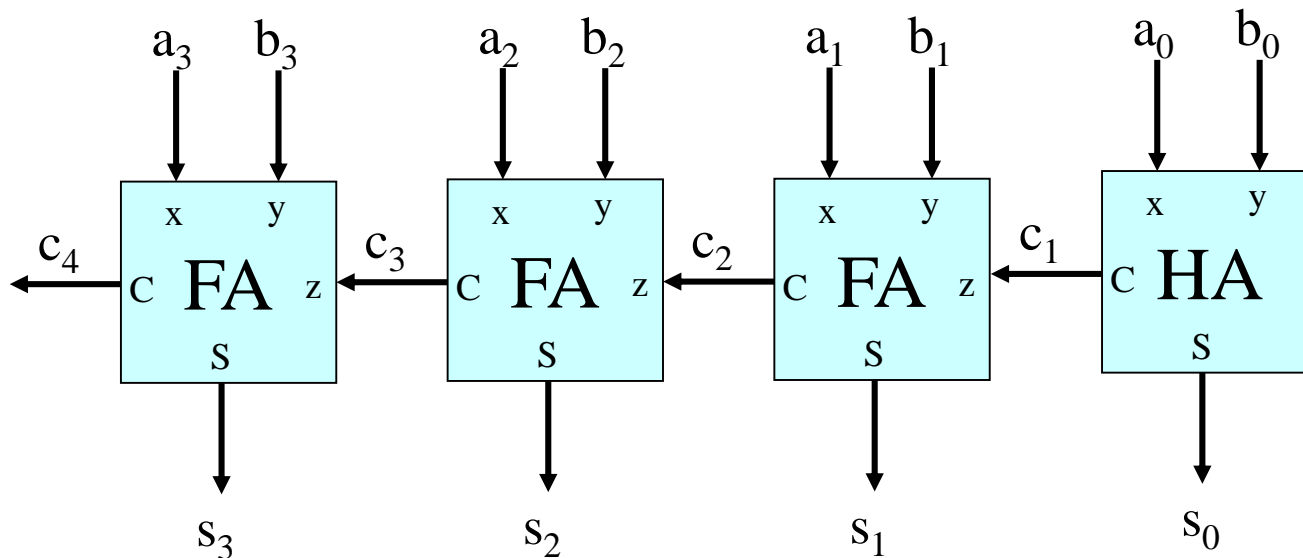

Integer Adder 2/2

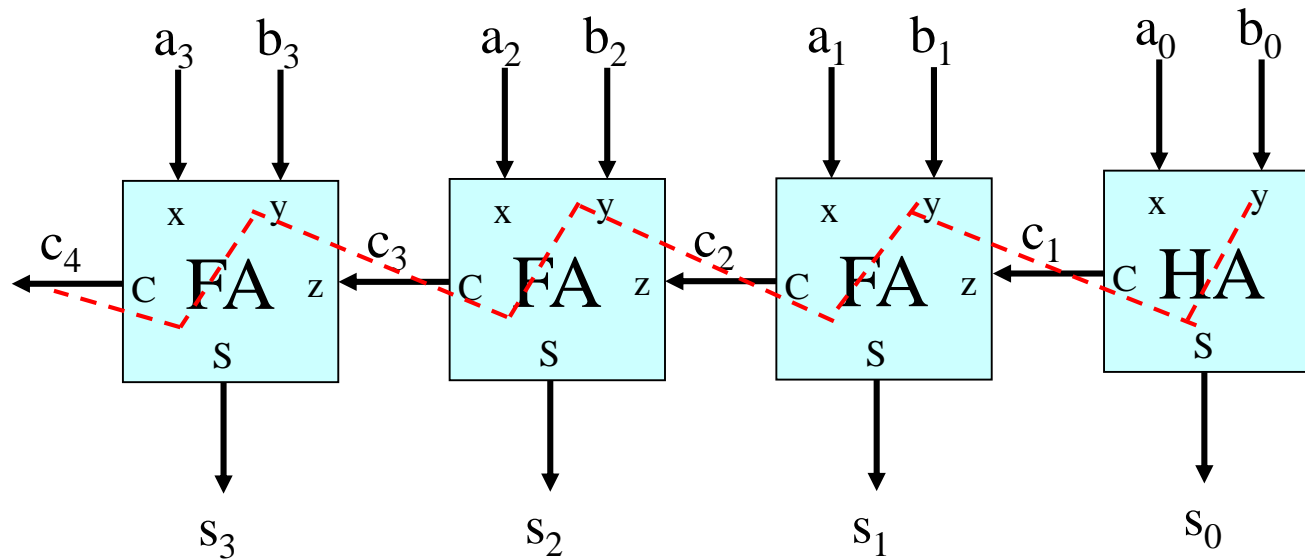

Ripple-carry adder

Reusable Functions

- We used top-down design method in ripple carry adder design.
- If we would use classical design method:
 - Number of inputs: 8
 - Number of outputs: 5
 - A truth table with $2^9 = 512$ is needed
 - We have to optimize 5 Boolean functions with 9 variables
- When reuse functions
 - We decompose the design to simpler operation blocks.
 - We design the complex function by the use of sub-blocks.

Reusable Functions

- **Whenever possible, we try to decompose a complex design into common, *reusable* function blocks**
- **These blocks are**
 - **verified and well-documented**
 - **placed in libraries for future use**

Top-Down versus Bottom-Up

- A *top-down design* proceeds from an abstract, high-level specification to a more and more detailed design by decomposition and successive refinement
- A *bottom-up design* starts with detailed primitive blocks and combines them into larger and more complex functional blocks
- Design usually proceeds top-down to known building blocks ranging from complete CPUs to primitive logic gates or electronic components.
- Much of the material in this chapter is devoted to learning about combinational blocks used in top-down design.

Verification

- **Verification - show that the final circuit designed implements the original specification**
- **Simple specifications are:**
 - truth tables
 - Boolean equations
 - HDL code
- **If the above result from formulation and are not the original specification, it is critical that the formulation process be flawless for the verification to be valid!**

Basic Verification Methods

■ Manual Logic Analysis

- Find the truth table or Boolean equations for the final circuit
- Compare the final circuit truth table with the specified truth table, or
- Show that the Boolean equations for the final circuit are equal to the specified Boolean equations

■ Simulation

- Simulate the final circuit (or its netlist, possibly written as an HDL) and the specified truth table, equations, or HDL description using test input values that fully validate correctness.
- The obvious test for a combinational circuit is application of all possible “care” input combinations from the specification