

DIGITAL SYSTEM DESIGN APPLICATIONS

(CRN: 11275)

THE REPORT OF EXPERIMENT – 6



Faculty of Electrical and Electronics Engineering

Electronics and Communication Engineering

Yusuf Tekin – 040200043

1. Clock Generation

```
`timescale 1ns / 1ps

module top_module(
    input clk,
    input rst,
    output reg [6:0] cnt100,
    output reg [6:0] cnt80,
    output reg [6:0] cnt60
);

    wire clk80, clk60;

    // Clocking Wizard instantiation
    clk_wiz_0 clknetwork (
        .clk_out1(clk80),
        .clk_out2(clk60),
        .reset(rst),
        .locked(),
        .clk_in1(clk)
    );

    // Counter for 100 MHz clock
    always @(posedge clk or posedge rst) begin
        if (rst) begin
            cnt100 <= 7'b0;
        end else if (cnt100 < 100) begin
            cnt100 <= cnt100 + 1;
        end
    end

    // Counter for 80 MHz clock
    always @(posedge clk80 or posedge rst) begin
        if (rst) begin
            cnt80 <= 7'b0;
        end else if (cnt80 < 80) begin
            cnt80 <= cnt80 + 1;
        end
    end

    // Counter for 60 MHz clock
    always @(posedge clk60 or posedge rst) begin
        if (rst) begin
            cnt60 <= 7'b0;
        end else if (cnt60 < 60) begin
            cnt60 <= cnt60 + 1;
        end
    end

endmodule
```

Clock Generation Verilog Code

```
`timescale 1ns / 1ps

module top_module_tb;

reg clk, rst;
wire [6:0] cnt100, cnt80, cnt60;


top_module dut (
    .clk(clk),
    .rst(rst),
    .cnt100(cnt100),
    .cnt80(cnt80),
    .cnt60(cnt60)
);

always #5 clk = ~clk;

initial begin

    clk = 0; rst = 1; #15;
    rst = 0; #10; rst = 1;
    #10; rst = 0;
    #4200;
    $finish();
end
endmodule
```

Clock Generation Testbench Code

 

Clock Generation Behavioral Simulation

Primitives		
Ref Name	Used	Functional Category
OBUF	21	IO
FDCE	20	Flop & Latch
LUT5	6	LUT
LUT3	6	LUT
LUT4	4	LUT
LUT6	3	LUT
LUT2	3	LUT
LUT1	3	LUT
BUFG	3	Clock
IBUF	2	IO
MMCM2_ADV	1	Clock

Clock Generation Primitive Usage

```

  ✓ clknetwork/inst/clk_in1 (100.00 MHz) (drives 15 loads)
    ✓ clk_in1 (clknetwork/inst/clk_in1)
      inst (clk_wiz_0_clk_wiz)
    ✓ CLKIN1 (clknetwork/inst/mmcm_adv_inst/CLKIN1)
      > mmcm_adv_inst (MMCME2_ADV)
  ✓ sys_clk_pin (100.00 MHz) (drives 21 loads)
    ✓ clk
      I (clk_IBUF_inst/I)
        clk_IBUF_inst (IBUF)

```

Clock Generation Clock Networks Report

2. Clock Gating

```
`timescale 1ns / 1ps
module clock_gating(
    input clk,
    input rst,
    output reg [6:0] cnt50,
    output reg [6:0] cnt25
);

reg clk50_en, clk25_en;
wire clk50, clk25;

integer i;

BUFR #(
    .BUFR_DIVIDE("2"),
    .SIM_DEVICE("7SERIES")
)
BUFR_inst_1 (
    .O(clk50),
    .CE(clk50_en),
    .CLR(1'b0),
    .I(clk)
);

BUFR #(
    .BUFR_DIVIDE("4"),
    .SIM_DEVICE("7SERIES")
)
BUFR_inst_2 (
    .O(clk25),
    .CE(clk25_en),
    .CLR(1'b0),
    .I(clk)
);

always @(posedge clk50 or posedge rst) begin
    if(rst) begin
        cnt50 <= 7'b0;
    end else if(cnt50 < 50) begin
        cnt50 <= cnt50 + 1;
    end
end

always @(posedge clk25 or posedge rst) begin
    if(rst) begin
        cnt25 <= 7'b0;
    end else if(cnt25 < 25) begin
        cnt25 <= cnt25 + 1;
    end
end

always @(posedge clk or posedge rst) begin
    if (rst) begin
        clk50_en <= 1'b0;
        clk25_en <= 1'b0;
    end else begin
        if (cnt50 < 50)
            clk50_en <= 1'b1;
        else
            clk50_en <= 1'b0;

        if (cnt25 < 25)
            clk25_en <= 1'b1;
        else
            clk25_en <= 1'b0;
    end
end
endmodule
```

Clock Gating Verilog Code

```
`timescale 1ns / 1ps

module clock_gating_tb;


wire [6:0] cnt50, cnt25;
reg clk, rst;

clock_gating dut(
    .clk(clk),
    .rst(rst),
    .cnt50(cnt50),
    .cnt25(cnt25)
);

always #5 clk = ~clk;

initial begin
    clk = 1'b0; rst = 1'b0; #100;
    rst = 1'b1; #10; rst = 1'b0;
    #4200;
    $finish();
end
endmodule
```


Clock Gating Testbench Code

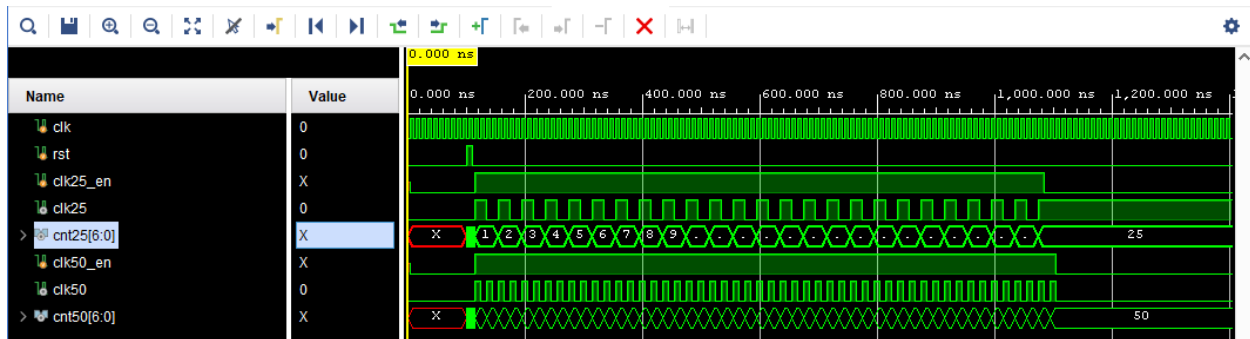

Clock Gating Behavioral Simulation

Primitives		
Ref Name	Used	Functional Category
OBUF	14	IO
FDCE	13	Flop & Latch
LUT5	4	LUT
LUT4	2	LUT
LUT3	2	LUT
LUT2	2	LUT
LUT1	2	LUT
IBUF	2	IO
BUFR	2	Clock
LUT6	1	LUT
BUFG	1	Clock

Clock Gatin Primitive Usage

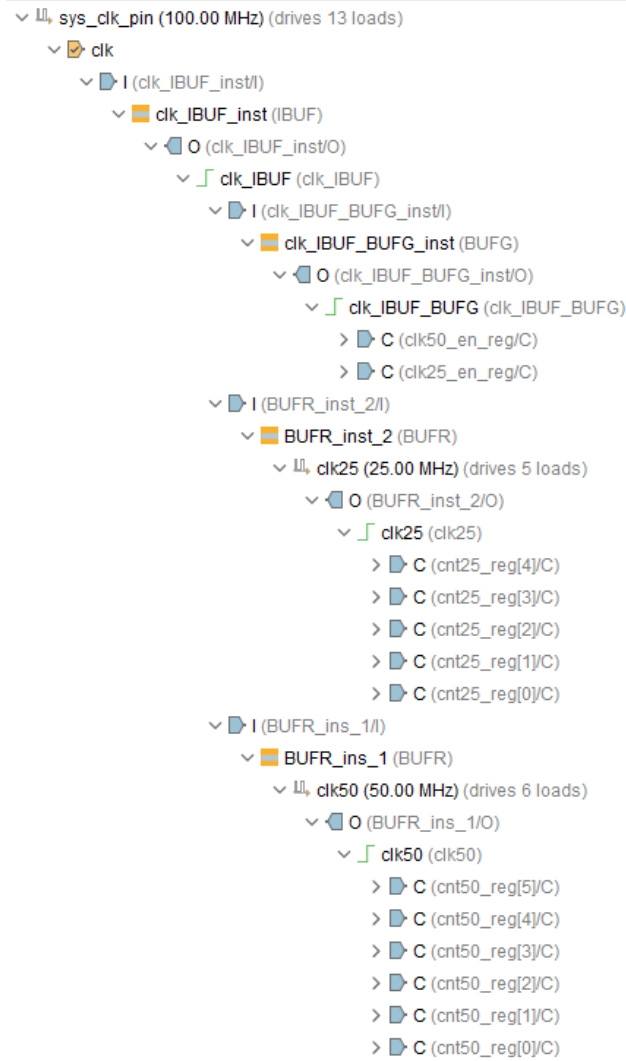

Clock Gating Clock Network Report

3. Block RAM

```
//Copyright 1986-2022 Xilinx, Inc. All Rights Reserved.

//Copyright 2022-2024 Advanced Micro Devices, Inc. All Rights
Reserved.
//-----
-----
//Tool Version: Vivado v.2024.1 (win64) Build 5076996 Wed May 22
18:37:14 MDT 2024
//Date       : Mon Dec  9 11:36:38 2024
//Host       : DESKTOP-KMJ9JAC running 64-bit major release (build
9200)
//Command    : generate_target block_ram_50MHz_wrapper.bd
//Design     : block_ram_50MHz_wrapper
//Purpose    : IP block netlist
//-----
-----
`timescale 1 ps / 1 ps

module block_ram_50MHz_wrapper
    (addra_0,
     clk_100MHz,
     dina_0,
     douta_0,
     wea_0);
    input [3:0]addra_0;
    input  clk_100MHz;
    input [7:0]dina_0;
    output [7:0]douta_0;
    input [0:0]wea_0;

    wire [3:0]addra_0;
    wire  clk_100MHz;
    wire [7:0]dina_0;
    wire [7:0]douta_0;
    wire [0:0]wea_0;

    block_ram_50MHz block_ram_50MHz_i
        (.addra_0(addra_0),
         .clk_100MHz(clk_100MHz),
         .dina_0(dina_0),
         .douta_0(douta_0),
         .wea_0(wea_0));
endmodule
```

Block RAM Verilog Code


```
`timescale 1ns / 1ps

module block_ram_50MHz_wrapper_tb;

wire [7:0] douta_0;
reg clk_100MHz, wea_0;
reg [3:0] addra_0;
reg [7:0] dina_0;

integer i;

block_ram_50MHz_wrapper dut(
    .addra_0(addra_0),
    .clk_100MHz(clk_100MHz),
    .dina_0(dina_0),
    .douta_0(douta_0),
    .wea_0(wea_0)
);

always #5 clk_100MHz = ~clk_100MHz;

initial begin
    clk_100MHz = 1'b0; wea_0 = 1'b0; #500;

    $display("\n--- Reading Initial Data ---");
    for (i = 0; i < 16; i = i + 1) begin
        addra_0 = i;
        #40;
        $display("Address %0d: Data = %0d", addra_0, douta_0);
    end

    $display("\n--- Writing School Number in reverse to the RAM ---");
    wea_0 = 1'b1; #90;
    addra_0 = 4'b0000; dina_0 = 8'b000000011; #60;
    addra_0 = 4'b0001; dina_0 = 8'b00000100; #60;
    addra_0 = 4'b0010; dina_0 = 8'b00000000; #60;
    addra_0 = 4'b0011; dina_0 = 8'b00000000; #60;
    addra_0 = 4'b0100; dina_0 = 8'b00000000; #60;
    addra_0 = 4'b0101; dina_0 = 8'b00000010; #60;
    addra_0 = 4'b0110; dina_0 = 8'b00000000; #60;
    addra_0 = 4'b0111; dina_0 = 8'b00000100; #60;
    addra_0 = 4'b1000; dina_0 = 8'b00000011; #60;
    addra_0 = 4'b1001; dina_0 = 8'b00000100; #60;
    addra_0 = 4'b1010; dina_0 = 8'b00000000; #60;
    addra_0 = 4'b1011; dina_0 = 8'b00000000; #60;
    addra_0 = 4'b1100; dina_0 = 8'b00000000; #60;
    addra_0 = 4'b1101; dina_0 = 8'b00000010; #60;
    addra_0 = 4'b1110; dina_0 = 8'b00000000; #60;
    addra_0 = 4'b1111; dina_0 = 8'b00000100; #60;

    wea_0 = 1'b0; #90;
    addra_0 = 4'b0000; #80;
    addra_0 = 4'b0001; #80;
    addra_0 = 4'b0010; #80;
    addra_0 = 4'b0011; #80;
    addra_0 = 4'b0100; #80;
    addra_0 = 4'b0101; #80;
    addra_0 = 4'b0110; #80;
    addra_0 = 4'b0111; #80;
    addra_0 = 4'b1000; #80;
    addra_0 = 4'b1001; #80;
    addra_0 = 4'b1010; #80;
    addra_0 = 4'b1011; #80;
    addra_0 = 4'b1100; #80;
    addra_0 = 4'b1101; #80;
    addra_0 = 4'b1110; #80;
    addra_0 = 4'b1111; #80;
    $display("\n--- Writing Complete ---");
    $display("\n--- Reading data from RAM ---");
    for (i = 0; i < 16; i = i + 1) begin
        addra_0 = i;
        #40;
        $display("Address %0d: Data = %0d", addra_0, douta_0);
    end

    $display("\nBenchmark finished.\n");
    $finish();
end
endmodule
```

Block RAM Testbench Code

```
--- Reading Initial Data ---
Address 0: Data = 4
Address 1: Data = 0
Address 2: Data = 2
Address 3: Data = 0
Address 4: Data = 0
Address 5: Data = 0
Address 6: Data = 4
Address 7: Data = 3
Address 8: Data = 4
Address 9: Data = 0
Address 10: Data = 2
Address 11: Data = 0
run 4500 ns
Address 12: Data = 0
Address 13: Data = 0
Address 14: Data = 4
Address 15: Data = 3

--- Writing School Number in reverse to the RAM ---


--- Writing Complete ---

--- Reading data from RAM ---
Address 0: Data = 3
Address 1: Data = 4
Address 2: Data = 0
Address 3: Data = 0
Address 4: Data = 0
Address 5: Data = 2
Address 6: Data = 0
Address 7: Data = 4
Address 8: Data = 3
Address 9: Data = 4
Address 10: Data = 0
Address 11: Data = 0
Address 12: Data = 0
Address 13: Data = 2
Address 14: Data = 0
Address 15: Data = 4

Benchmark finished.

$finish called at time : 4200 ns : File "C:/Users/jsp
```

Block RAM Simulation TCL Console Log

 


Block RAM Behavioral Simulation

Primitives

Ref Name	Used	Functional Category
IBUF	14	IO
OBUF	8	IO
BUFG	2	Clock
RAMB18E1	1	Block Memory
MMCME2_ADV	1	Clock

Block RAM Primitive Usage

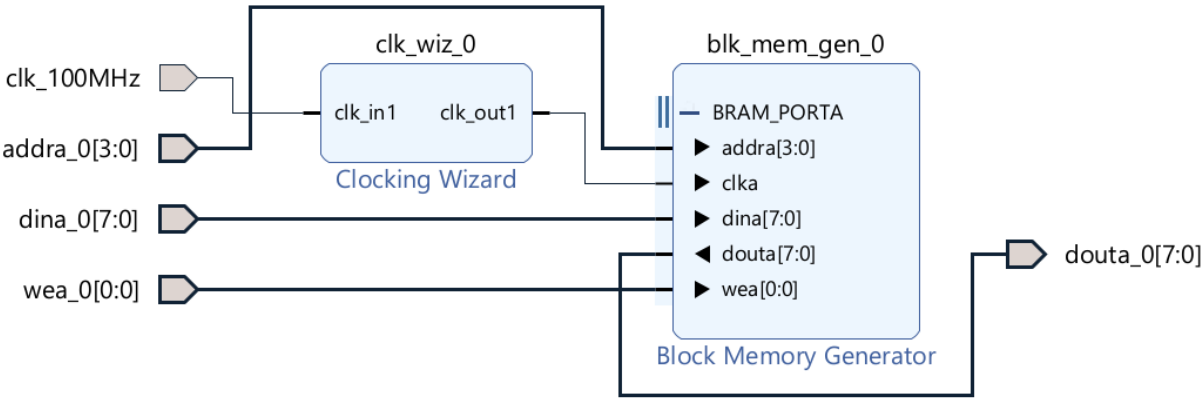

Block RAM Block Design

4. FIFO for Clock Domain Crossing

```
`timescale 1ns / 1ps

module top_module(
    input clk,
    input rst,
    input wr_en,
    input rd_en,
    input [7:0] din,
    output [7:0] dout,
    output empty,
    output full,
    output overflow,
    output underflow
);

    reg [2:0] counter = 3'b0;
    wire wr_clk, rd_clk;

    assign wr_clk = counter[0];
    assign rd_clk = counter[1];

    always @(posedge clk or posedge rst) begin
        if(rst) counter <= 3'b0;
        else counter <= counter + 1;
    end

    fifo_generator_0 memory1(
        .wr_clk(wr_clk),
        .wr_rst (rst),
        .rd_clk(rd_clk),
        .rd_rst(rst),
        .din(din),
        .wr_en(wr_en),
        .rd_en(rd_en),
        .dout(dout),
        .full(full),
        .overflow(overflow),
        .empty(empty),
        .underflow(underflow));

endmodule
```

FIFO Verilog Code

```

`timescale 1ns / 1ps

module top_module_tb;

wire full, overflow, underflow, empty;
wire [7:0] dout;
reg [7:0] din;
reg clk, rst, wr_en, rd_en;
integer i;

top_module dut(
    .clk(clk),
    .rst(rst),
    .wr_en(wr_en),
    .rd_en(rd_en),
    .din(din),
    .dout(dout),
    .empty(empty),
    .full(full),
    .overflow(overflow),
    .underflow(underflow));


always #5 clk = ~clk;

initial begin
    clk = 1'b0; rst = 1'b1; wr_en = 1'b0; rd_en = 1'b0; #40;
    rst = 1'b0; wr_en = 1'b1; rd_en = 1'b1; #80;

    for (i = 0; i < 64; i = i + 1) begin
        din <= i; #40;
    end
    #1200;
    $finish();
end
endmodule

```

FIFO Testbench Code

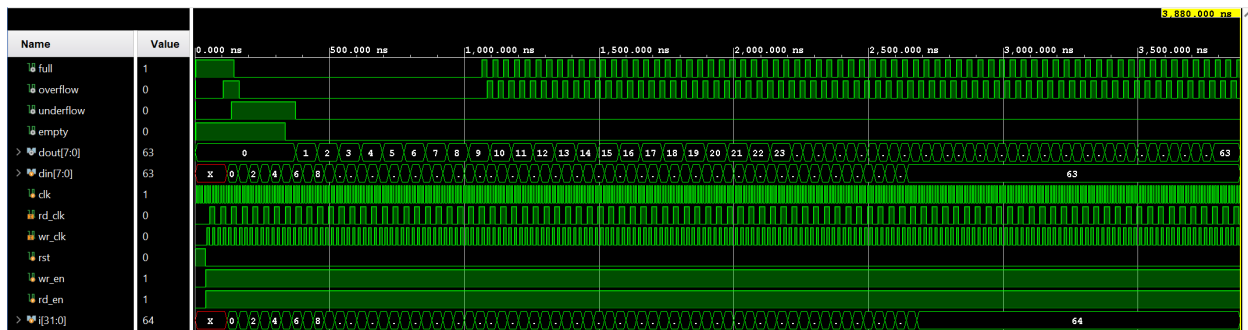

FIFO Behavioral Simulation

Primitives		
Ref Name	Used	Functional Category
FDRE	42	Flop & Latch
FDCE	24	Flop & Latch
LUT2	17	LUT
OBUF	12	IO
IBUF	12	IO
FDPE	10	Flop & Latch
LUT4	8	LUT
LUT6	6	LUT
LUT3	5	LUT
LUT5	4	LUT
LUT1	3	LUT
BUFG	3	Clock
RAMB18E1	1	Block Memory


FIFO Primitive Usage

- clk_25MHz (25.00 MHz) (drives 35 loads)
 - Q (counter_reg[1]/Q)
 - rd_clk (rd_clk)
 - I (rd_clk_BUFG_inst/I)
 - rd_clk_BUFG_inst (BUFG)
 - O (rd_clk_BUFG_inst/O)
 - rd_clk_BUFG (rd_clk_BUFG)
 - clk_50MHz (50.00 MHz) (drives 44 loads)
 - Q (counter_reg[0]/Q)
 - counter_reg_n_0_[0] (counter_reg_n_0_[0])
 - I (counter_reg_n_0_[0]_BUFG_inst/I)
 - counter_reg_n_0_[0]_BUFG_inst (BUFG)
 - O (counter_reg_n_0_[0]_BUFG_inst/O)
 - counter_reg_n_0_[0]_BUFG (counter_reg_n_0_[0]_BUFG)
 - clk_100MHz (100.00 MHz) (drives 2 loads)
 - clk
 - I (clk_IBUF_inst/I)
 - clk_IBUF_inst (IBUF)
 - O (clk_IBUF_inst/O)
 - clk_IBUF (clk_IBUF)
 - I (clk_IBUF_BUFG_inst/I)
 - clk_IBUF_BUFG_inst (BUFG)
 - O (clk_IBUF_BUFG_inst/O)
 - clk_IBUF_BUFG (clk_IBUF_BUFG)

Clock Network Reports




Clock Interaction Report

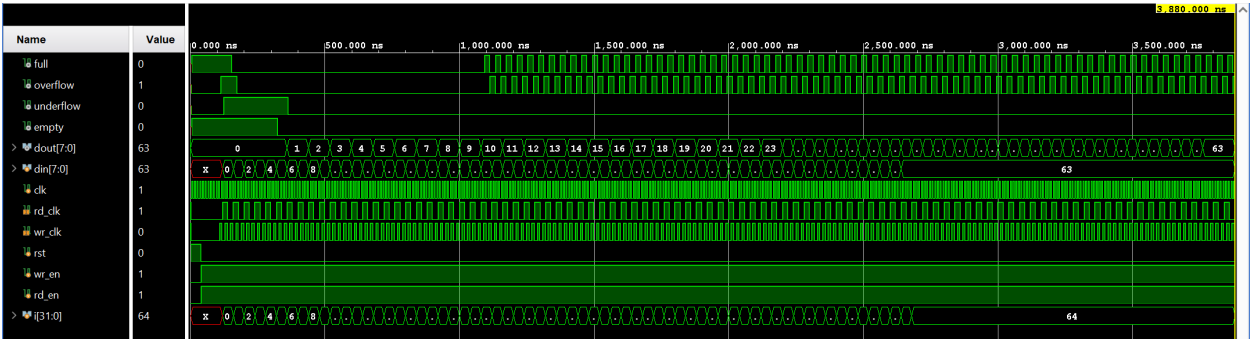

FIFO Post-Implementation Timing Simulation

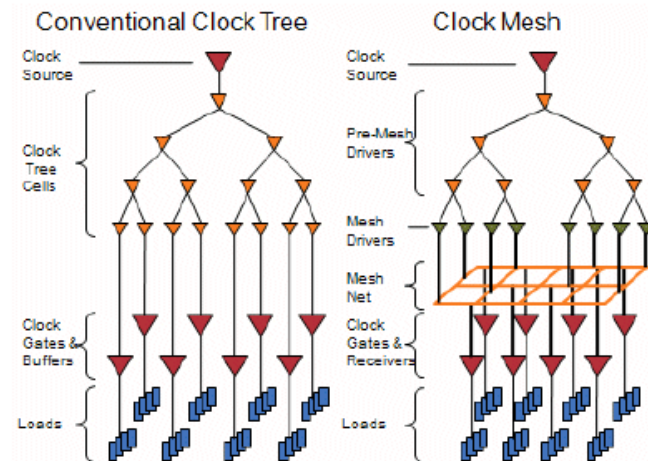5. Research

Clock Tree Synthesis (CTS) aims to distribute the clock signal from a single clock source to all clocked elements in a design while minimizing skew and maintaining signal integrity.




CTS Figure¹

A clock tree is a hierarchical network of buffers, inverters, and interconnect wires that distribute the clock signal. It starts at the clock source and branches out to clock sinks. The topology can be:

- H-Tree: Balanced tree structure for equal latency.
- Spine or Mesh: Grid-based clock distribution, typically used in high-frequency designs.
- Buffered Tree: Uses buffers at branching points to strengthen the clock signal.


Clock Tree Architecture

 

Clock Tree Architecture²

Dual FF Synchronizer:

Clock Domain Crossing (CDC) occurs when signals pass from one clock domain to another domain with a different clock frequency or phase relationship. CDC introduces the risk of metastability, where a flip-flop enters an unstable state and delays the signal propagation. The **dual flip-flop synchronizer** is a common technique used to address metastability. It ensures that data crossing clock domains stabilizes before it is used in the new clock domain.

 

Dual FF Figure with Clocks & Outputs³

- **First Flip-Flop:** Captures the signal from the source clock domain and allows metastability to resolve over one clock cycle.
- **Second Flip-Flop:** Further stabilizes the signal, ensuring that it is safe to use in the destination clock domain.
- The two flip-flops act as a buffer, allowing metastability to settle while ensuring signal integrity.

References

- 1- <https://www.design-reuse.com/articles/21019/clock-mesh-benefits-analysis.html>
- 2- <https://slideplayer.com/slide/4442868/>
- 3- https://commons.wikimedia.org/wiki/File:2FF_synchronizer.gif