

Chapter 3 – Combinational Digital Circuit Design

Part 1 – Implementation Technology and Logic Design

Overview


- **Part 1 – Design Procedure**
 - **Steps**
 - **Specification**
 - **Formulation**
 - **Optimization**
 - **Technology Mapping**
 - **Beginning Hierarchical Design**
 - **Technology Mapping - AND, OR, and NOT to NAND or NOR**
 - **Verification**
 - **Manual**
 - **Simulation**

Overview (continued)

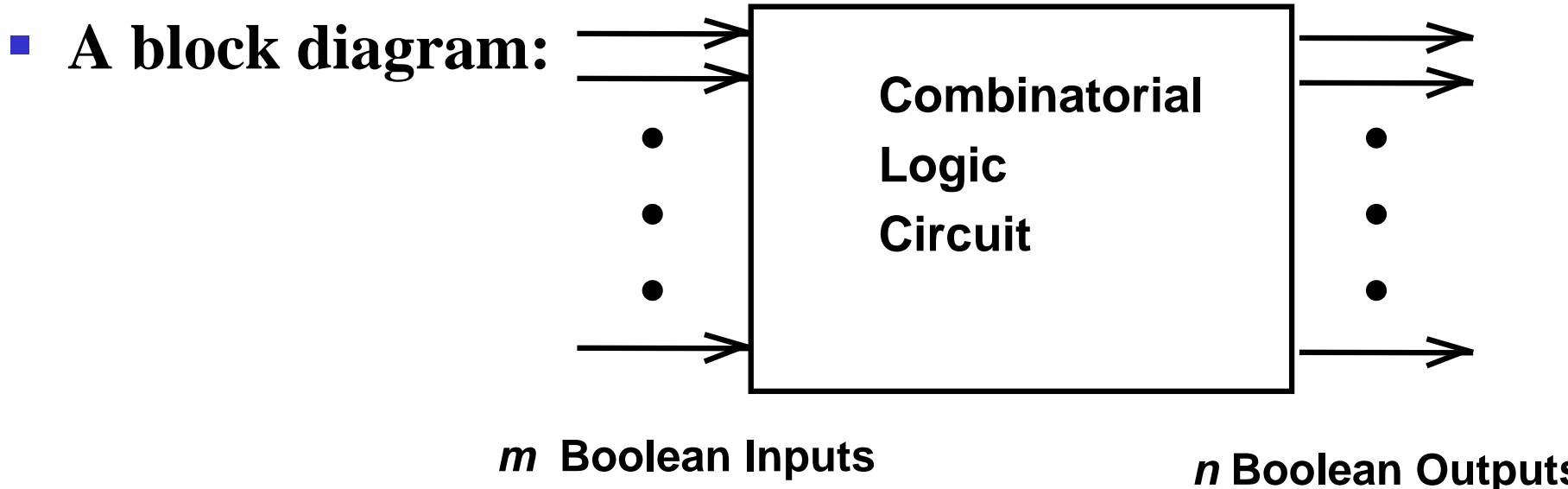- **Part 2 – Combinational Logic**
 - **Functions and functional blocks**
 - **Rudimentary logic functions**
 - **Decoding using Decoders**
 - **Implementing Combinational Functions with Decoders**
 - **Encoding using Encoders**
 - **Selecting using Multiplexers**
 - **Implementing Combinational Functions with Multiplexers**

Combinational Circuits

- A combinational logic circuit has:
 - A set of m Boolean inputs,
 - A set of n Boolean outputs, and
 - n switching functions, each mapping the 2^m input combinations to an output such that the current output depends only on the current input values




Analysis of Combinational Digital Circuits

- **Analysis:** Finding the Boolean function that a digital circuit implements
 - A digital circuits is given.
 - We should find
 1. Boolean function
 2. Truth table
 3. Some information about the operation of the digital circuit.

Finding the Boolean Function

Example

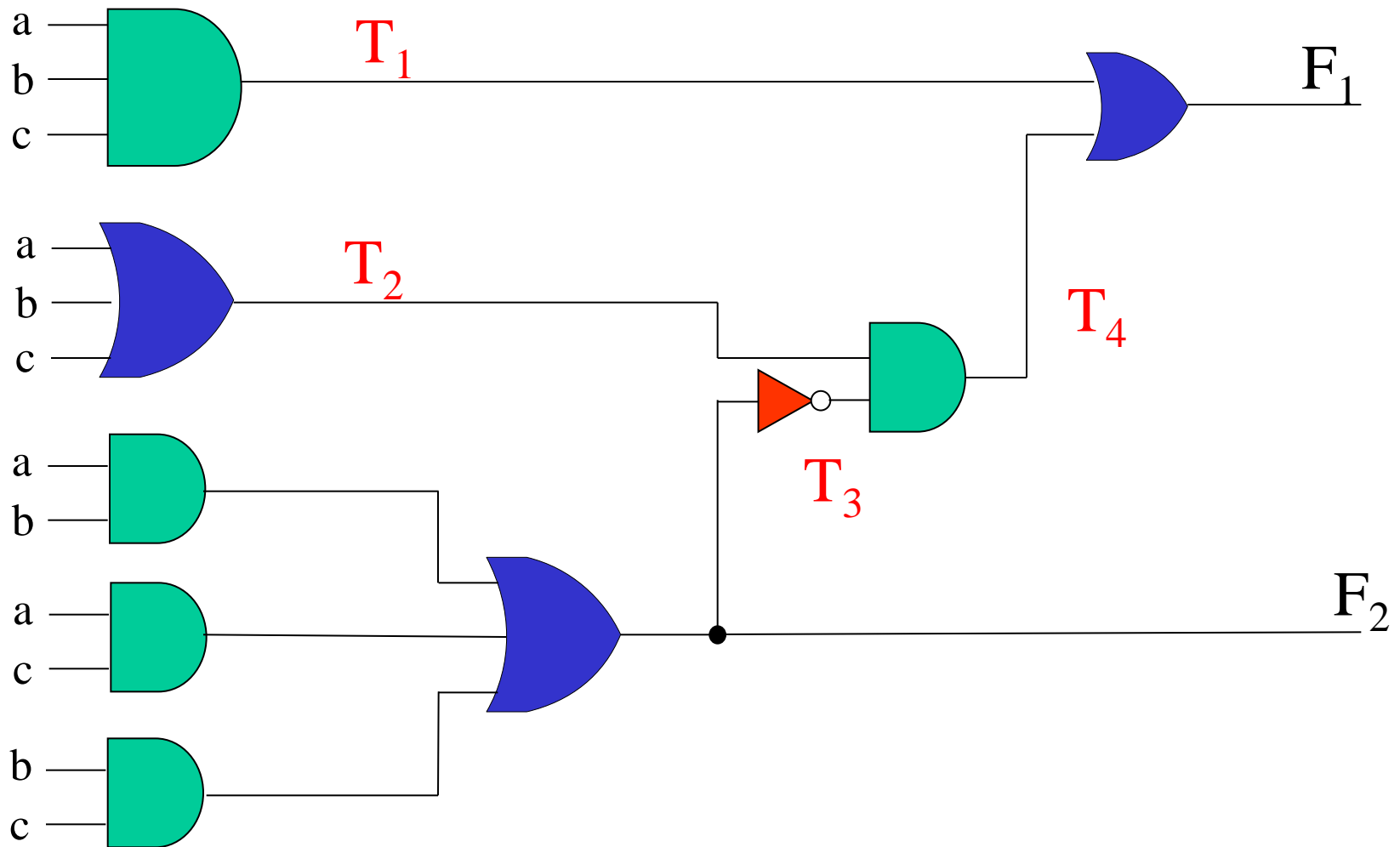

Example: Finding the Boolean Function

- The Boolean functions of the shown points on the circuit
 - $T_1 = abc$
 - $T_2 = a + b + c$
 - $F_2 = ab + ac + bc$
 - $T_3 = F_2' = (ab + ac + bc)'$
 - $T_4 = T_3 T_2 = (ab + ac + bc)' (a + b + c)$
 - $F_1 = T_1 + T_4$
 - $= abc + (ab + ac + bc)' (a + b + c)$
 - $= abc + ((a' + b')(a' + c')(b' + c')) (a + b + c)$
 - $= abc + ((a' + a'c' + a'b' + b'c')(b' + c')) (a + b + c)$
 - $= abc + (a'b' + a'c' + a'b'c' + a'b' + a'b'c' + b'c' + b'c') (a + b + c)$

Example: Finding the truth table

$$F_1 = a \oplus b \oplus c$$

$$F_2 = ab + ac + bc$$

							elde	toplama
a	b	c	T_1	T_2	T_3	T_4	F_2	F_1
0	0	0	0	0	1	0	0	0
0	0	1	0	1	1	1	0	1
0	1	0	0	1	1	1	0	1
0	1	1	0	1	0	0	1	0
1	0	0	0	1	1	1	0	1
1	0	1	0	1	0	0	1	0
1	1	0	0	1	0	0	1	0
1	1	1	1	1	0	0	1	1

Full Adder (FA)

Design Procedure

1. Specification

- Write a specification for the circuit if one is not already available

2. Formulation

- Derive a truth table or initial Boolean equations that define the required relationships between the inputs and outputs, if not in the specification
- Apply hierarchical design if appropriate

3. Optimization

- Apply 2-level and multiple-level optimization
- Draw a logic diagram or provide a netlist for the resulting circuit using ANDs, ORs, and inverters

Design Procedure

4. Technology Mapping

- Map the logic diagram or netlist to the implementation technology selected

5. Verification

- Verify the correctness of the final design manually or using simulation

Addition Circuit

■ Addition of two 2-bit numbers

- $Z = X + Y$
- $X = (x_1 \ x_0)$ and $Y = (y_1 \ y_0)$
- $Z = (z_2 \ z_1 \ z_0)$

■ Addition of bits

$$s_0 = x_0 \oplus y_0$$

$$c_1 = x_0 y_0 \text{ (carry)}$$

$$2. \ s_1 = x_1 \oplus y_1 \oplus c_1$$

$$c_2 = x_1 y_1 + x_1 c_1 + y_1 c_1$$

$$3. \ s_2 = c_2$$

x_i	y_i	c_i	s_i	c_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Carry: 0 0 0 0 0

$$\begin{array}{r} x: \quad 0 \ 1 \ 1 \ 0 \ 0 \quad 12 \\ y: \quad + \ 1 \ 0 \ 0 \ 0 \ 1 \quad 17 \\ \hline \text{Sum:} \quad 1 \ 1 \ 1 \ 0 \ 1 \quad 29 \end{array}$$

0 1 1 0 0

$$\begin{array}{r} \quad 1 \ 0 \ 1 \ 1 \ 0 \quad 22 \\ + \ 1 \ 0 \ 1 \ 1 \ 1 \quad 23 \\ \hline 1 \ 0 \ 1 \ 1 \ 0 \ 1 \quad 45 \end{array}$$

Note:

1. The carry input to the LSB is always '0'
2. The sum of two n -bit numbers has $n+1$ bits



$$X = (x_2, x_1, x_0)_2$$

$$Y = (y_2, y_1, y_0)_2$$

$$S = X + Y = (s_3, s_2, s_1, s_0)_2$$

$$C = (c_2, c_1, c_0)_2$$

x_i	y_i	c_i	C_{i+1}	S_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

x_i, y_i, c_i	00	01	11	10
0	0	0	1	0
1	0	1	1	1

$$C_{i+1} = x_i y_i' + y_i c_i' + x_i c_i'$$

x_i, y_i, c_i	00	01	11	10
0	0	1	0	1
1	1	0	1	0

$$S_i = x_i' y_i' c_i' + x_i' y_i' c_i + x_i' y_i c_i' + x_i' y_i c_i$$

$$= c_i' (x_i' y_i' + x_i' y_i)$$

$$+ c_i (x_i' y_i' + x_i' y_i)$$

$$= c_i' (x_i \oplus y_i) + c_i (x_i \oplus y_i)'$$


$$= c_i \oplus x_i \oplus y_i$$

XOR


$$X \oplus Y = x'y + xy'$$

$$(X \oplus Y)' = x'y' + xy$$


→ XNOR

 

Full Adder
FA

 

Half adder
HA

 

Ripple Carry Adder
RCA


Addition Circuit for 2 bits addition

$$s_1 = x_1 \oplus y_1 \oplus e_1$$

$$s_2 = c_2 \quad c_2 = x_1 y_1 + x_1 c_1 + y_1 c_1$$

$$s_0 = x_0 \oplus y_0$$

$$c_1 = x_0 y_0$$

 

Full Adder


Half Adder

Integer Adder 1/2


■ n-bit Binary Adder:

- $A = (a_{n-1}, a_{n-2}, \dots, a_1, a_0)$
- $B = (b_{n-1}, b_{n-2}, \dots, b_1, b_0)$
- $A + B = S = (s_n, s_{n-1}, s_{n-2}, \dots, s_1, s_0)$

■ 4-bit Binary Adder:

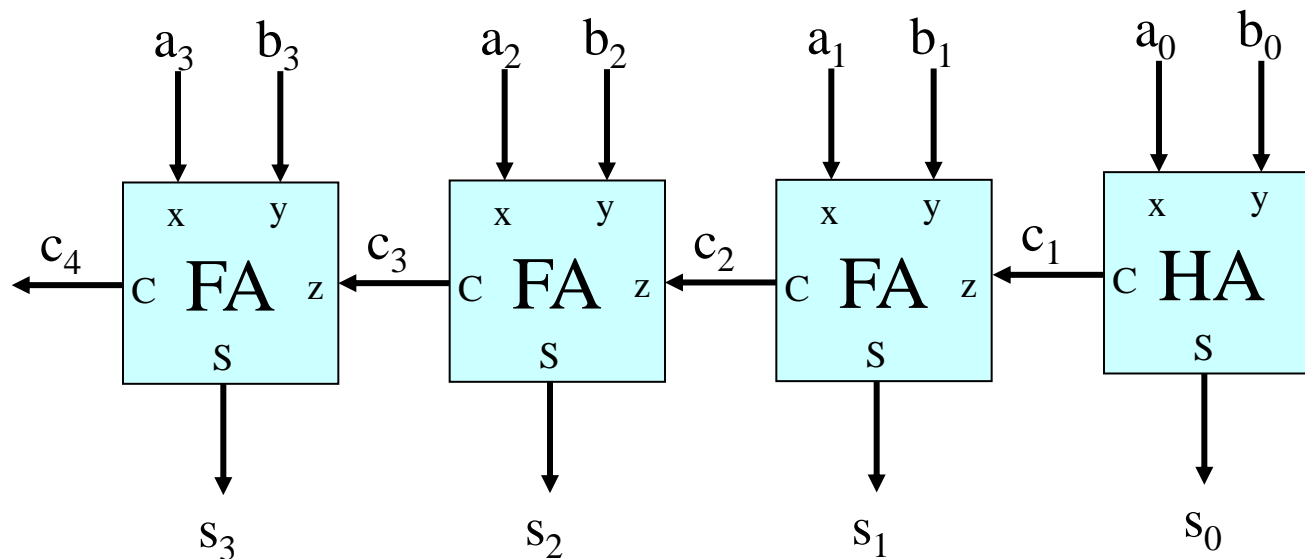

Integer Adder 2/2

 

Ripple-carry adder

Reusable Functions

- We used top-down design method in ripple carry adder design.
- If we would use classical design method:
 - Number of inputs: 8
 - Number of outputs: 5
 - A truth table with $2^9 = 512$ is needed
 - We have to optimize 5 Boolean functions with 9 variables
- When reuse functions
 - We decompose the design to simpler operation blocks.
 - We design the complex function by the use of sub-blocks.

Reusable Functions

- **Whenever possible, we try to decompose a complex design into common, *reusable* function blocks**
- **These blocks are**
 - **verified and well-documented**
 - **placed in libraries for future use**

Top-Down versus Bottom-Up

- A *top-down design* proceeds from an abstract, high-level specification to a more and more detailed design by decomposition and successive refinement
- A *bottom-up design* starts with detailed primitive blocks and combines them into larger and more complex functional blocks
- Design usually proceeds top-down to known building blocks ranging from complete CPUs to primitive logic gates or electronic components.
- Much of the material in this chapter is devoted to learning about combinational blocks used in top-down design.

Verification

- **Verification - show that the final circuit designed implements the original specification**
- **Simple specifications are:**
 - truth tables
 - Boolean equations
 - HDL code
- **If the above result from formulation and are not the original specification, it is critical that the formulation process be flawless for the verification to be valid!**

Basic Verification Methods

■ Manual Logic Analysis

- Find the truth table or Boolean equations for the final circuit
- Compare the final circuit truth table with the specified truth table, or
- Show that the Boolean equations for the final circuit are equal to the specified Boolean equations

■ Simulation

- Simulate the final circuit (or its netlist, possibly written as an HDL) and the specified truth table, equations, or HDL description using test input values that fully validate correctness.
- The obvious test for a combinational circuit is application of all possible “care” input combinations from the specification