

# **Chapter 2 – Combinational Digital Circuits**

## **Part 3 – Additional Gates and Circuits**

# Overview

- **Part 1 – Gate Circuits and Boolean Equations**
  - **Binary Logic and Gates**
  - **Boolean Algebra**
  - **Standard Forms**
- **Part 2 – Circuit Optimization**
  - **Two-Level Optimization**
  - **Map Manipulation**
  - **Practical Optimization (Espresso)**
  - **Multi-Level Circuit Optimization**
- **Part 3 – Additional Gates and Circuits**
  - **Other Gate Types**
  - **Exclusive-OR Operator and Gates**
  - **High-Impedance Outputs**

# Other Gate Types

## ■ Why?

- Implementation feasibility and low cost
- Power in implementing Boolean functions
- Convenient conceptual representation

## ■ Gate classifications

- Primitive gate - a gate that can be described using a single primitive operation type (AND or OR) plus an optional inversion(s).
- Complex gate - a gate that requires more than one primitive operation type for its description

## ■ Primitive gates will be covered first

# AND, OR, NOT Operations

- They are defined by Boolean functions.
- They represent 3 functions out of 16 possible two variable functions.


x	y	F <sub>0</sub>	F <sub>1</sub>	F <sub>2</sub>	F <sub>3</sub>	F <sub>4</sub>	F <sub>5</sub>	F <sub>6</sub>	F <sub>7</sub>
0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1

x	y	F <sub>8</sub>	F <sub>9</sub>	F <sub>10</sub>	F <sub>11</sub>	F <sub>12</sub>	F <sub>13</sub>	F <sub>14</sub>	F <sub>15</sub>
0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1


# Other Logic Operations

- **Some of the two variable Boolean functions**
  - **Constant functions**:  $F_0 = 0$  and  $F_{15} = 1$
  - **AND function**:  $F_1 = xy$
  - **OR function**:  $F_7 = x + y$
  - **ExclusiveOR function (XOR)**:
    - $F_6 = x' y + xy' = x \oplus y$  (x or y, but not both)
  - **Equivalence function (XNOR)**:
    - $F_9 = xy + x' y' = (x \oplus y)'$  (x equals to y)
  - **NOR function**:
    - $F_8 = (x + y)' = (x \downarrow y)$  (Not-OR)
  - **NAND function**:
    - $F_{14} = (x y)' = (x \uparrow y)$  (Not-AND)


# Logic Gate Symbols

 


NOT

 


BUFFER

 


AND

 


XOR

 


OR

 

XNOR

 


NAND

 

NOR
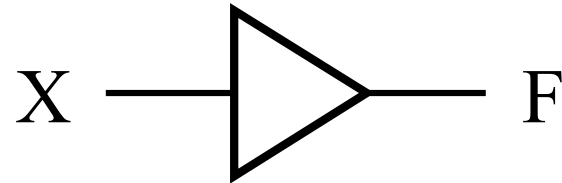
# Buffer


- A buffer is a gate with the function  $F = X$ :



- In terms of Boolean function, a buffer is the same as a connection!
- So why use it?
  - A buffer is an electronic amplifier used to improve circuit voltage levels and increase the speed of circuit operation.
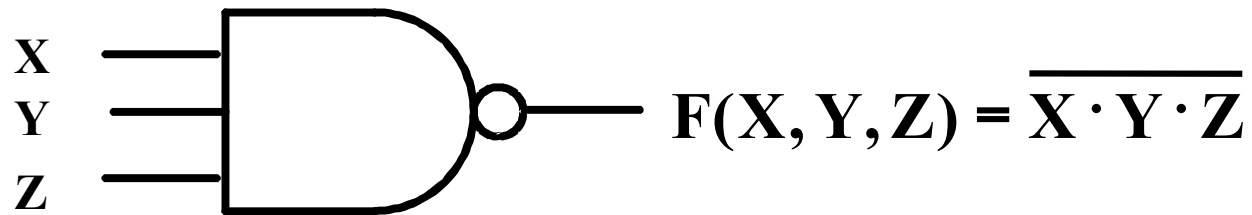
# NAND Gate

- The basic NAND gate has the following symbol, illustrated for three inputs:
  - **AND-Invert (NAND)**




- NAND represents NOT AND, i. e., the AND function with a NOT applied. The symbol shown is an AND-Invert. The small circle (“bubble”) represents the invert function.


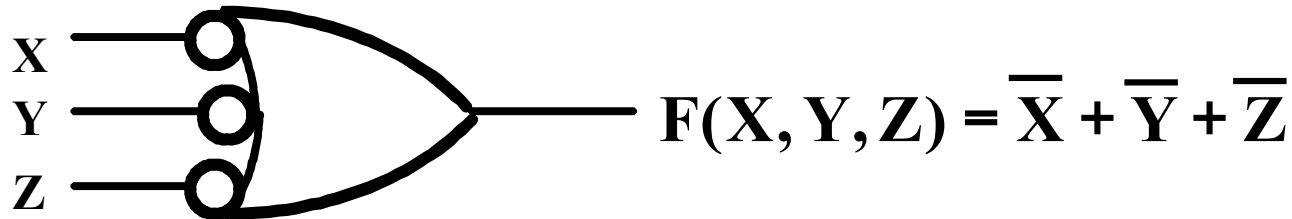
# NAND Gates (continued)

- Applying DeMorgan's Law gives Invert-OR (NAND)




- This NAND symbol is called Invert-OR, since inputs are inverted and then ORed together.
- AND-Invert and Invert-OR both represent the NAND gate. Having both makes visualization of circuit function easier.
- A NAND gate with one input degenerates to an inverter.

# NAND Gates (continued)

- **The NAND gate is the natural implementation for CMOS technology in terms of chip area and speed.**
- ***Universal gate* - a gate type that can implement any Boolean function.**
- **The NAND gate is a universal gate as shown in Figure 2-24 of the text.**
- **NAND usually does not have a operation symbol defined since**
  - **the NAND operation is not associative, and**
  - **we have difficulty dealing with non-associative mathematics!**
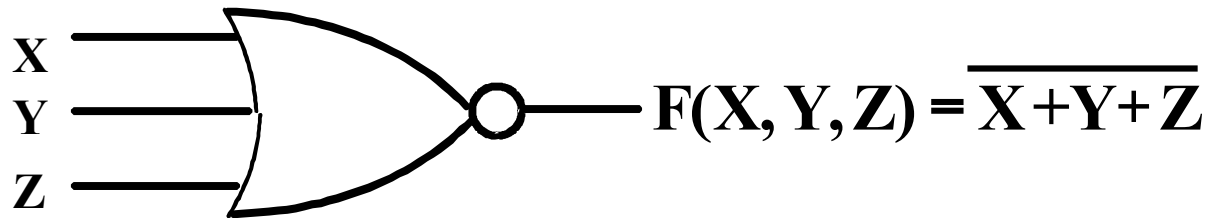
# NOR Gate


- The basic NOR gate has the following symbol, illustrated for three inputs:
  - OR-Invert (NOR)



- NOR represents NOT - OR, i. e., the OR function with a NOT applied. The symbol shown is an OR-Invert. The small circle (“bubble”) represents the invert function.
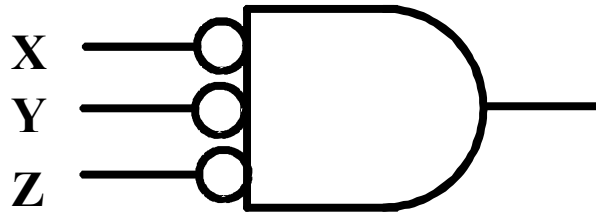
# NOR Gate (continued)

- Applying DeMorgan's Law gives Invert-AND (NOR)



- This NOR symbol is called Invert-AND, since inputs are inverted and then ANDed together.
- OR-Invert and Invert-AND both represent the NOR gate. Having both makes visualization of circuit function easier.
- A NOR gate with one input degenerates to an inverter.

# NOR Gate (continued)

- **The NOR gate is a natural implementation for some technologies other than CMOS in terms of chip area and speed.**
- **The NOR gate is a universal gate**
- **NOR usually does not have a defined operation symbol since**
  - **the NOR operation is not associative, and**
  - **we have difficulty dealing with non-associative mathematics!**

# Exclusive OR/ Exclusive NOR

- The *eXclusive OR (XOR)* function is an important Boolean function used extensively in logic circuits.
- The XOR function may be;
  - implemented directly as an electronic circuit (truly a gate) or
  - implemented by interconnecting other gate types (used as a convenient representation)
- The *eXclusive NOR* function is the complement of the XOR function
- By our definition, XOR and XNOR gates are complex gates.

# Exclusive OR/ Exclusive NOR

- Uses for the XOR and XNORs gate include:
  - Adders/subtractors/multipliers
  - Counters/incrementers/decrementers
  - Parity generators/checkers
- Definitions
  - The XOR function is:  $X \oplus Y = X \bar{Y} + \bar{X} Y$
  - The eXclusive NOR (XNOR) function, otherwise known as *equivalence* is:  $\overline{X \oplus Y} = X Y + \bar{X} \bar{Y}$
- Strictly speaking, XOR and XNOR gates do not exist for more than two inputs. Instead, they are replaced by odd and even functions.

# Truth Tables for XOR/XNOR

- Operator Rules: XOR

X	Y	$X \oplus Y$
0	0	0
0	1	1
1	0	1
1	1	0

## XNOR

X	Y	$\overline{(X \oplus Y)}$ or $X \equiv Y$
0	0	1
0	1	0
1	0	0
1	1	1

- The XOR function means:

**X OR Y, but NOT BOTH**

- Why is the XNOR function also known as the *equivalence* function, denoted by the operator  $\equiv$ ?



# XOR/XNOR (Continued)

- The XOR function can be extended to 3 or more variables. For more than 2 variables, it is called an *odd function* or *modulo 2 sum (Mod 2 sum)*, not an XOR:

$$X \oplus Y \oplus Z = \overline{X} \overline{Y} Z + \overline{X} Y \overline{Z} + X \overline{Y} \overline{Z} + X Y Z$$

- The complement of the odd function is the even function.
- The XOR identities:

$$X \oplus 0 = X$$

$$X \oplus X = 0$$

$$X \oplus Y = Y \oplus X$$


$$(X \oplus Y) \oplus Z = X \oplus (Y \oplus Z) = X \oplus Y \oplus Z$$

$$X \oplus 1 = \overline{X}$$


$$X \oplus \overline{X} = 1$$
 
# XOR Implementations

- The simple SOP implementation uses the following structure:



- A NAND only implementation is:



 


# Universal Gate



- **NAND and NOR gates are universal.**
- **All Boolean functions can be implemented by AND, OR and NOT gates.**
- **These operations can be implemented by NAND and NOR gates.**

$x$	$y$	$(xy)'$	$x'$	$y'$	$(x' y')'$
0	0	1	1	1	0
0	1	1	1	0	1
1	0	1	0	1	1
1	1	0	0	0	1

# NAND Gates

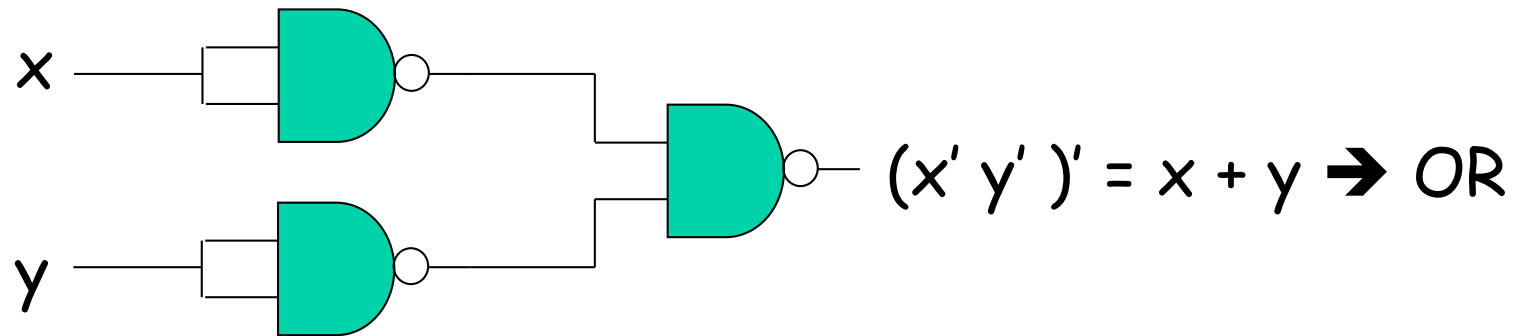  


# NOR Gate

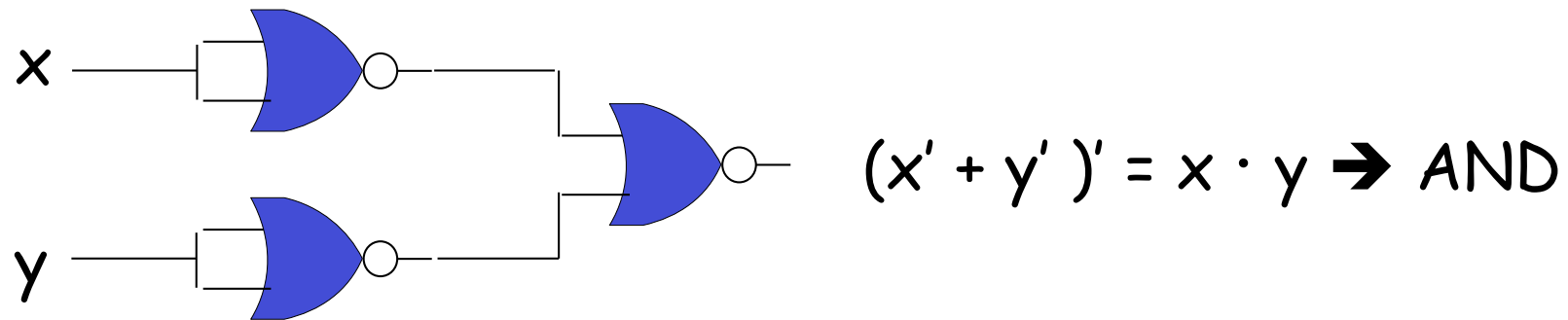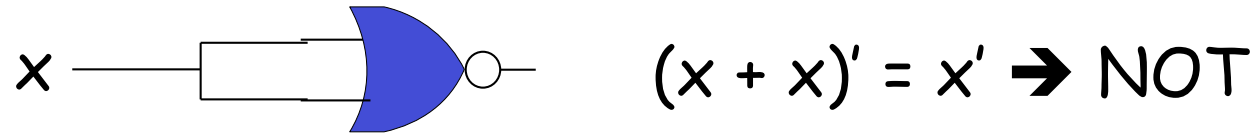


# Example 1

- $F_1 = x' y + x y'$

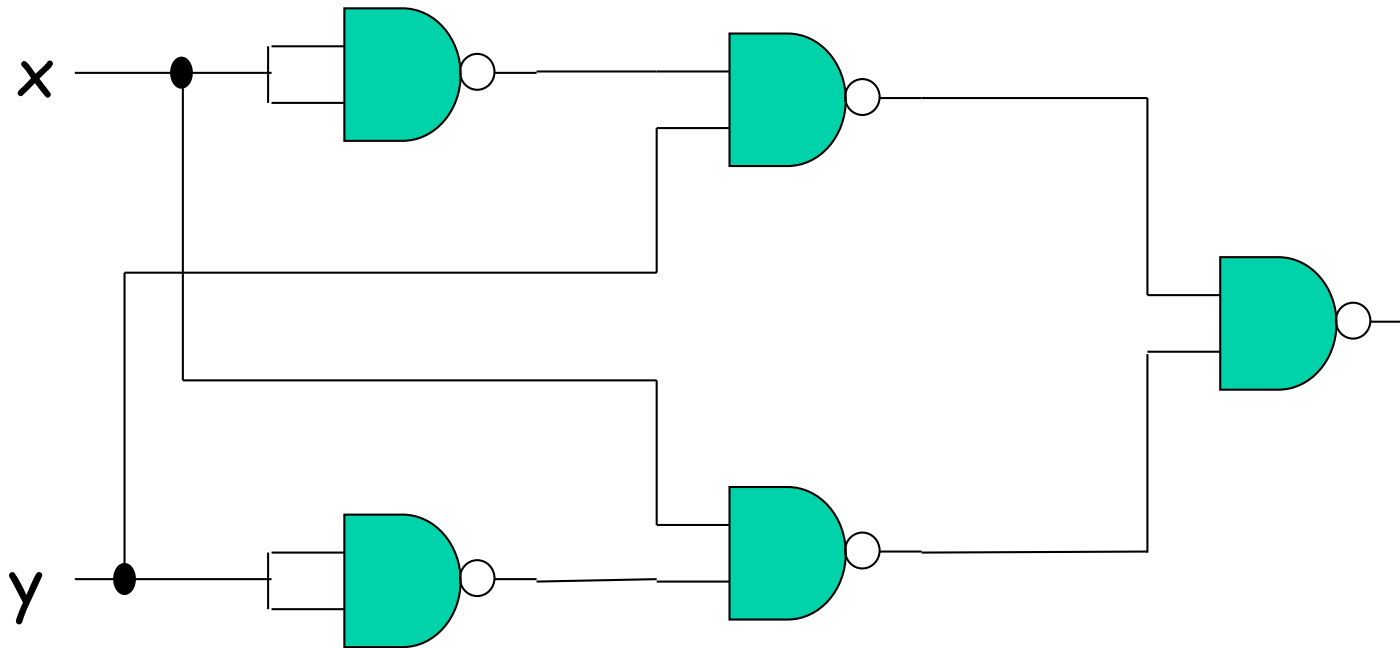

## Example 2

- $F_2 = x' y' + xy'$

 

# Multiple Input Gates

- **AND and OR gates:**

- Commutative and associative properties exist.
- There is no problem to increase the number of inputs.

- **NAND and NOR gates:**

- They have commutative, but not associative property.
- It is not easy to increase the number of inputs.

- **Example: NAND gates**

- $((x \text{ y})'z)' \neq (x(yz)')'$

- $((xy)'z)' = ((x'+y')z)' = xy+yz'$

- $(x (yz)')' = x'+yz$

