



Very Large Scale Integration II - VLSI II

Digital Design Methodology

ITU VLSI Laboratories

Istanbul Technical University



Outline

- Properties of Digital Circuits
- Implementation Methods
 - Programmable Logic
 - Semi Custom
 - Full Custom
- Project Constraints
- Digital Circuit Representations
- Digital Design Considerations
- Digital Design Flow



Properties of Digital Circuits

- Most general form
 - Inputs + Present State \rightarrow Output + Next State
- For most cases, only 1 and 0
 - No 0.5 or Z
- Less specifications
 - Delay
 - Transition
 - Power
 - Area




Properties of Digital Circuits

- Combinational
 - Inputs \rightarrow Output
- Sequential
 - Moore Type
 - Inputs \rightarrow Next State
 - Present State \rightarrow Output
 - Mealy Type
 - Inputs + Present State \rightarrow Output + Next State



Properties of Digital Circuits

 
- Delay = Gate Delay + Interconnect Delay
- Gate Delay





Properties of Digital Circuits


- Interconnect Delay

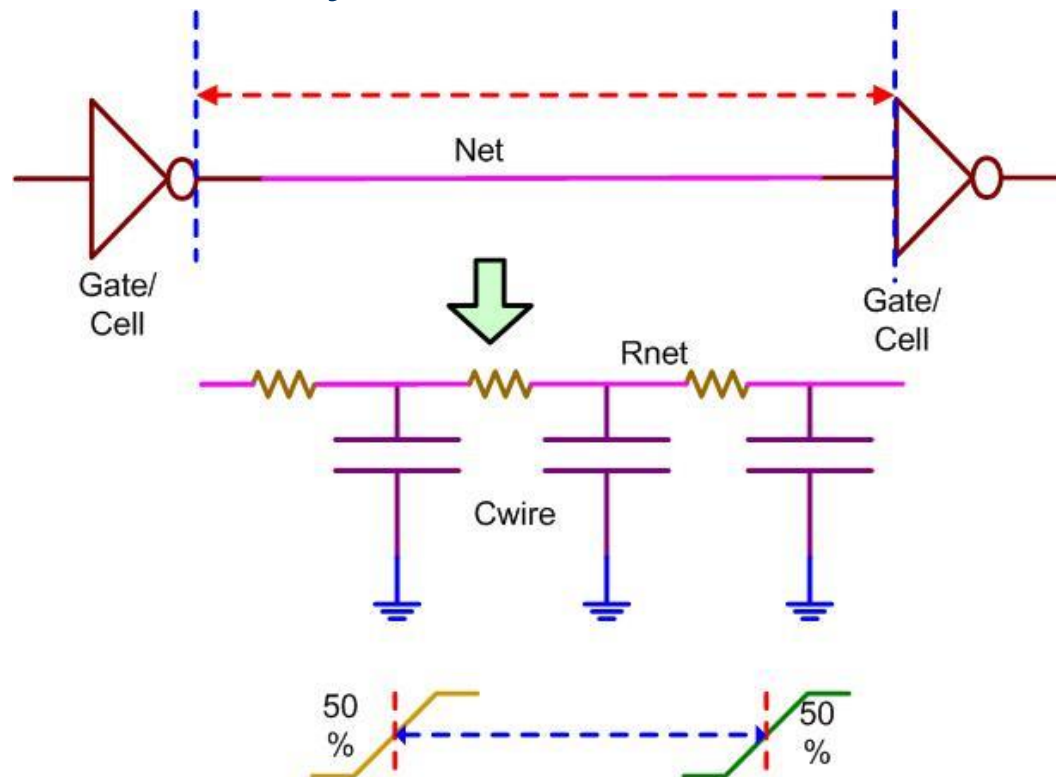



Properties of Digital Circuits

- Transition

 





Implementation Methods

- Programmable Logic (FPGA, CPLD, PLA, PAL)
- Semi Custom (ASIC, Standard Cell)
- Full Custom



Programmable Logic


● PLA and PAL

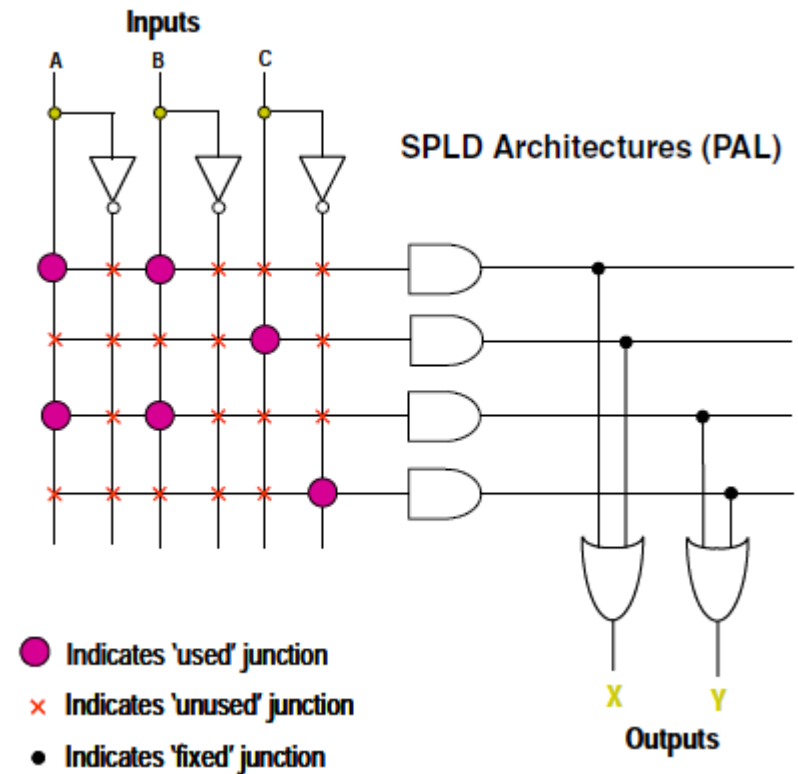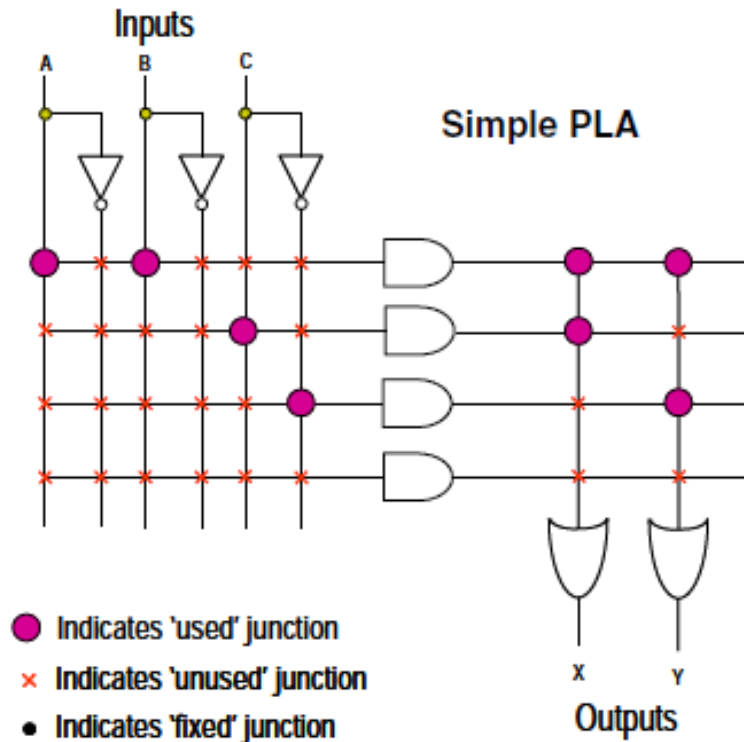



Programmable Logic


- CPLD

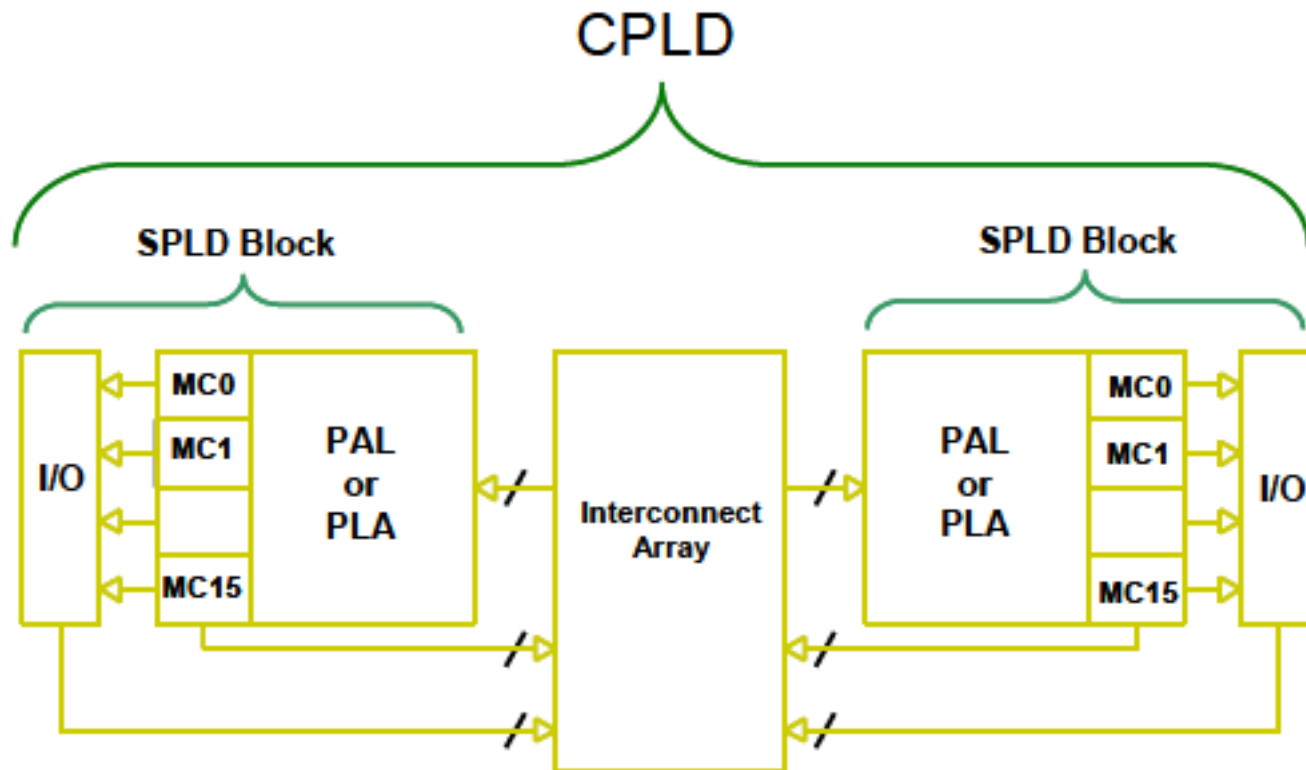



Programmable Logic

 
- **FPGA**
 - **CLB (LUT)**
 - Interconnect
 - PLL, DCM
 - I/O





Programmable Logic

 
- **FPGA**
 - CLB (LUT)
 - **Interconnect**
 - PLL, DCM
 - I/O





Programmable Logic

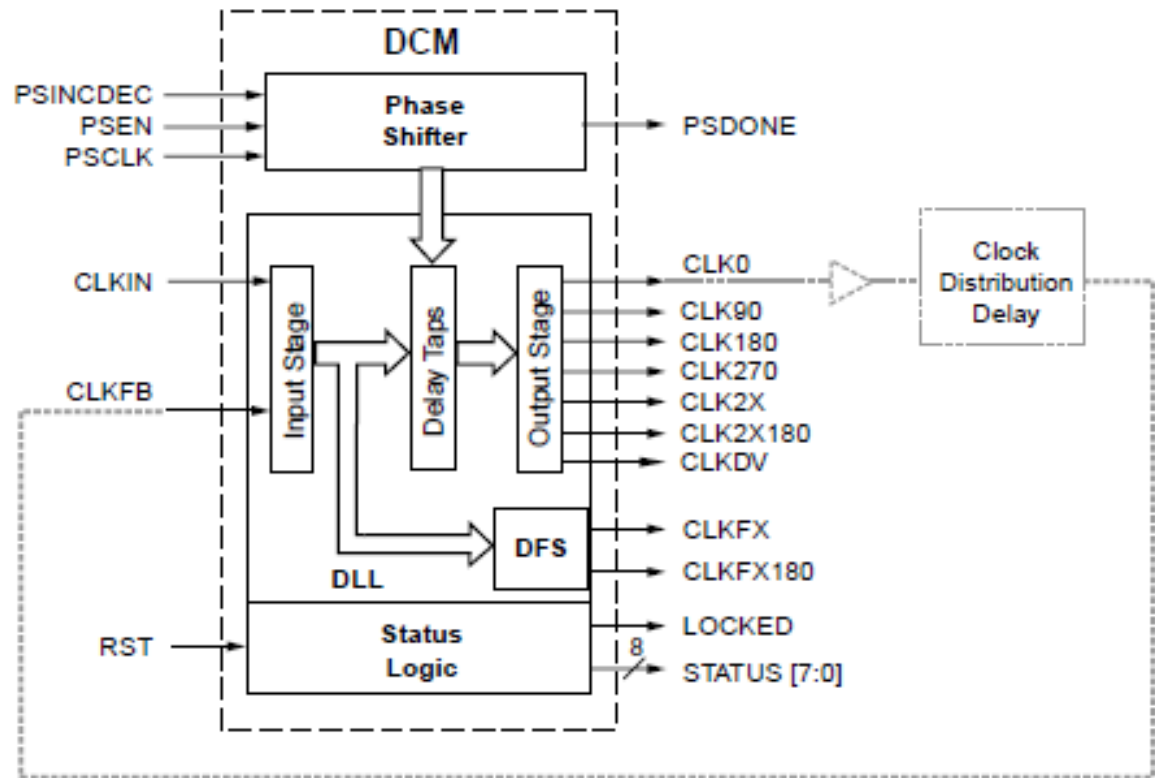
- FPGA
 - CLB (LUT)
 - Interconnect
 - **PLL, DCM**
 - I/O





Programmable Logic

 - FPGA
 - CLB (LUT)
 - Interconnect
 - PLL, DCM
 - I/O





Programmable Logic

- FPGA Design
 - Architecture Driven
 - Dedicated Multipliers
 - FFT
 - CPU
 - No Area Control
 - %1 utilization cost = %100 utilization cost
 - Limited Power Control



Semi Custom

- Logic Cells from Process
- Technology Specific
- Generic Gates
 - Function
 - Driving Capacity
- Well Characterized Delay & Transition
 - Supply
 - Temperature
 - Process Corner
 - Load
- Systematic Layout (LEGO Parts)



Full Custom

- Analog/RF design methods
- Design from scratch
- Custom schematic
- Custom layout








ENGINEERING THE FUTURE





Project Constraints

	Time to market	Volume	Performance
FPGA			
Semi Custom			
Full Custom			



Digital Circuit Representations

TOP DOWN

BOTTOM UP

- Behavioral
 - Define what the digital circuit does
- Register Transfer Level (RTL)
 - Define the logical operations of busses and wires
- Structural
 - Define the gates and the connections between them
- Gate Level
 - Schematic representation at the gate level
- Transistor Level
 - Schematic representation at the transistor level



Digital Circuit Representations

- Behavioral

```
module FA_behavioral(a, b, carry_in, carry_out, sum);
```

```
    input a, b, carry_in;  
    output carry_out, sum;
```

```
    reg [1:0] tmp;  
    reg carry_out, sum;
```

```
    always@(a or b or carry_in) begin  
        tmp = a + b + carry_in;  
        sum = tmp[0];  
        carry_out = tmp[1];
```

```
    end  
endmodule
```



Digital Circuit Representations

- Register Transfer Level (RTL)

```
module FA_RTL(a, b, carry_in, carry_out, sum);
```

```
    input a, b, carry_in;  
    output carry_out, sum;
```

```
    wire x1, x2, x3;
```

```
    assign x1 = a ^ b;  
    assign sum = x1 ^ carry_in;  
    assign x2 = x1 & carry_in;  
    assign x3 = a & b;  
    assign carry_out = x2 | x3;
```

```
endmodule
```



Digital Circuit Representations

- Structural

```
module FA_structural(a, b, carry_in, carry_out, sum);
```

```
    input a, b, carry_in;  
    output carry_out, sum;
```

```
    wire x1, x2, x3;
```


```
    XOR U1(a, b, x1);  
    XOR U2(x1, carry_in, sum);  
    AND U3(x1, carry_in, x2);  
    AND U4(a, b, x3);  
    OR U5(x2, x3, carry_out);
```

```
endmodule
```




Digital Circuit Representations


- Gate Level

 



Digital Circuit Representations

- Transistor Level

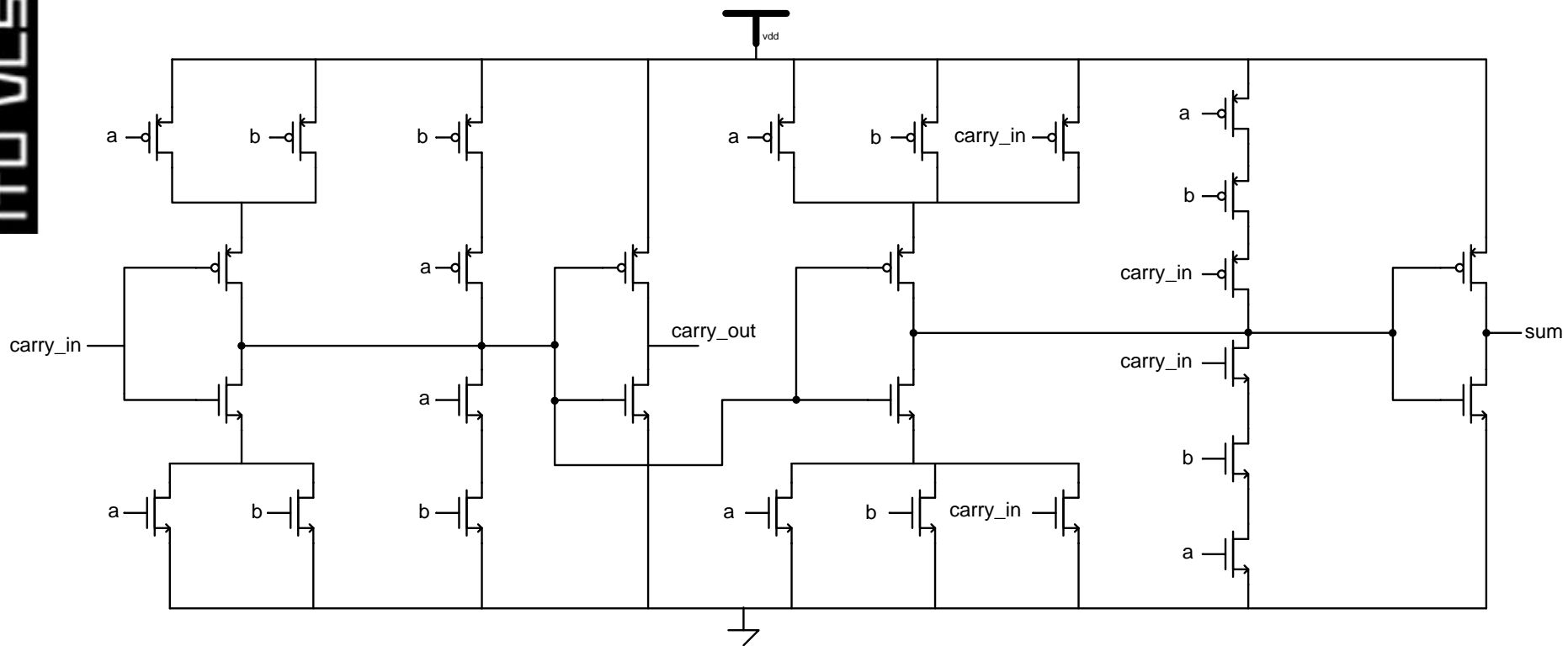




Digital Design Considerations

- Digital Design \neq “Let do and let pass, the world goes on by itself!” Vincent de Gournay
- Digital Design \neq Do-it-all tools
- One should:
 - Consider code style
 - Consider coding for an architecture
 - Investigate the tool outputs
 - Know how synthesizer thinks



Digital Design Flow

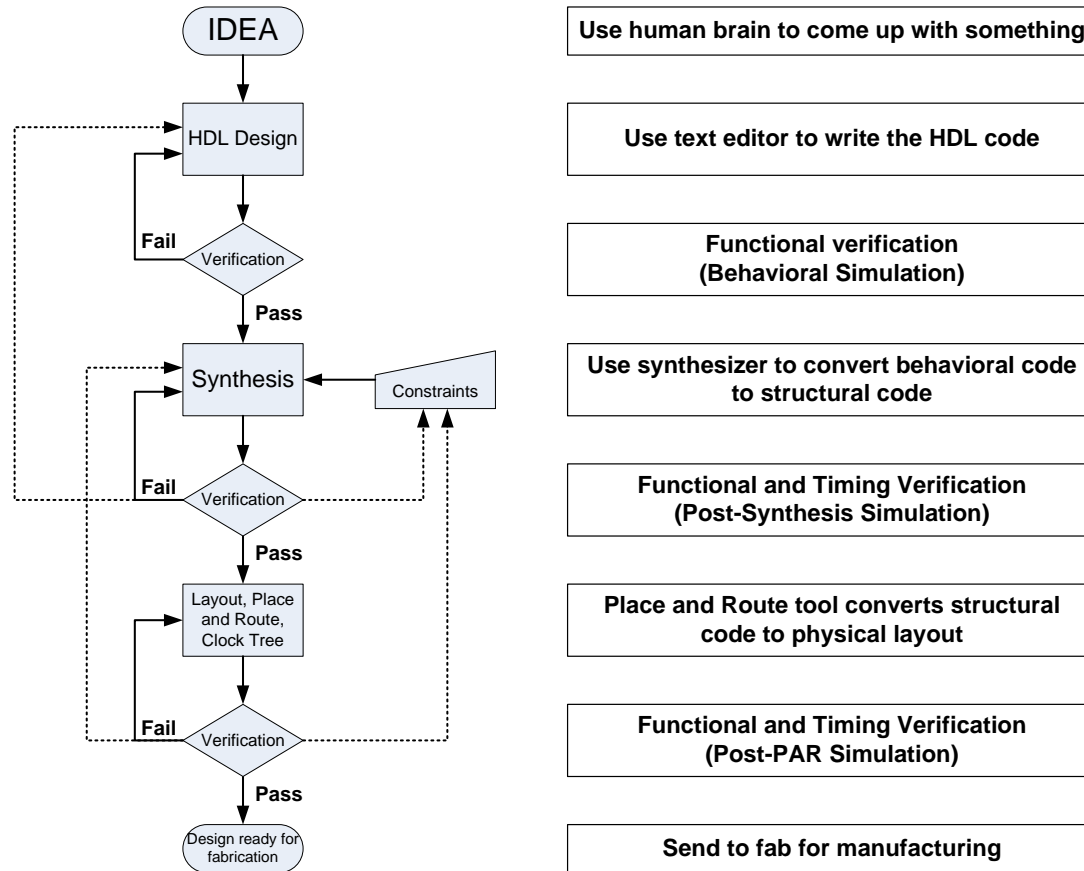



References

- http://ocw.mit.edu/NR/rdonlyres/Electrical-Engineering-and-Computer-Science/6-111Spring2004/F19D2F2D-5FE9-4C59-AA67-D2113639B022/0/l6_fsm_toCMS_080904.pdf
- <http://asic-soc.blogspot.com/2008/12/transition-delay-and-propagation-delay.html>
- <http://asic-soc.blogspot.com/2008/10/net-delay.html>
- http://people.bu.edu/rknepper/sc571/chapter4_b.ppt
- http://www.xilinx.com/publications/products/cpld/logic_handbook.pdf
- [http://en.wikipedia.org/wiki/Adder_\(electronics\)](http://en.wikipedia.org/wiki/Adder_(electronics))
- <http://www.askkia.com/articles/how-to-create-a-single-bit-full-adder.html>