



# ISTANBUL TECHNICAL UNIVERSITY

Digital System Design & Applications

*Verilog HDL*

RES. ASST. FIRAT KULAK

# Introduction



**Hardware Description Languages (HDLs)** are used to describe digital logic circuits without being tied to a specific electronic technology.

**HDLs** uses **Register-transfer level (RTL)** abstraction model.


**Register-transfer level (RTL)** means the flow of digital signals (data) between hardware registers and logical operators.

RTL is a high-level representation of a digital circuit.

RTL does not consider the physical hardware (real hardware).


The details of gates and their interconnections (**Gate-Level Netlist**) are extracted by logic synthesis tools (e.g. Vivado, Genus) from the RTL description.

# Introduction

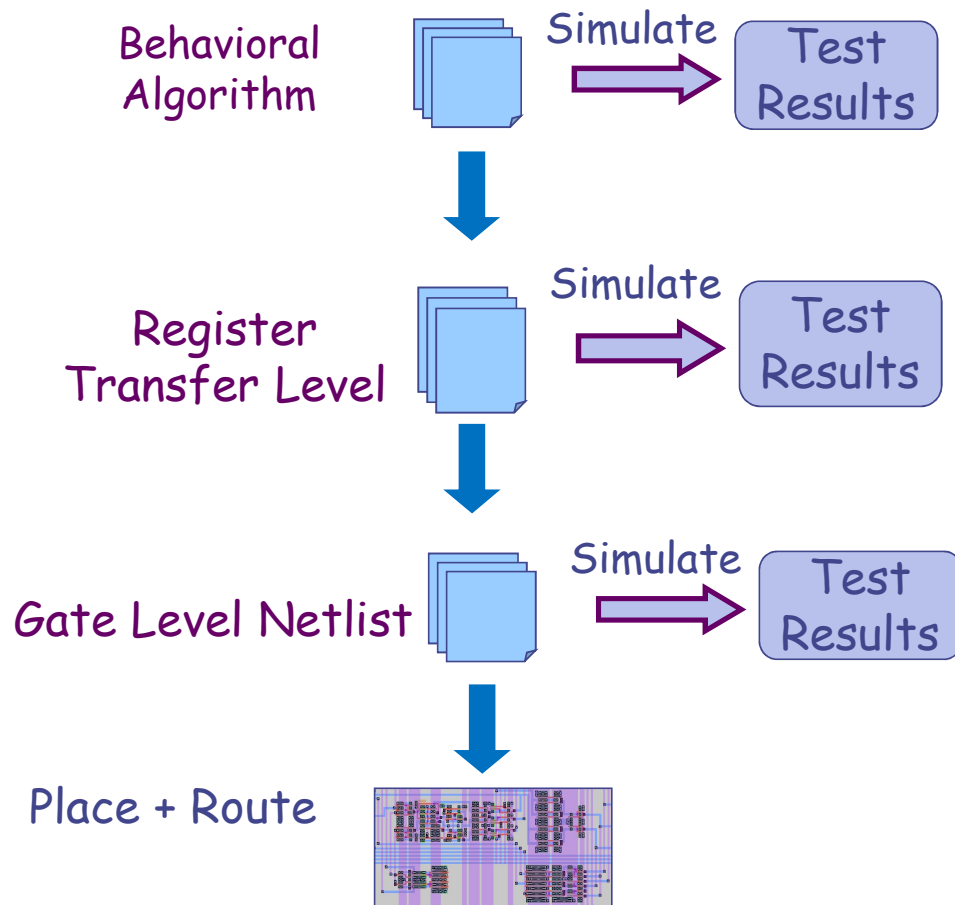

- Coding HDL, C - C++, MATLAB or Python.
- Describing the behavior of the circuit.
- **Textual** representation.
- High-level representation of the circuit.
- Describing registers and combinatorial logic.
- **Schematical** representation at high-level.
- Generating gates and their interconnections using synthesis tools.
- **Schematical** representation.
- Generate the layout (physical chip/circuit) by using placement/routing tools.
- **Physical** representation.

# Introduction

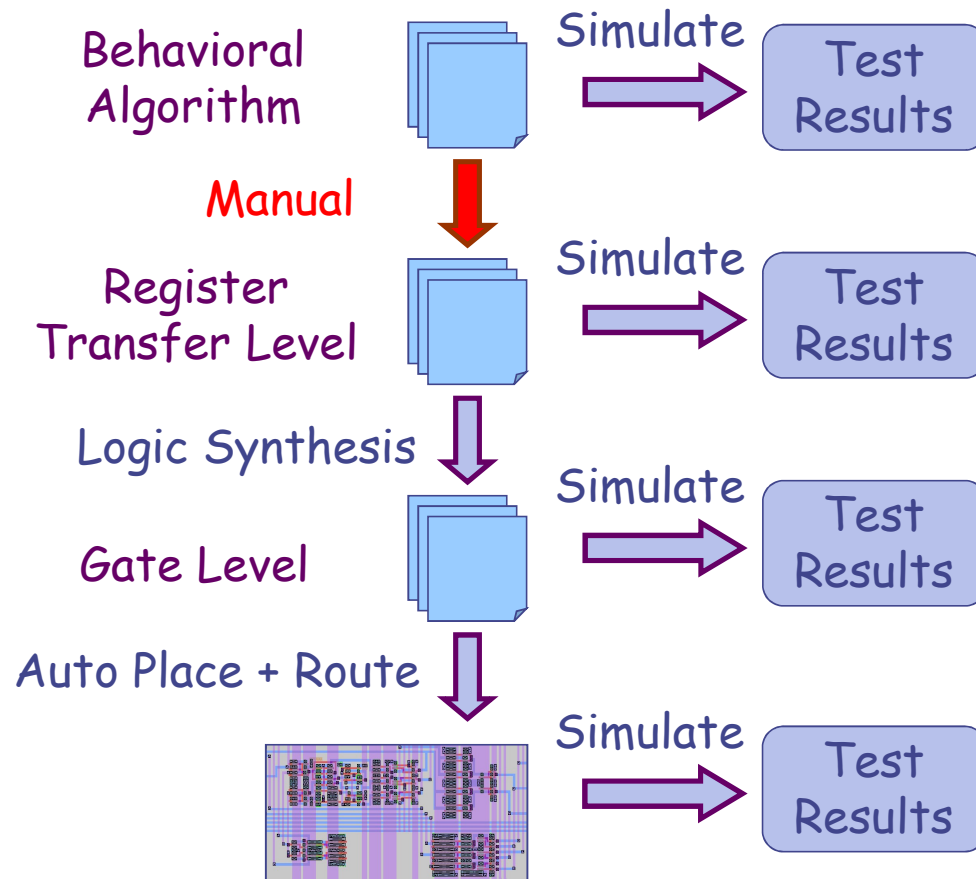

❖ HDL tools are used for automatic translation.

- ❖ In each step we need to simulate and verify our design.
- Behavioral Simulation
  - RTL Sim.
  - Post Synthesis Sim.
  - Post Imp Sim.

# Introduction




## Verilog Code


```
module and2( output z, input x, input y);  
    assign z = x&y;  
endmodule
```




## RTL Description

 

## Gate-Level Netlist

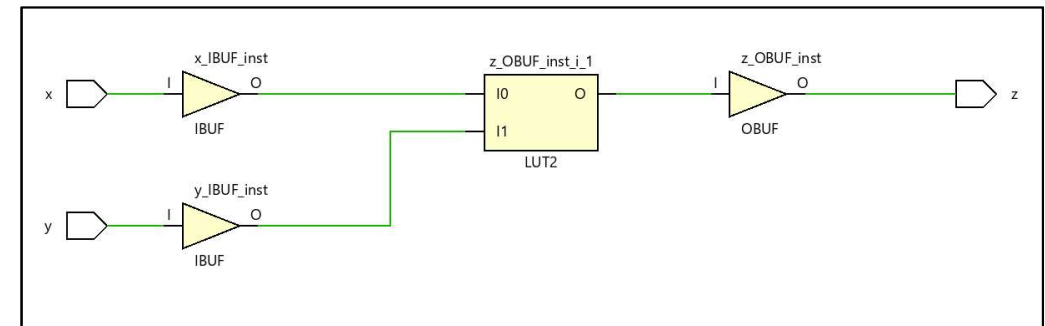

## Layout

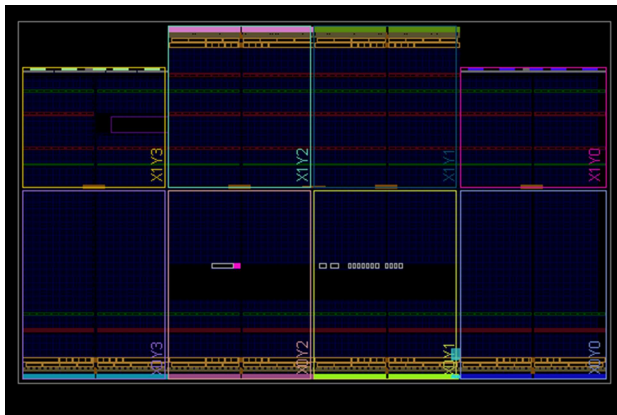

Taken from Vivado, Xilinx Nexsys 4 DDR FPGA Chip  
Artix-7 XC7A100T-1CSG324C

# Introduction



The most commonly used HDLs are **Verilog HDL** and **VHDL**.

For simulation and Verification:

VHDL, SystemVerilog, Verilog, UVM

**Intel Altera FPGAs:** Quartus, Modelsim (old)

**Xilinx FPGAs:** Vitis-Vivado

**For Asic Designs:** Cadence Virtuoso

Xcelium (RTL Sim)

Genus (Synthesis)

Innovus (Place/Route)

Calibre (DRC Check), Quantus(Noise), Tempus(Temperature), Voltus(Power Integrity) and others.

# Introduction



Verilog is **NOT** a programming language.

In terms of hardware description, Verilog **ONLY** describes the behavior of digital circuits. Testbenches are another story.

Verilog code is inherently **concurrent** contrary to regular programming languages, which are sequential ( C, C++, Python ).

# Verilog Basics - Lexical Conventions



- ❑ White space: Spaces, tabs, newlines...
- ❑ Comments: One-line and block comments, same as C,C++
- ❑ Operators
- ❑ Numbers
- ❑ Strings
- ❑ Identifiers
- ❑ Keywords
- ❑ System Tasks/Functions
- ❑ Compiler Directives
- ❑ Attributes

```
module hello_world(  
    input A,B,C,  
    output Z  
);  
  
assign Z = (A==C) ? 1'b1 : (~A | B) & C;  
  
// A one-line comment  
  
/*  
    This is a  
    block comment  
*/  
  
endmodule
```

Diagram illustrating Verilog lexical conventions:

- Identifiers:** `hello_world`, `A`, `B`, `C`, `Z` (indicated by red arrows).
- Keywords:** `module`, `input`, `output`, `assign`, `endmodule` (indicated by blue arrows).
- Number:** `1'b1` (indicated by an orange arrow).
- Operators:** `=`, `?`, `:`, `~`, `|`, `&` (indicated by a green arrow).



# Verilog Basics - Value Set




- ❑ In hardware modeling aspect Verilog HDL consists of four basic values:

Value	What it represents
0	Logic zero, or a false condition
1	Logic one, or a true condition
x	Unknown logic value
z	High-impedance state

# Verilog Basics - Number Representations



`<size> ' <base format> <number>`

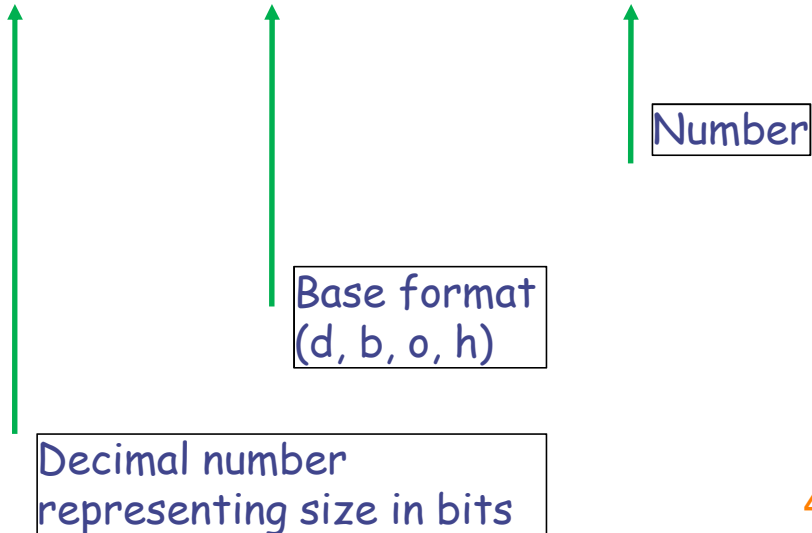


- `<size>` is written only in decimal and specifies the number of bits in the number.
- Base formats are decimal ('d or 'D), hexadecimal ('h or 'H), binary ('b or 'B) and octal ('o or 'O).

```
4'b1111 // This is a 4-bit binary number
12'habc  // This is a 12-bit hexadecimal number
16'd255  // This is a 16-bit decimal number.
```

# Verilog Basics - Number Representations



`<size> ' <base format> <number>`

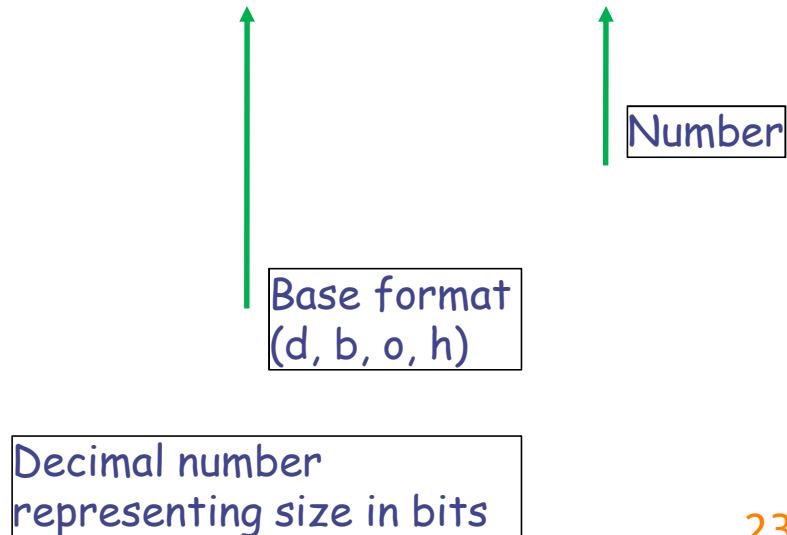

- Numbers that are written without a `<size>` specification have a default number of bits that is simulator- and machine-specific (must be at least 32).
- Numbers that are specified without a `<base format>` specification are decimal numbers by default.

```
23456 // This is a 32-bit decimal number by default  
'hc3  // This is a 32-bit hexadecimal number  
'o21  // This is a 32-bit octal number
```

# Verilog Basics - Number Representations



`<size> ' <base format> <number>`



Decimal number  
representing size in bits



Base format  
(d, b, o, h)



Number

- Negative numbers can be specified by putting a minus sign before the size for a constant number.
- Negative numbers are always specified as 2's complement form of the corresponding number.

`-6'd3` // 6-bit negative number stored as 2's complement of 3

// 111101 => -3

# Verilog Basics - Number Representations



- Verilog has two symbols for **unknown** and **high impedance** values. An unknown value is denoted by an **X**. A high impedance value is denoted by **Z**.
- If the most significant bit of a number is 0, x, or z, the number is automatically extended to fill the most significant bits, respectively, with 0, x, or z.

```
12'h13x // This is a 12-bit hex number; 4 least significant bits unknown
6'hx    // This is a 6-bit unknown hex number
32'bz   // This is a 32-bit high impedance number
```

# Verilog Basics - Number Representations



- An underscore character "\_" is allowed anywhere in a number except the first character.
- Underscore characters are allowed only to improve readability of numbers and are ignored by Verilog.

```
12'b1111_0000_1010 // Use of underline characters for readability
```

# Verilog Basics - Modules



- ❑ Modules are the basic building blocks in Verilog
- ❑ Communicates with the outside world via its inputs and outputs (ports)
- ❑ A module has a **unique name, a port list and a parameter list** (more on this later)
- ❑ **Two alternative module declarations:**

```
module <module_name>
( <port_name_list> );

    <declare_port_directions>

    /*
    *   Functionality of the circuitry
    *   described by this module
    */

endmodule
```

Verilog-1995 style

```
module <module_name>
( <port_list_with_directions> );

    /*
    *   Functionality of the circuitry
    *   described by this module
    */

endmodule
```

Verilog-2001 style

# Verilog Basics - Modules



- ❑ Inputs and outputs of a module are called PORTS of this module
- ❑ In Verilog, a port can have 3 possible directions:

Keyword	Behaviour
input	Input port
output	Output port
inout	Bidirectional port



# Verilog Basics - Modules



## □ Example module declarations:

```
module mystery_box( I1, I2, O1);  
  
    input I1,I2;  
    output O1;  
  
    /*  
        Functionality of the circuitry  
        described by this module  
    */  
  
endmodule
```

Verilog-1995 style



```
module mystery_box(  
    input I1,I2,  
    output O1  
);  
  
    /*  
        Functionality of the circuitry  
        described by this module  
    */  
  
endmodule
```

Verilog-2001 style
  
# Verilog Basics - Modules



```
module mystery_box(  
    input I1,  
    input I2,  
    output O1  
);  
  
    /*  
     * Functionality of the circuitry  
     * described by this module  
     */  
  
endmodule
```



- This current code represents an empty box with two single-bit inputs named I1,I2; and a single-bit output named O1


# Verilog Basics - wire keyword

- ❑ "wire" keyword represent physical nets in the design.
- ❑ Like in real circuits, nets have values that are continuously driven on them
- ❑ Ports are wires by default (originated from Verilog-1995)
- ❑ Wires can be declared inside a module body.

```
wire w0;           // A one bit wire declaration
wire a,b,c;        // Three different one-bit wire declarations
wire [4:0] interconnect; // A five bit wire declaration
wire [7:0] bus_A, bus_B; // Two different eight-bit wire declarations
```
 
# Verilog Basics - wire keyword

- ❑ "wire" keyword represent physical nets in the design.
- ❑ Like in real circuits, nets have values that are continuously driven on them
- ❑ Ports are **wires** by default (originated from Verilog-1995)
- ❑ Wires can be declared inside a module body.



```
wire W0,W1,W2,W3;
```


Or...

```
wire W0;
wire W1;
wire W2;
wire W3;
```

Note that ports X,Y,Z are already treated as wires by default, so there's no need to re-identify those
 
# Verilog Basics - wire keyword

- ❑ "wire" keyword represent physical nets in the design.
- ❑ Like in real circuits, nets have values that are continuously driven on them
- ❑ Ports are **wires** by default (originated from Verilog-1995)
- ❑ Wires can be declared inside a module body.



Or...

```
wire [3:0] W;
```

Then these wires would be represented by  
W[0],W[1],W[2],W[3]

# Verilog Basics - assign keyword

- ❑ "assign" keyword is used to specify a driver for a wire
- ❑ Continuous assignments, always active.
- ❑ The assignment expression is evaluated as soon as the right-hand-side expression changes.
- ❑ Assign can be used inside a module body, but outside a procedural block (more on this later)

```
assign <net_name> = <expression>;
```

```
wire A1, A2;
```

```
wire B1, B2;
```

```
assign B1 = A1 & A2    // Assign bitwise and of A1 and A2 to B1
```

```
assign B2 = 1;        // Assign constant logic-1 to B2.
```


# Verilog Basics - assign keyword

□ Let's add some new stuff to our mystery box...

```
module mystery_box(
    input I1,
    input I2,
    output O1
);


    assign O1 =

endmodule
```

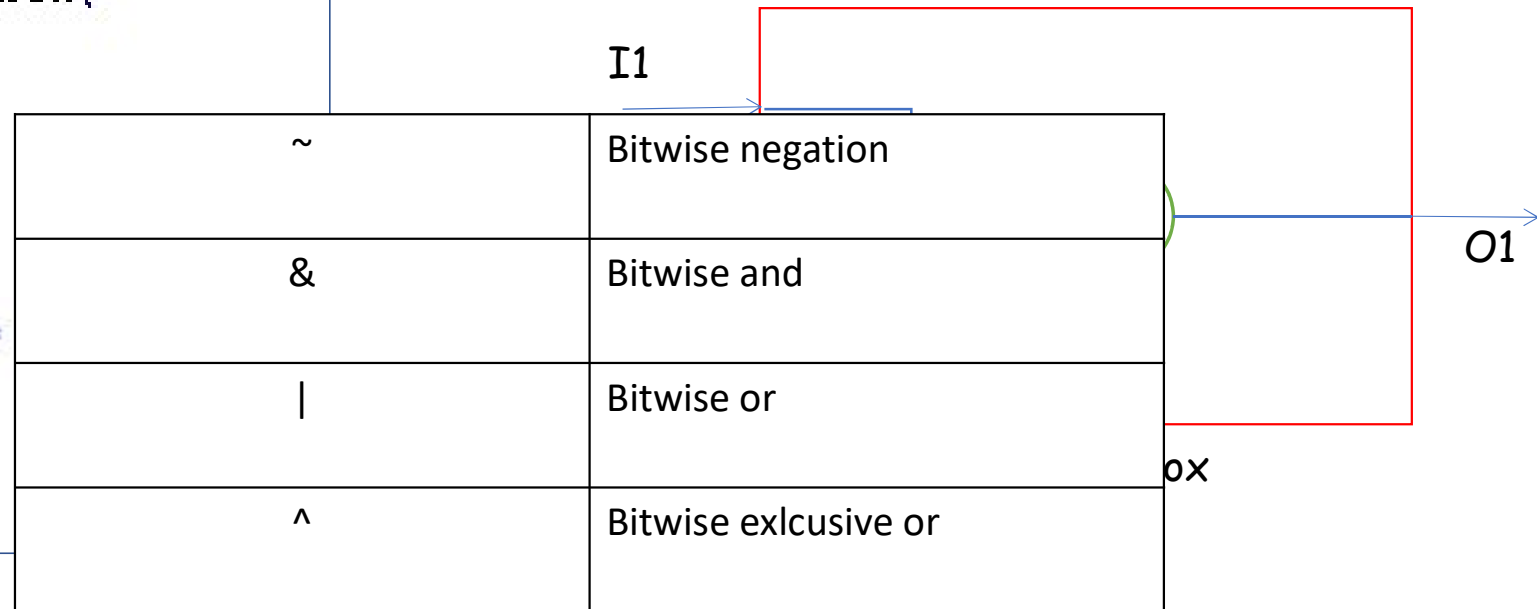

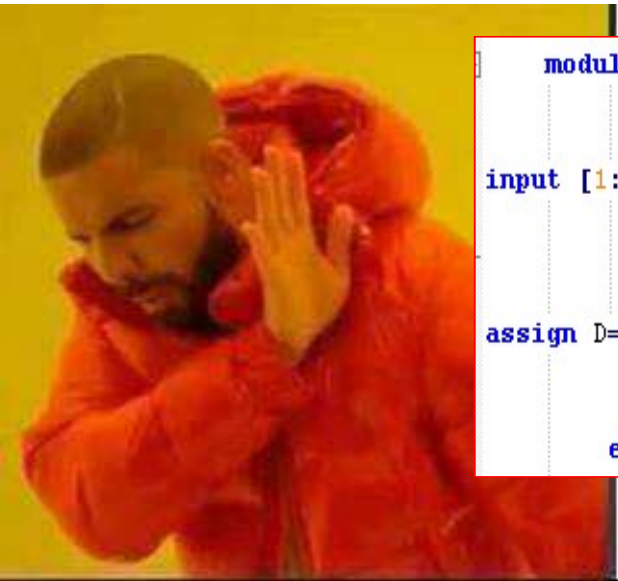□ And operator represented an and gate...





```


module asdfasdfasd( input A, input B
                    input C,
                    output D,
input [1:0] sel,output address_3

                    );

assign D= A&~sel[0]&~sel[1]|b&~sel[0]&sel[1]|C&sel[0]&~sel[1]|D&sel[0]&sel[1];assign address_3=sel[1]&&sel[0];

endmodule

```

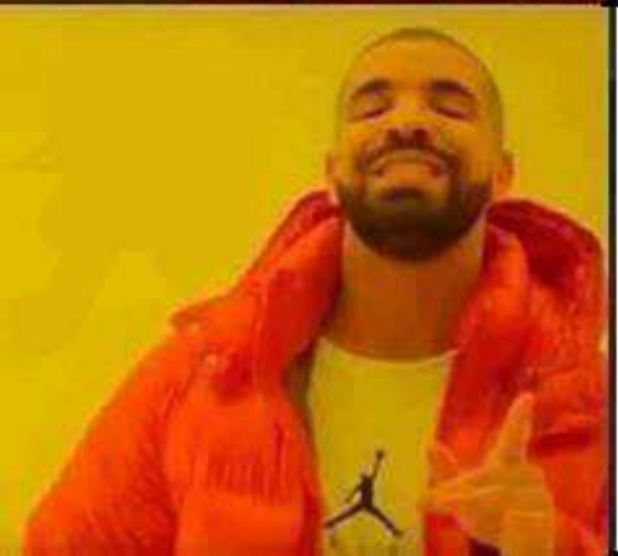

```

module mux_2x4(

    /* Multiplexer Data inputs */
    input A,
    input B,
    input C,
    input D,
    /* Multiplexer Select Input */
    input [1:0] sel,
    /* Outputs */
    output data_out,
    output isAddr3      // Set if address 3 is being selected

);

    assign data_out = ( A & ~sel[1] & ~sel[0] ) |
                     ( B & ~sel[1] & sel[0] ) |
                     ( C & sel[1] & ~sel[0] ) |
                     ( D & sel[1] & sel[0] );

    assign isAddr3 = sel[1] & sel[0];

endmodule

```



# Modeling Concepts



- ❑ In the scope of the course, we will see three types of circuit modeling approaches:
  - ❑ Dataflow modeling
  - ❑ Structural modeling
  - ❑ Behavioural modeling
- ❑ All three of them provide different abstractions for forming circuit descriptions, and are usually used together in bigger designs.

# Dataflow Modeling



- ❑ In dataflow modeling, connections between signals are expressed using Verilog operators,
- ❑ What we see so far was a glimpse of this approach.
  - ❑ We have seen bitwise operators. Using them we described the circuits from gate level expressions.

~	Bitwise negation
&	Bitwise and
	Bitwise or
^	Bitwise exclusive or

# More Operators - Conditional Assignment Operator

- ❑ Also known as ( ? : ) operator

```
assign <target_signal> = (<condition>) ? (<assigned_expression_if_true>) : (<assigned_expression_if_false>);
```

```
assign data_out = (sel==1) ? (I1 ^ I2) : (~I1 & I2);
```

- ❑ In terms of hardware, this corresponds to multiplexing

# More Operators - Relational & Logical

Symbol	Meaning	# of Operands
>	greater than	two
<	less than	two
>=	greater than or equal	two
<=	less than or equal	two
==	equality	two
!=	inequality	two
===	case equality	two
!==	case inequality	two
!	logical negation	one
&&	logical and	two
	logical or	two

Relational

Equality

Logical

- These are usually used within conditional statements
- Results may not always be boolean, but it will be single-bit

# More Operators - Examples

```
//suppose that: a = 3 and b = 0, then...
```

```
(a && b) //evaluates to zero
```

```
(b || a) //evaluates to one
```

```
(!a) //evaluates to 0
```

```
(!b) //evaluates to 1
```

```
//with unknowns: a = 2'b0x; b = 2'b10;
```

```
(a && b) // evaluates to x
```

```
//with expressions...
```

```
(a == 2) && (b == 3) //evaluates to 1 only if both comparisons are true
```

## More Operators - Examples

```
//let a = 4, b = 3, and...  
//x = 4'b1010, y = 4'b1101,  
//z = 4'b1xxz, m = 4'b1xxz, n = 4'b1xxx
```

```
a == b //evaluates to logical 0  
x != y //evaluates to logical 1  
x == z //evaluates to x  
z === m //evaluates to logical 1  
z === n //evaluates to logical 0  
m !== n //evaluates to logical 1
```

# More Operators - Arithmetic & Shift

Symbol	Meaning	# of Operands
*	multiply	two
/	divide	two
+	add	two
-	subtract	two
%	modulus	two
**	power (exponent)	two

>>	Right shift	Two
<<	Left shift	Two
>>>	Arithmetic right shift	Two
<<<	Arithmetic left shift	Two

Arithmetic

□ They might be synthesisable or not, depending on the tool

Shifts

# More Operators - Examples

```
//suppose that: a = 4'b0011;
//              b = 4'b0100;
//              d = 6; e = 4; f = 2;
//then,
a + b //add a and b; evaluates to 4'b0111
b - a //subtract a from b; evaluates to 4'b0001
a * b //multiply a and b; evaluates to 4'b1100
d / e //divide d by e, evaluates to 4'b0001. Truncates fractional part
e ** f //raises e to the power f, evaluates to 4'b1111
      //power operator is most likely not synthesizable
```



# More Operators - Concatenation & Replication

```
//let a = 1'b1, b = 2'b00, c = 2'b10, d = 3'b110  
y = {b, c} // y is then 4'b0010  
y = {a, b, c, d, 3'b001} // y is then 11'b10010110001  
y = {a, b[0], c[1]} // y is then 3'b101
```

## Concatenation

```
//let a = 1'b1, b = 2'b00, c = 2'b10, d = 3'b110  
y = { 4{a} } // y = 4'b1111  
y = { 4{a}, 2{b} } // y = 8'b111110000  
y = { 4{a}, 2{b}, c } // y = 8'b11111000010
```

## Replication

Operator Type	Operator Symbol	Operation Performed	Number of Operands
Arithmetic	*	multiply	two
	/	divide	two
	+	add	two
	-	subtract	two
	%	modulus	two
	**	power (exponent)	two
Logical	!	logical negation	one
	&&	logical and	two
		logical or	two
Relational	>	greater than	two
	<	less than	two
	>=	greater than or equal	two
	<=	less than or equal	two
Equality	==	equality	two
	!=	inequality	two
	===	case equality	two
	!==	case inequality	two

Bitwise	~	bitwise negation	one
	&	bitwise and	two
		bitwise or	two
	^	bitwise xor	two
	^^ or ~^	bitwise xnor	two
Reduction	&	reduction and	one
	~&	reduction nand	one
		reduction or	one
	~	reduction nor	one
	^	reduction xor	one
	^^ or ~^	reduction xnor	one
Shift	>>	Right shift	Two
	<<	Left shift	Two
	>>>	Arithmetic right shift	Two
	<<<	Arithmetic left shift	Two
Concatenation	{ }	Concatenation	Any number
Replication	{ { } }	Replication	Any number
Conditional	?:	Conditional	Three

# Verilog Basics - reg keyword

- ❑ "reg" keyword correspond to a variable that can hold values between assignments
- ❑ Because of this property, edge sensitive or level sensitive storage elements can be modelled by regs
- ❑ regs are declared inside a module body, but outside of a procedural block
- ❑ Does not necessarily need to represent memory elements. **Combinational logic can also be modelled with regs**

Currently, we are interested in this...

Regs are more commonly used in modelling of storage elements and sequential circuits. These will be covered in upcoming lectures...

# Verilog Basics – Procedural Blocks

- ❑ Assignments to regs can only be done within procedural blocks
- ❑ Procedural blocks can be used within a module body
- ❑ First two types of procedural blocks are "initial" and "always" blocks
- ❑ Procedural block encapsulation can be specified with "begin" and "end" keywords, in a similar manner with C's curly braces { } .
- ❑ If "begin" and "end" is not used, only the first upcoming statement is within that procedural block's scope.

```
module AND( output reg Q, input A ,  
input B );  
  
initial  
begin  
.  
<initialization>  
.  
end  
  
always @( ..sensitivity_list.. )  
begin  
.  
<functionality>  
.  
end  
endmodule
```

# Verilog Basics – Procedural Blocks

- ❑ Initial block:
  - ❑ Non-synthesisable procedural blocks
  - ❑ In hardware modelling, it can be used to give initial values to regs, for simulation purposes only.
  - ❑ Initial blocks are executed just once, starting at time 0.
  - ❑ Mainly used in testbenches

```
module test(  
    // ...  
);  
  
    reg r1,r2,r3;  
    reg r4 = 1; //Alternative way  
  
    initial  
    begin  
        r1 = 0;  
        r2 = 1;  
        r3 = 0;  
    end  
  
    // ..... //  
  
endmodule
```

# Verilog Basics – Procedural Blocks

- ❑ Always block:
  - ❑ Similar to initial, but the statements inside it are continuously evaluated, in looping fashion, unless a sensitivity list is used
  - ❑ @( ) statement represent a sensitivity list for an always block
  - ❑ The block is triggered once a change occurs in at least one of the expressions specified in sensitivity list
  - ❑ Assignments done within procedural blocks with "=" operator are evaluated sequentially (blocking assignment)

```
module test(  
    // ...  
);  
  
    reg r1,r2,r3;  
  
    initial  
    begin  
        r1 = 0;  
        r2 = 1;  
        r3 = 0;  
    end  
  
    always @(r1,r2)  
    begin  
        r3 = ~r1 & r2;  
    end  
  
endmodule
```



# Verilog Basics – Procedural Blocks



- ❑ What about this case?
- ❑ When modelling combinational logic, sensitivity list must be properly filled. Otherwise, **latches** will occur.
- ❑ @(\*) operator is later introduced to cope with this potential oversight. When modelling combinational logic, it auto-detects which signals could trigger the block.

**Important:** If there are multiple procedural blocks inside a module, they will be evaluated concurrently.

```
module test(  
    // ...  
);  
  
    reg r1,r2,r3;  
  
    initial  
    begin  
        r1 = 0;  
        r2 = 1;  
        r3 = 0;  
    end  
  
    always @(*)  
    begin  
        r3 = ~r1 & r2;  
    end  
  
endmodule
```




  
# Combinational circuits with procedural blocks



□ Returning back to our mystery box...

```
module mystery_box(  
    input I1,  
    input I2,  
    output reg O1  
);  
  
    initial I1=0;  
    initial I2=0;  
  
    always @(I1,I2)  
        O1 = I1 & I2;  
  
    // Functionally same as before!  
  
endmodule
```




□ We modeled the same circuit, but in a different way


 
# Verilog Basics - Procedural Blocks



□ How would you express the circuit below using procedural assignments only?



```
module example(  
    input X,Y  
    output reg Z  
);  
  
    reg [3:0] W;  
  
    always@(*)  
    begin  
        W[0] = X;    // Not necessary  
        W[1] = ~(X|Y);  
        W[2] = W[0] & W[1];  
        W[3] = W[1] & Y;  
        Z = Y ^ W[2] ^ W[3];  
    end  
endmodule
```

# Behavioural Modeling



- ❑ Why bother modelling combinational circuits like this?
  - ❑ What we've seen so far was dataflow modeling...
  - ❑ Using procedural blocks allows the usage of procedural statements (or behavioral statements), this approach is called behavioural modelling.

These are;



- If-else-else if blocks
- Case statement
- Loops (not all are synthesizable)  
(more on these in upcoming lectures...)
  
# Combinational circuits with procedural blocks



□ A small example for behavioural modelling...

```
module mystery_box(  
    input I1,  
    input I2,  
    output reg O1  
);  
  
    initial I1=0;  
    initial I2=0;  
  
    always @(*)  
    begin  
        if(I1==1 && I2==1)  
            O1 = 1;  
        else  
            O1 = 0;  
        end  
  
        // Functionally same as before!  
    endmodule
```




□ Again, we modeled the same circuit in a different way
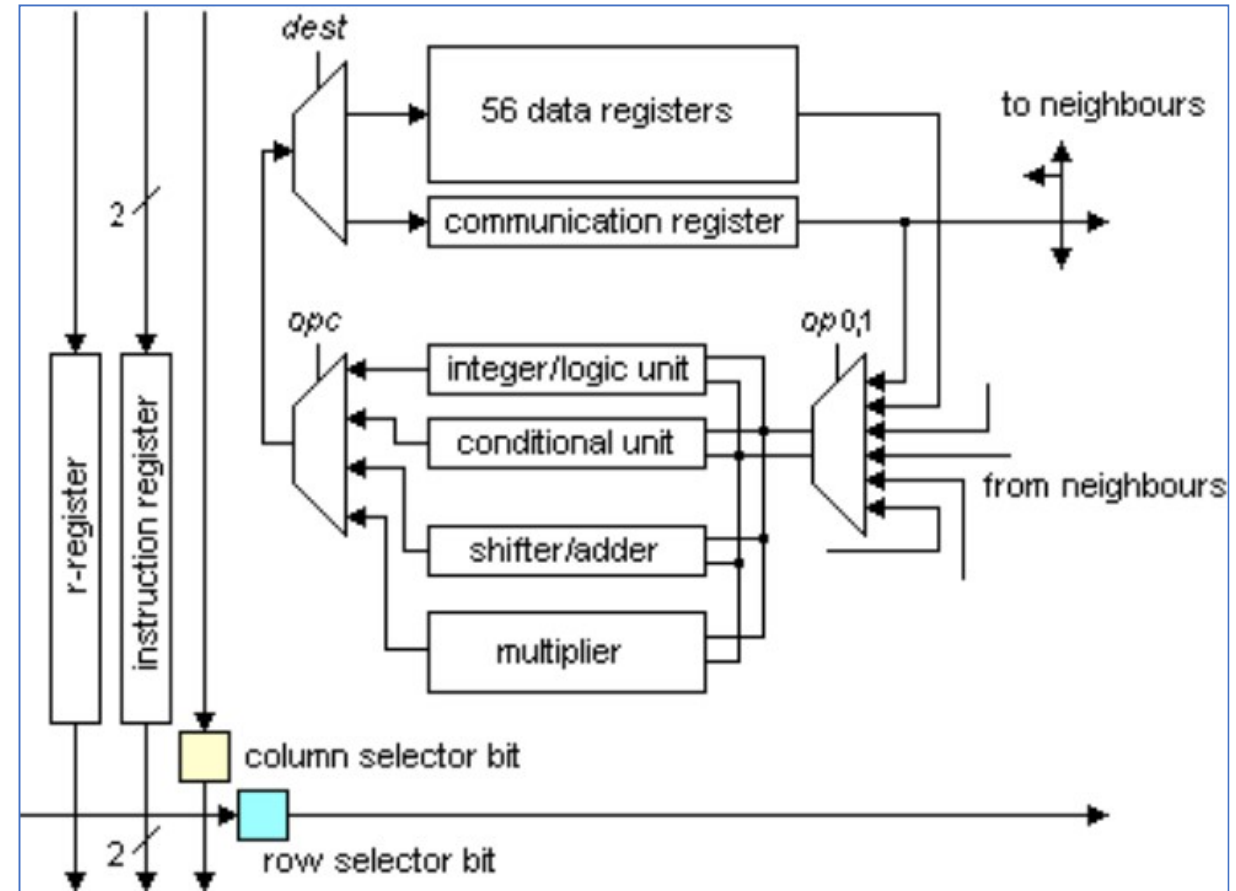
# Structural Modeling



- ❑ Modules are instantiated as submodules inside a top level design...
- ❑ Design Hierarchy
- ❑ Divide & Conquer
- ❑ Describe different blocks as separate modules
- ❑ More readable, modular, neat looking designs
- ❑ Easier to debug/track errors



# Structural Modeling - Instantiation



- ❑ Instantiation means creating an instance of a module within another module
- ❑ A module can be formed from various lower-level modules connected together
- ❑ Created submodules are called instances


```
module <upper_module_name> (<module_terminals>)  
.  
.  
<module_name> <instance_name> (<terminals>)  
.  
.  
<module_internals>  
.  
.  
endmodule
```

Instantiation

- The order of the statements (including instantiations) are not important.
- Remember that the code is not executed in sequence!
 
# Structural Modeling - Instantiation

- ❑ Instantiation means creating an instance of a module within another module
- ❑ A module can be formed from various lower-level modules connected together




```

module FA( input a, b, c_in,
           output c_out, sum );


    assign sum = a ^ b ^ c_in;
    assign c_out = ( c_in & ( a ^ b ) ) | ( a & b );

endmodule;
    
```

# Structural Modeling - Instantiation

 

Top Module

 

Lower Module

```
module adder( input [3:0] A, B,
              output cout,
              output [3:0] S );
```

Vectors (data type)

```
wire c0 = 0;
wire c1, c2, c3;
```

```
FA fa0( A[0], B[0], c0, c1, S[0] );
FA fa1( A[1], B[1], c1, c2, S[1] );
FA fa2( A[2], B[2], c2, c3, S[2] );
FA fa3( A[3], B[3], c3, cout, S[3] );
```

Instantiations

```
endmodule
```

```
module FA( input a, b, c_in,
           output c_out, sum );

assign sum = a ^ b ^ c_in;
assign c_out = ( c_in & ( a ^ b ) ) | ( a & b );

endmodule;
```

- Full adder is another module and must be defined in the **same project**.



# Structural Modeling - Instantiation

```
module adder( input [3:0] A, B,
              output cout,
              output [3:0] S );
wire c0 = 0;
wire c1, c2, c3;

FA fa0( A[0], B[0], c0, c1, S[0] );
FA fa1( A[1], B[1], c1, c2, S[1] );
FA fa2( A[2], B[2], c2, c3, S[2] );
FA fa3( A[3], B[3], c3, cout, S[3] );

endmodule
```

Instantiation by ordered list

Same

```
FA fa0
(
    .a(A[0]),
    .b(B[0]),
    .c_in(c0),
    .c_out(c1),
    .sum(S[0])
);
```

Instantiation by mapping

- ❑ Verilog has two ways of instantiating a module
- ❑ In ordered list style, as the name implies, port order matters. In mapping style, it does not.



# Structural Modeling - Instantiation

□ If we use mapping style instantiation, the same adder code would look like this:

```
module adder( input [3:0] A, B,
              output cout,
              output [3:0] S );

  wire c0 = 0;
  wire c1, c2, c3;

  FA fa0( .c_out(c1), .sum(S[0]), .a(A[0]), .b(B[0]), .c_in(c0) );
  FA fa1( .c_out(c2), .sum(S[1]), .a(A[1]), .b(B[1]), .c_in(c1) );
  FA fa2( .c_out(c3), .sum(S[2]), .a(A[2]), .b(B[2]), .c_in(c2) );
  FA fa3( .c_out(cout), .sum(S[3]), .a(A[3]), .b(B[3]), .c_in(c3) );

endmodule
```

# Structural Modeling - Primitives

- ❑ Another concept of structural modeling is the language-defined primitives
- ❑ Verilog provides logic gates as primitives



and



nand



or



nor



xor



xnor

# Structural Modeling - Primitives

```
wire OUT, IN1, IN2;

// basic gate instantiations.
and a1(OUT, IN1, IN2);
nand na1(OUT, IN1, IN2);

or or1(OUT, IN1, IN2);
nor nor1(OUT, IN1, IN2);

xor x1(OUT, IN1, IN2);
xnor nx1(OUT, IN1, IN2);

// More than two inputs: 3 input nand gate
nand na1_3inp(OUT, IN1, IN2, IN3);

// gate instantiation without instance name
and (OUT, IN1, IN2);
```

- ❑ Instance name is optional for primitives
- ❑ More than two inputs can be specified for these gates

# Structural Modeling - Primitives

- ❑ Vendor specific or technology specific primitives may also be available
- ❑ For example, Xilinx library contains LUT primitives that can be instantiated directly

```
LUT2
#( .INIT (4'h9))
O1
= (
    .IO(I1),
    .I1(I2),
    .O(O)
);
```

## A Xilinx 2-input LUT primitive instantiation

- ❑ The part shown with #( ) is called module parameter list  
(more on that later)

# Structural Modeling - Primitives



□ Summary for designing **purely combinational circuits** with Verilog

Our arsenal:

## □ Dataflow modeling:

- ❖ Continuous assignment
- ❖ Operators
- ❖ Procedural blocks (initial,always) with blocking assignments

## □ Structural modeling:

- ❖ Module instances (submodules)
- ❖ Primitives

## □ Behavioral modeling:

- ❖ Procedural blocks (initial,always) with blocking assignments
- ❖ Procedural statements (if,else,case...)

# Misc. Data Types



## String:

- A string is a sequence of characters that are enclosed by double quotes.

```
"Hello Verilog World"    // is a string
```

```
"a / b"                  // is a string
```

## Integer:

- An integer is a 32-bits signed number. Registers store values as unsigned quantities, whereas integers store values as **signed** quantities.

```
integer counter; // general purpose variable used as a counter.  
initial  
    counter = -1; // A negative one is stored in the counter
```

# Misc. Data Types



## Real:

- They can be specified in decimal notation (e.g., 3.14) or in scientific notation (e.g., 3e6, which is  $3 \times 10^6$ ).
- When a real value is assigned to an integer, the real number is rounded off to the nearest integer.

```
// real
real delta; // Define a real variable called delta
initial
begin
    delta = 4e10; // delta is assigned in scientific
                  // notation
    delta = 2.13; // delta is assigned a value 2.13
end

integer i; // Define an integer i
initial
    i = delta; // i gets the value 2 (rounded value
of 2.13)
end
```

# Misc. Data Types



## Arrays and Vectors:

- **Wires** or **reg** data types can be declared as vectors (multiple bit widths).
- If bit width is not specified, the default is a scalar (1-bit).

```
// DECLARATION:
wire a;                                // scalar net variable, default
wire [7:0] bus;                        // 8-bit bus
wire [31:0] busA,busB,busC;           // 3 buses of 32-bit width.

reg clock;                            // scalar register, default
reg [0:40] virtual_addr;              // vector register, 41 bits wide

// ACCESSING:
busA[7]                                // bit # 7 of vector busA
bus[2:0]                               // Three least significant bits of vector bus,
virtual_addr[0:1]                     // Two most significant bits of vector virtual_addr
```



# Misc. Data Types



- Multi-dimensional **arrays** can also be declared with any number of dimensions.
- Do NOT confuse arrays with vectors!
- A vector is a single element that is n-bits wide. On the other hand, arrays are multiple elements that are 1-bit or n-bits wide.
- Ports can not be declared as arrays.

`<data_type> <[vector]> <name> <[array]> <[array]> <[array]> ...`

└──────────┘

wire, register,  
integer etc.

└──────────┘

vectoral size,  
scalar default

└──────────────────────────┘

array size of the dimensions

# Misc. Data Types



```
// DECLARATION:
integer count[0:7];           // An array of 8 count variables
reg bool[31:0];               // Array of 32 one-bit boolean register variables

reg [4:0] port_id[0:7];       // Array of 8 port_ids; each port_id is 5 bits wide
wire [7:0] w_array2 [5:0];    // Declare an array of 8 bit vector wire

integer matrix[4:0][0:255];    // Two dimensional array of integers
wire w_array1[7:0][5:0];      // Declare an array of single bit wires

reg [63:0] array_4d [15:0][7:0][7:0][255:0]; //Four dimensional array
```




```
// ACCESSING:
count[5] = 0;                 // Reset 5th element of array of count variables
chk_point[100] = 0;          // Reset 100th time check point value
port_id[3] = 0;              // Reset 3rd element (a 5-bit value) of port_id array.
matrix[1][0] = 33559;        // Set value of element indexed by [1][0] to

array_4d[0][0][0][0][15:0] = 0; // Clear bits 15:0 of the register
                                // Accessed by indices [0][0][0][0]
port_id = 0;                  // Illegal syntax - Attempt to write the entire array
matrix [1] = 0;               // Illegal syntax - Attempt to write [1][0]..[1][255]
```
   
# References



- *Verilog HDL: A Guide to Digital Design and Synthesis, Second Edition, Samir Palnitkar*
- *FPGA Prototyping by Verilog Examples: Xilinx Spartan-3 Version, Pong P. Chu*
- *Digital Design and Verilog HDL Fundamentals, Joseph Cavanagh*



Thank You!