



ISTANBUL TECHNICAL UNIVERSITY

Digital System Design & Applications

Verilog - Procedural Statements 1

RES. ASST. FIRAT KULA

So far...



- Summary for designing **purely combinational circuits** with Verilog

Our arsenal:

- Dataflow modeling:

- ❖ Continuous assignment
- ❖ Operators
- ❖ Procedural blocks (initial,always) with blocking assignments

- Structural modeling:



- ❖ Module instances (submodules)
- ❖ Primitives

- Behavioral modeling:

- ❖ Procedural blocks (initial,always) with blocking assignments
- ❖ Procedural statements (if,else,case...)

So far...

 
 
```
module mystery_box(  
    input I1,  
    input I2,  
    output reg O1  
);  
  
    initial I1=0;  
    initial I2=0;  
  
    always @(I1,I2)  
        O1 = I1 & I2;  
  
    // Functionally same as before!  
endmodule
```



mystery_box

So far...
  
```
module mystery_box(  
    input I1,  
    input I2,  
    output reg O1  
);  
  
    initial I1=0;  
    initial I2=0;  
  
    always @(*)  
    begin  
        if(I1==1 && I2==1)  
            O1 = 1;  
        else  
            O1 = 0;  
        end  
  
        // Functionally same as before!  
    endmodule
```



□ We modeled the same circuit, but in a different way

Behavioral Modeling



- ❑ Why bother modeling combinational circuits like this?
 - ❑ Using procedural blocks allows the usage of procedural statements (or behavioral statements), this approach is called behavioural modeling.
 - ❑ Procedural statements allow the designers to express a circuit in a **higher-level language/abstraction**

These statements are;

- If-else-else if blocks
- Case statement
- Loops (not all are synthesizable)

This week

Behavioral Modeling - if/else blocks



```
if( /*conditional_expression*/ )
begin
    /*statements*/
end

else if(/*conditional_expression*/)
begin
    /*statements*/
end

// ...

else
begin
    /*statements*/
end
```

- ❑ Used to make a decision whether the statements within the block should be executed or not
- ❑ if conditional expression is true, evaluate all statements within particular block
- ❑ If false ('0','x','z'), particular block won't be evaluated
- ❑ If there is an 'optional' **else** statement, it will be evaluated in case of conditional expression being false

Can only be used within a procedural block ('always' or 'initial')

For non-procedural coding styles, we use ? : operator

□ Example 1: If-else block

```
always @ (*)  
begin
```

```
    if(IN & ENABLE)
```

```
    begin
```

```
        OUT = 2'b01;
```

```
    end
```


```
    else
```

```
        OUT = 'b10;    // If only one statement is written, |  
                        // begin-end encapsulation might be discarded
```

```
end
```

```
assign OUT = (ENABLE & IN) ? 2'b01 : 2'b10;  
                //      condition  if_true  if_false
```

Non-procedural equivalent

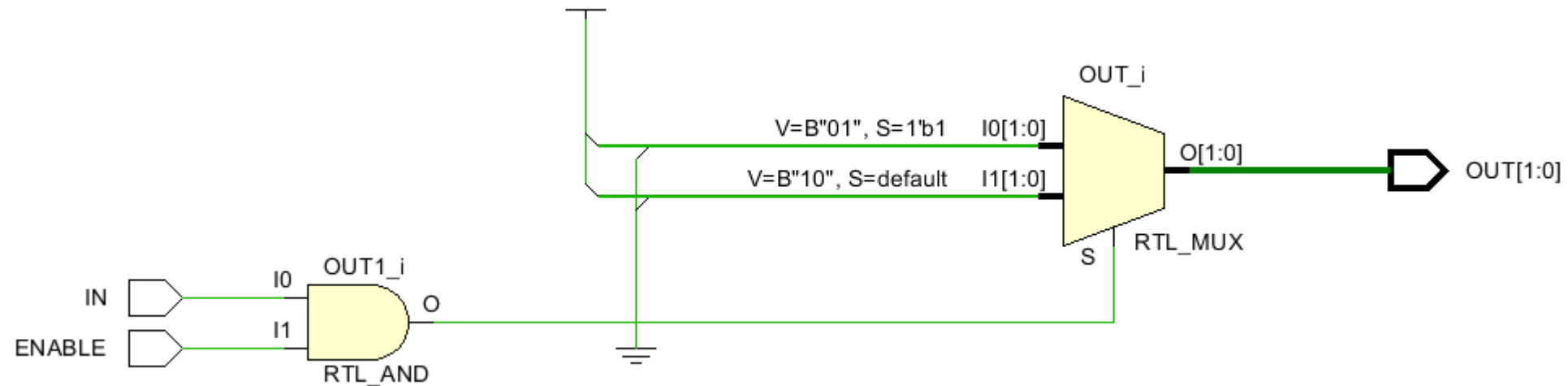

An if-else pair corresponds to a MUX structure

Behavioral Modeling - if/else blocks



□ Example 2

I3	I2	I1	I0	F	
0	0	0	0	0	I1 and I0
0	0	0	1	0	
0	0	1	0	0	
0	0	1	1	1	
0	1	0	0	0	I1 or I0
0	1	0	1	1	
0	1	1	0	1	
0	1	1	1	1	
1	0	0	0	0	I1 xor I0
1	0	0	1	1	
1	0	1	0	1	
1	0	1	1	0	
1	1	x	x	1	

□ Let inputs I3 and I2 be used as conditions:

- When they are both zero, we see that the function works as **I0 and I1**
- When I3=0 and I2=1, we see that the function works as **I0 or I1**
- When I3=1 and I2=0, we see that the function works as **I0 xor I1**
- Otherwise, F = 1.

Behavioral Modeling - Chained if/else if blocks



□ Example 2: If/else-if chain


```
module function_F(I,F);  
    input [3:0] I;  
    output reg F;  
  
    always @ (I)  
    begin  
        if( {I[3],I[2]} == 2'd0 )  
            F = I[1] & I[0];  
        else if( {I[3],I[2]} == 2'd1 )  
            F = I[1] | I[0];  
        else if( I[3]==1 && I[2]==1'b0 ) // Alternative!  
            F = I[1] ^ I[0];  
        else  
            F = 1'b1;  
    end  
endmodule
```

Equivalent Behavioral Code

□ Example 2: If/else-if chain

```
module function_F(I,F);  
    input [3:0] I;  
    output reg F;  
  
    always @ (I)  
    begin  
        if( {I[3],I[2]} == 2'd0 )  
            F = I[1] & I[0];  
        else if( {I[3],I[2]} == 2'd1 )  
            F = I[1] | I[0];  
        else if( I[3]==1 && I[2]==1'b0 ) // Alternative!  
            F = I[1] ^ I[0];  
        else  
            F = 1'b1;  
    end  
endmodule
```

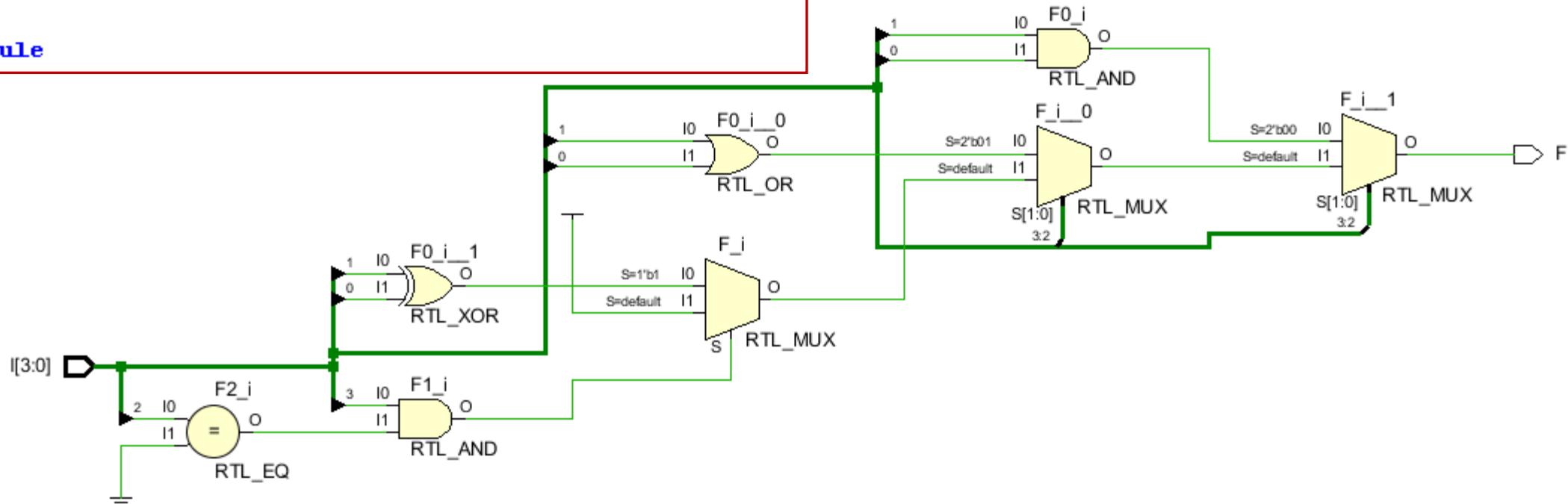if/else-if chains correspond to
priority mux structure



```

`timescale 1ns / 1ps
module conditional_test;
wire O;
reg [3:0] I;

initial
    $monitor($time, "I=%b: O=%b",I,O);

```

```

conditional_if c1(.I(I),.F(O));

```

```

initial
begin

```

```

    I=4'b0000; #20;
    I=4'b0001; #20;
    I=4'b0010; #20;
    I=4'b0011; #20;
    I=4'b0100; #20;
    I=4'b0101; #20;
    I=4'b0110; #20;
    I=4'b0111; #20;
    I=4'b1000; #20;
    I=4'b1001; #20;
    I=4'b1010; #20;
    I=4'b1011; #20;
    I=4'b1100; #20;
    I=4'b1101; #20;
    I=4'b1110; #20;
    I=4'b1111; #20;

```

```

end

```

```

endmodule

```

```

# run 1000ns

```

```

    0I=0000: O=0
    20I=0001: O=0
    40I=0010: O=0
    60I=0011: O=1
    80I=0100: O=0
    100I=0101: O=1
    120I=0110: O=1
    140I=0111: O=1
    160I=1000: O=0
    180I=1001: O=1
    200I=1010: O=1
    220I=1011: O=0
    240I=1100: O=1
    260I=1101: O=1
    280I=1110: O=1
    300I=1111: O=1

```

I3	I2	I1	I0	F	
0	0	0	0	0	I1 and I0
0	0	0	1	0	
0	0	1	0	0	
0	0	1	1	1	
0	1	0	0	0	I1 or I0
0	1	0	1	1	
0	1	1	0	1	
0	1	1	1	1	
1	0	0	0	0	I1 exor I0
1	0	0	1	1	
1	0	1	0	1	
1	0	1	1	0	
1	1	x	x	1	


□ Example 3: Nested if/else

```
module example1
(
    input [1:0] SEL,
    input [1:0] IN,
    input ENABLE,
    output reg [1:0] OUT
);

    always @ (*)
    begin
        if(SEL==2'b11)
        begin
            if(ENABLE) OUT = IN[0] + IN[1]; //Nested if-else
            else OUT = 0;
        end
        else if(SEL==2'b01)
        begin
            OUT[0]= IN[1] & IN[0];
            OUT[1]= IN[1] ^ IN[0];
        end
        else
            OUT = 0;
    end
endmodule
```

Behavioral Modeling - Nested if/else blocks

□ Example 3: Nested if/else

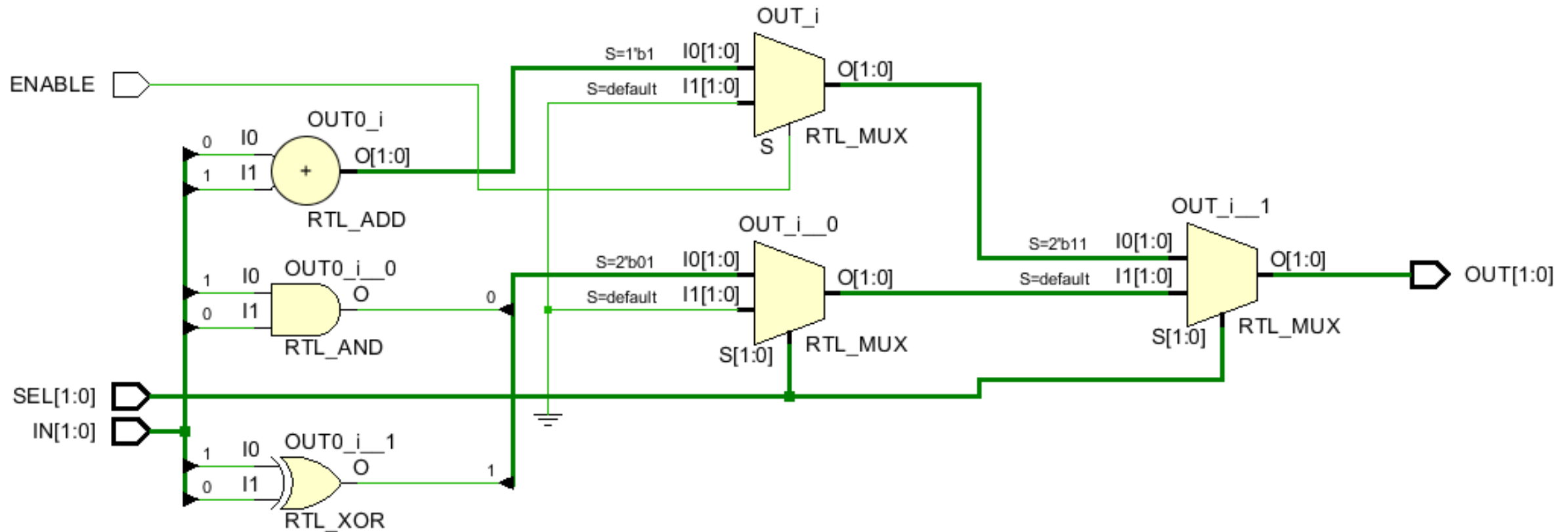

Resulting RTL

□ Example 4: If without else

□ While coding combinational logic, **if statements without elses** will produce **latches**. This should be avoided.

□ Latches are mostly unintentional and caused by incomplete conditional assignments (forgetting to define outputs for certain possible input cases)

□ Latches cause timing and routing complications in FPGAs. Design tools usually throw a warning if they detect an inferred latch.

□ Note that latches only appear while coding combinational logic with procedural statements.

```
module example2
(
    input [1:0] SEL,
    input [1:0] IN,
    input ENABLE,
    output reg [1:0] OUT
);

always @ (*)
begin
    if(ENABLE)
    begin
        if(SEL==2'b11)
        begin
            OUT = IN[0] + IN[1];
        end


        else if(SEL==2'b01)
        begin
            OUT[0]= IN[1] & IN[0];
            OUT[1]= IN[1] ^ IN[0];
        end

        else
            OUT = 0;
    end
end

endmodule
```

Behavioral Modeling - if without else

□ Example 4: If without else

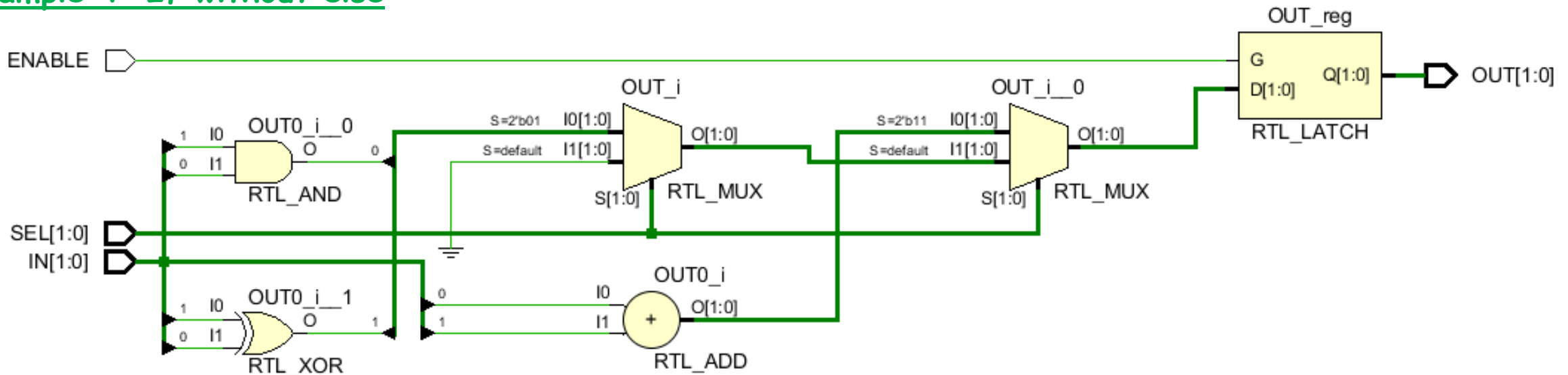

Resulting RTL schematic



Synthesis tool threw a warning!

Behavioral Modeling - Case statement



```
case(*ExpressionToBeChecked*)

    /*value1>*/:
    begin
        /*statements*/
    end

    /*value1>*/:
    begin
        /*statements*/
    end

    // ...

    default:
    begin
        /*statements*/
    end

endcase
```

- ❑ When input combinations are various and many in number, coding with **case blocks** will be easier than coding with if-else blocks.
- ❑ "default" statement is optional, and corresponds to the case where none of the listed items match the check expression value
- ❑ The value of the check expression and each case item will be compared one by one, in the exact order specified, until a match is found. If there is no match, default expression will be executed.
- ❑ Check expressions and case items can be computed at runtime. They do not need to be a constant.

Behavioral Modeling - Case statement




□ Example 5: Example 2 reworked with case statement

I3	I2	I1	I0	F	
0	0	0	0	0	I1 and I0
0	0	0	1	0	
0	0	1	0	0	
0	0	1	1	1	
0	1	0	0	0	I1 or I0
0	1	0	1	1	
0	1	1	0	1	
0	1	1	1	1	
1	0	0	0	0	I1 exor I0
1	0	0	1	1	
1	0	1	0	1	
1	0	1	1	0	
1	1	x	x	1	

```
module conditional_case(I,F);  
input [3:0] I;  
output reg F;  
  
always @(I)  
    case({I[3],I[2]})  
        2'd0:F=I[1]&I[0];  
        2'd1:F=I[1]|I[0];  
        2'd2:F=I[1]^I[0];  
        default:F=1'b1;  
    endcase  
endmodule
```

Behavioral Modeling - Case statement

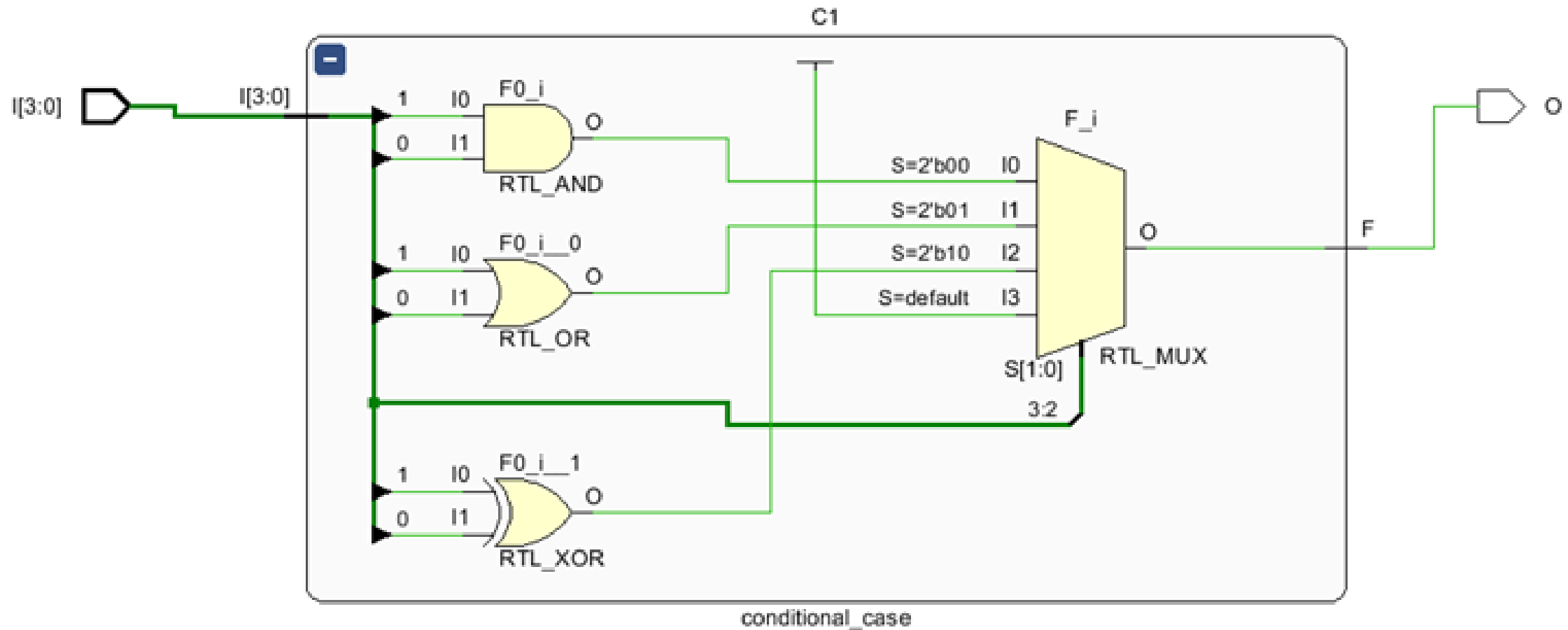□ Example 5: Example 2 reworked with case statement



Resulting RTL

Behavioral Modeling - Case statement



□ Example 6: Common cases


```
module conditional_case2(I,F);
input [3:0] I;
output reg F;

always @(I)
    case(I)
        4'b0000,4'b0001,4'b0010,4'b0011:F=I[1]&I[0];
        4'b0100,4'b0101,4'b0110,4'b0111:F=I[1]|I[0];
        4'b1000,4'b1001,4'b1010,4'b1011:F=I[1]^I[0];
        4'b1100,4'b1101,4'b1110,4'b1111:F=1'b1;
    endcase
endmodule
```

- Case items which correspond to the same expression can be combined using commas


Behavioral Modeling - Case statement

□ Example 6: Common cases

 

Resulting RTL

❑ Example 7: Incomplete case block

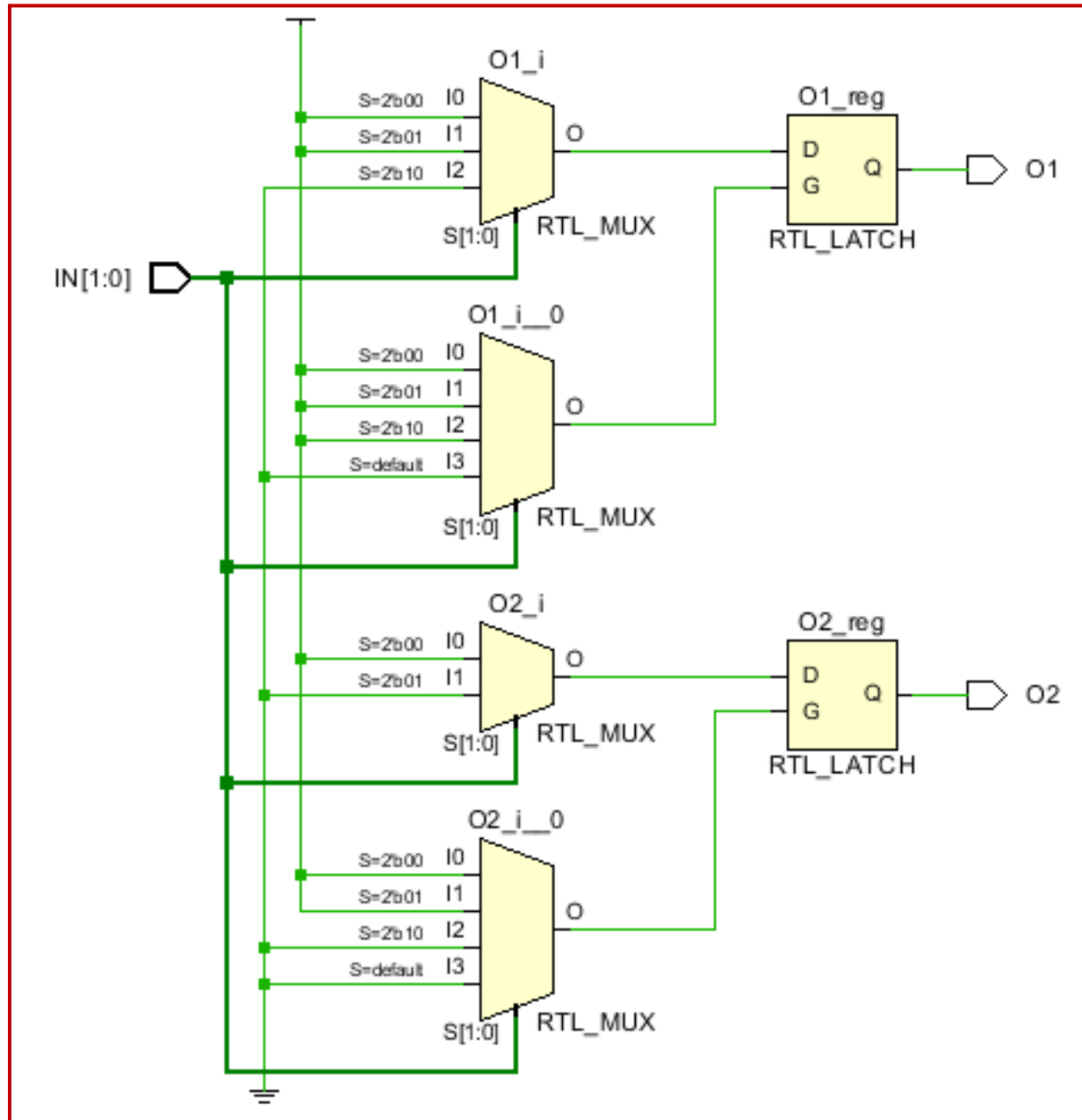

```

module example5
(
    input [1:0] IN,
    output reg O1,O2
);

    always @ (*)
    begin
        case( IN)
            0:
                begin
                    O1 = 1;
                    O2 = 1;
                end
            1:
                begin
                    O1 = 1; O2 = 0;
                end
            2:
                begin
                    O1 = 0;
                end


            // Missing case 3:
            // Missing default

        endcase
    end

endmodule

```

❑ Example 7: Incomplete case block

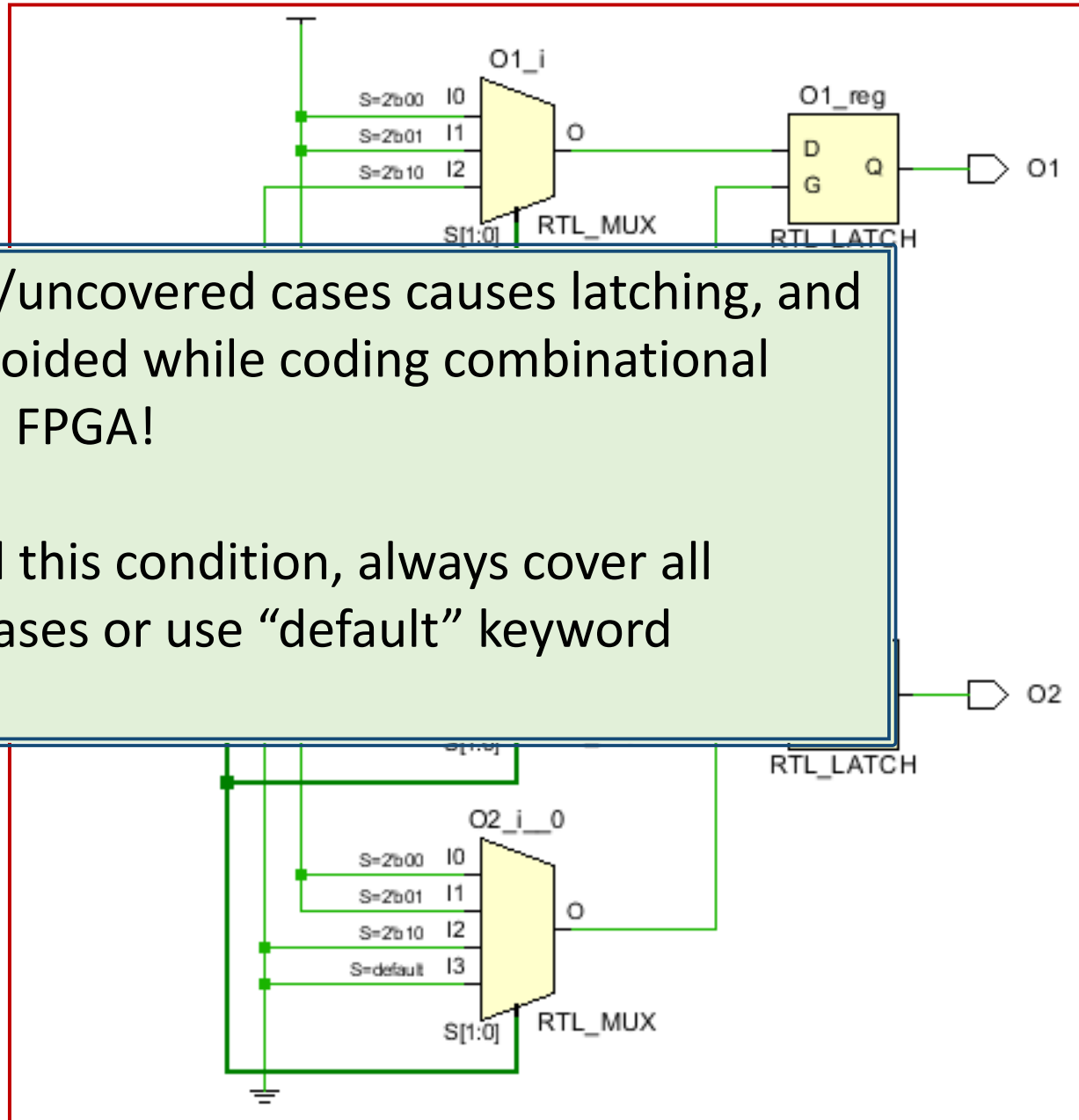

```
module example5
(
    input [1:0] IN,
    output reg O1,O2
);


always @ (*)
begin
    case(IN)
        0:
            begin
                O1 = 1;
                O2 = 1;
            end
        1:
            begin
                O1 = 1; O2 = 0;
            end
        2:
            begin
                O1 = 0;
            end

        // Missing case 3:
        // Missing default

    endcase
end

endmodule
```

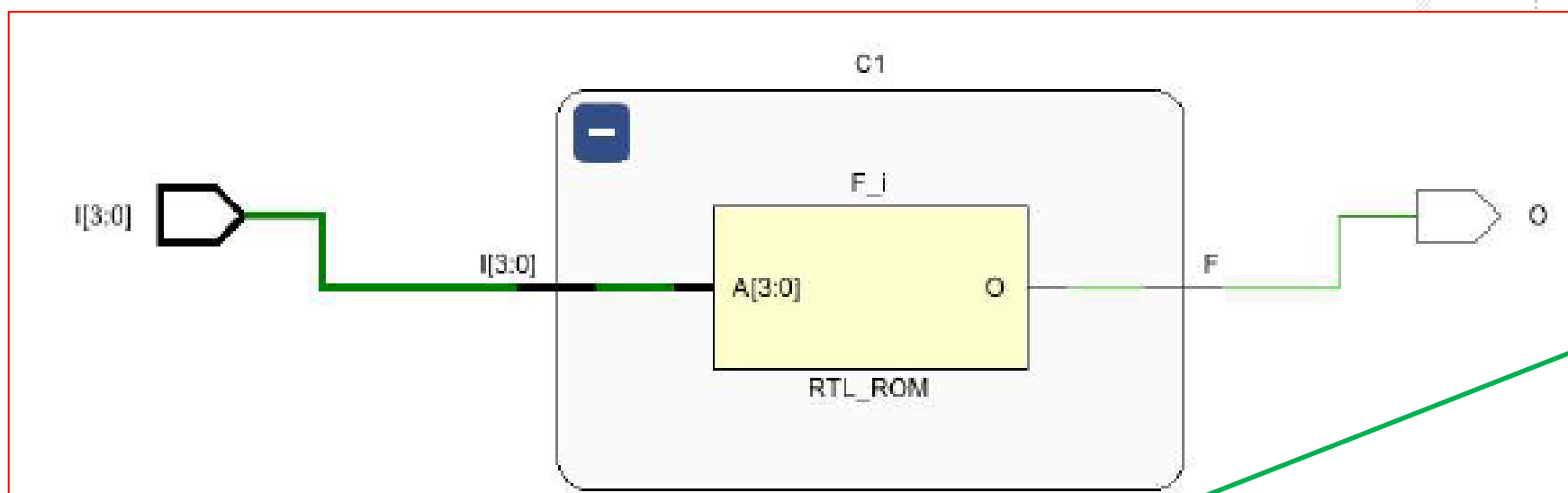□ Example 8: Fully pre-defined case statement



```
module conditional_case2(I,F);  
  input [3:0] I;  
  output reg F;  
  
  always @(I)  
  ]   case(I)  
    4'b0000: F=I[1]&I[0];  
    4'b0001: F=I[1]&I[0];  
    4'b0010: F=I[1]&I[0];  
    4'b0011: F=I[1]&I[0];  
    4'b0100: F=I[1]|I[0];  
    4'b0101: F=I[1]|I[0];  
    4'b0110: F=I[1]|I[0];  
    4'b0111: F=I[1]|I[0];  
    4'b1000: F=I[1]^I[0];  
    4'b1001: F=I[1]^I[0];  
    4'b1010: F=I[1]^I[0];  
    4'b1011: F=I[1]^I[0];  
    4'b1100: F=1'b1;  
    4'b1101: F=1'b1;  
    4'b1110: F=1'b1;  
    4'b1111: F=1'b1;  
  endcase  
endmodule
```

How come these expressions are inferred as constants??

Behavioral Modeling - "x" and "z" in case statements



```
case (select[1:2])
  2'b00: result = 0;
  2'b01: result = flaga;
  2'b0x,
  2'b0z: result = flaga ? 'bx : 0;
  2'b10: result = flagb;
  2'bx0,
  2'bz0: result = flagb ? 'bx : 0;
  default result = 'bx;
endcase
```

- ❑ Expression in case paranthesis and case item expressions are compared bit by bit; thus, case statement gives definitive results when "x" and "z" values are involved in either of these expressions

- ❑ For example, consider the values below for this code;

Select[1] == 0,
flaga == 0,

and when select[2] is "x" or "z", then **the result will be 0**, which is resolved at third case

Behavioral Modeling - "casex" and "casez"



- ❑ There are two special types of case statement to handle don't care situations: "casex" and "casez"
- ❑ "casez" treats the value "z" as "don't care"
- ❑ "casex" treats both "x" and "z" as "don't care"
- ❑ Using "?" character instead of "z" is also allowed for a more convenient don't care specification
- ❑ The syntax is the same as traditional case statement, except they begin with casex and casez keywords, respectively.

Behavioral Modeling - "casex" and "casez"



□ Example 9: casez example

```
module example6
(
    input [2:0] in,
    output reg out1,out2,out0
);
    always @(in)
    begin
        {out2,out1,out0} = 3'b000;
        casez (in)
            3'b1?? : out2 = 1'b1;
            3'b?1? : out1 = 1'b1;
            3'b??1 : out0 = 1'b1;
            default: {out2,out1,out0} = 3'b000;
        endcase
    end
endmodule
```

□ These are "wildcard" style of coding case statements, and prone to mistakes. Take extra care while using these

□ For example, if in[0] is left unconnected (value Z), then the first case branch will still be true

Behavioral Modeling - "casex" and "casez"



□ Example 10: casex example

```
module casex_example(  
    input [7:0] sig,  
    output reg [7:0] result  
);  
  
    reg [7:0] mask;  
  
    always@(*)  
    begin  
        mask = 8'b0x0x0x0x0;  
        casex (sig ^ mask)  
            8'b001100xx: result=0;  
            8'b1100xx00: result=1;  
            8'b00xx0011: result=2;  
            8'bxx010100: result=3;  
            default: result='bz;  
        endcase  
    end  
  
endmodule
```

□ Let's consider the case when "sig == 8'b0110_0110"

"sig ^ mask" expression would be

0110_0110

x0x0_x0x0

x1x0_x1x0

In that case, second case item will be a match, result will be 1

Behavioral Modeling - "casex" and "casez"

Example 11: Functions with don't care values using casex

```
module case_dontcare
(
    input [2:0] in,
    output reg out
);
always @(*)
begin
    casex (in)
        3'b000: out=1;
        3'b001: out=1'b $x$ ;
        3'b010: out=1;
        3'b011: out=1;
        3'b100: out=0;
        3'b101: out=0;
        3'b110: out=0;
        3'b111: out=1'b $x$ ;
    endcase
end
endmodule
```

In[2] In[1]In[0]	0	1
00	1	0
01	x	0
11	1	x
10	1	0


□ We expect this to be simplified as:

$$\text{out} = \sim \text{in}[2]$$

...according to Karnaugh Map simplification

Behavioral Modeling - "casex" and "casez"

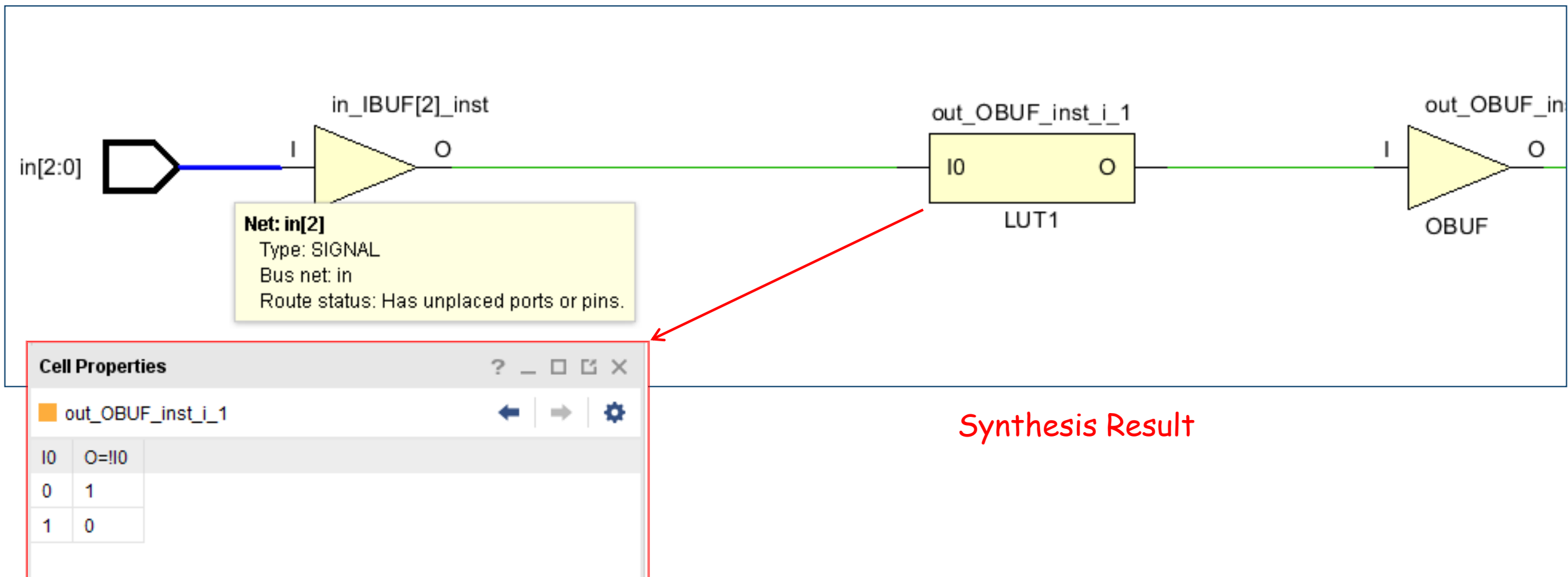Example 11: Functions with don't care values using casex



Synthesis Result

□ Example 12: Comparing case behaviours

```
module conditional_case3(I,F);
input I;
output reg [1:0] F;

always @(I)
    case(I)
        1'b0:F=
        1'b1:F=
        1'bx:F=
        1'bz:F=
    endcase
endmodule
```

```
module conditional_casex(I,F);
input I;
output reg [1:0] F;

always @(I)
    casex(I)
```

```
'b00;
'b01;
'b10;
'b11;
```

```
`timescale 1ns / 1ps
module conditional_test2;
wire [1:0] O;
reg I;

initial
    $monitor($time, "I=%b: O=%b",I,O);

conditional_casex c1(.I(I),.F(O));

initial
begin

    I=1'b0;    #20;
    I=1'b1;    #20;
    I=1'bx;    #20;
    I=1'bz;    #20;

end

endmodule
```

□ Example 12: Comparing case behaviours

What about
"casez" ?

```
module conditional_case3(I,F);
input I;
output reg [1:0] F;

always @(I)
    case(I)
        1'b0:F=2'b00;
        1'b1:F=2'b01;
        1'bx:F=2'b10;
        1'bz:F=2'b11;
    endcase
endmodule
```

```
I=1'b0;    #20;
I=1'b1;    #20;
I=1'bx;    #20;
I=1'bz;    #20;
```

Stimulus

```
# run 1000ns
```

```
0I=0: O=00
20I=1: O=01
40I=x: O=10
60I=z: O=11
```

"case" result

```
module conditional_casex(I,F);
input I;
output reg [1:0] F;


always @(I)
    casex(I)
        1'b0:F=2'b00;
        1'b1:F=2'b01;
        1'bx:F=2'b10;
        1'bz:F=2'b11;
    endcase
endmodule
```

```
# run 1000ns
```

```
0I=0: O=00
20I=1: O=01
40I=x: O=00
60I=z: O=00
```

"casex" result

References

 

□ IEEE Std 1364-2005

□ Brown & Vranesic - "Fundamentals of Digital Design with Verilog"

□ <https://www.chipverify.com/verilog/verilog-tutorial>

□ <http://www.asic-world.com/verilog/veritut.html>

Thank You!