

# **Chapter 4 – Arithmetic Functions and Some Building Blocks**

# Overview


- **Carry lookahead adders**
- **Binary subtraction**
- **Binary adder-subtractors**
  - Signed binary numbers
  - Signed binary addition and subtraction
  - Overflow
- **Binary multiplication**
- **Other arithmetic functions**
  - Design by contraction

# Functional Blocks: Addition

- **Addition Development:**
  - *Half-Adder* (HA), a 2-input bit-wise addition functional block,
  - *Full-Adder* (FA), a 3-input bit-wise addition functional block,
  - *Ripple Carry Adder*, an iterative array to perform binary addition, and
  - *Carry-Look-Ahead Adder* (CLA), a hierarchical structure to improve performance.
 
# Carry Propagation

- What is the total delay of 4-bit ripple carry adder?
  - $\tau_{FA}$ : delay of a one full adder
  - Serial connected 4 full adders are used.
  - Total delay:  $4\tau_{FA}$ .



4

$$4\tau_{FA} \approx 8\tau_{XOR}$$

input sayısı değişirse AND -ol gate  
delayi artar mı?

# Faster Adders

- The carry propagation technique is a limiting factor in the speed with which two numbers are added.
- Two alternatives
  - use faster gates with reduced delays
  - Increase the circuit complexity (i.e. put more gates) in such a way that the carry delay time is reduced.
- An example for the latter type of solution is **carry lookahead adders**
  - Two binary variables:
    1.  $P_i = a_i \oplus b_i$  – carry propagate
    2.  $G_i = a_i b_i$  – carry generate


# Carry Lookahead Adders

- **Sum and carry can be expressed in terms of  $P_i$  and  $G_i$ :**
  - $S_i = P_i \oplus C_i$
  - $C_{i+1} = G_i + P_i C_i$
- **Why the names (carry propagate and generate)?**
  - If  $G_i = 1$  (both  $a_i = b_i = 1$ ), then a “new” carry is generated
  - If  $P_i = 1$  (either  $a_i = 1$  or  $b_i = 1$ ), then a carry coming from the previous lower bit position is propagated to the next higher bit position

# 4-bit Carry Lookahead Adder

- We can use the carry propagate and carry generate signals to compute carry bits used in addition operation
  - $C_0 = \text{input}$
  - $C_1 = G_0 + P_0C_0$
  - $C_2 = G_1 + P_1C_1$   
$$= G_1 + P_1(G_0 + P_0C_0) = G_1 + P_1G_0 + P_1P_0C_0$$
  - $C_3 = G_2 + P_2C_2 = G_2 + P_2(G_1 + P_1G_0 + P_1P_0C_0)$   
$$= G_2 + P_2G_1 + P_2P_1G_0 + P_2P_1P_0C_0$$
  - $P_0 = a_0 \oplus b_0$  and  $G_0 = a_0b_0$
  - $P_1 = a_1 \oplus b_1$  and  $G_1 = a_1b_1$
  - $P_2 = a_2 \oplus b_2$  and  $G_2 = a_2b_2$
  - $P_3 = a_3 \oplus b_3$  and  $G_3 = a_3b_3$

# 4-bit Carry Lookahead Circuit 1/3

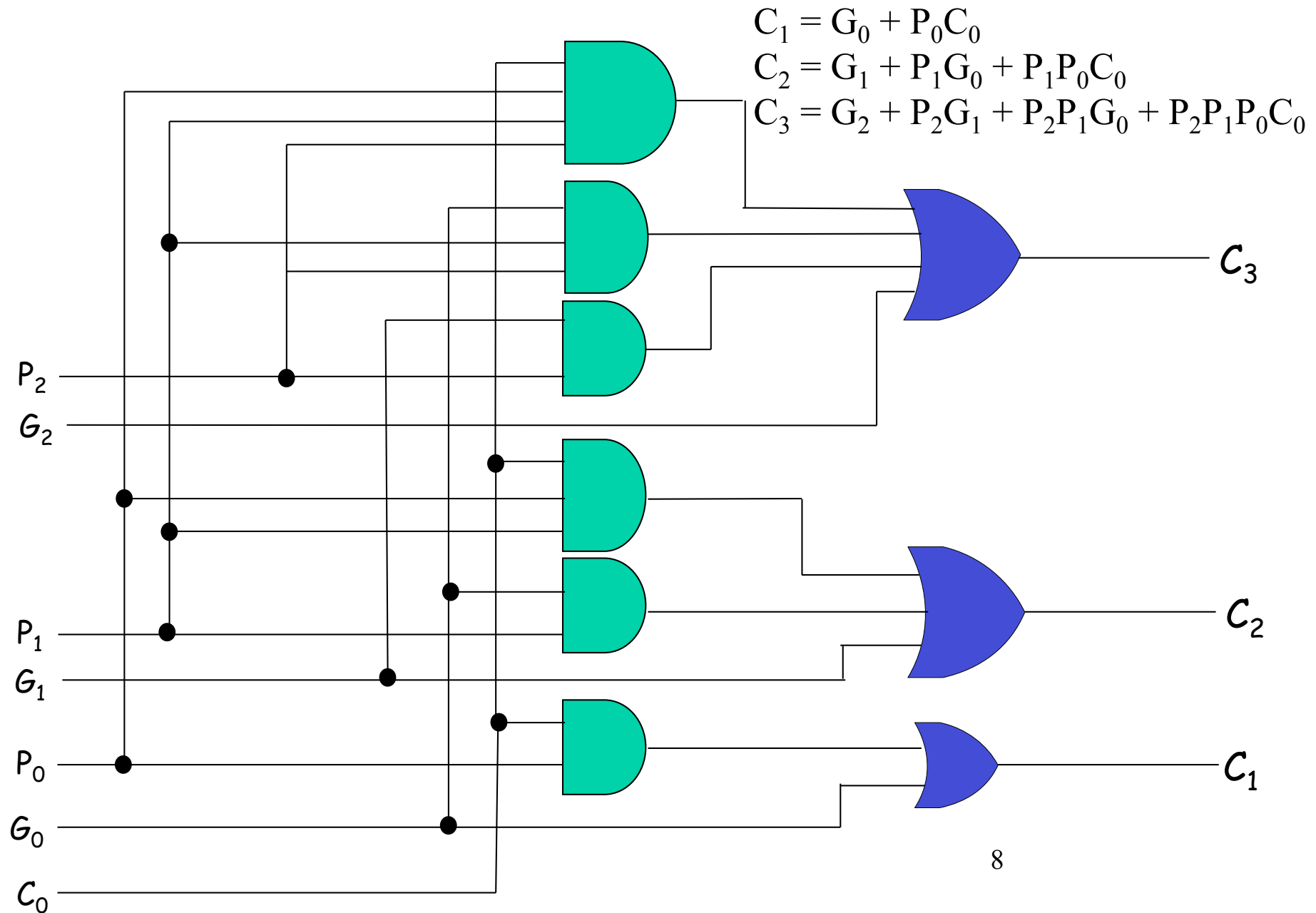




## 4-bit Carry Lookahead Circuit 2/3


- All three carries ( $C_1$ ,  $C_2$ ,  $C_3$ ) can be realized as two-level implementation (i.e. AND-OR)
- $C_3$  does not have to wait for  $C_2$  and  $C_1$  to propagate
- $C_3$  has its own circuit
- The propagations happen concurrently

# 4-bit Carry Lookahead Circuit 3/3

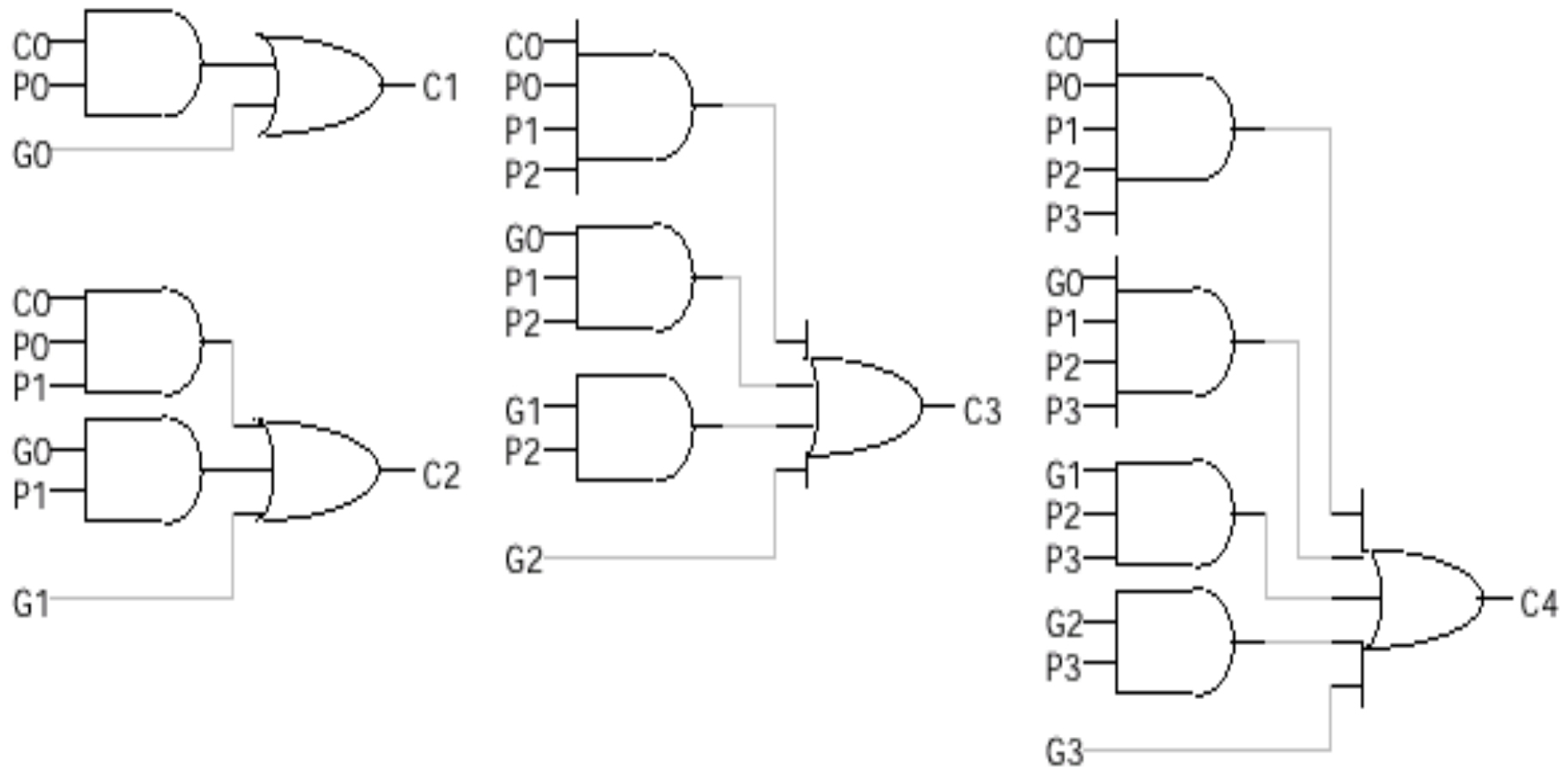


- Two levels of logic

# 4-bit Carry Lookahead Adder

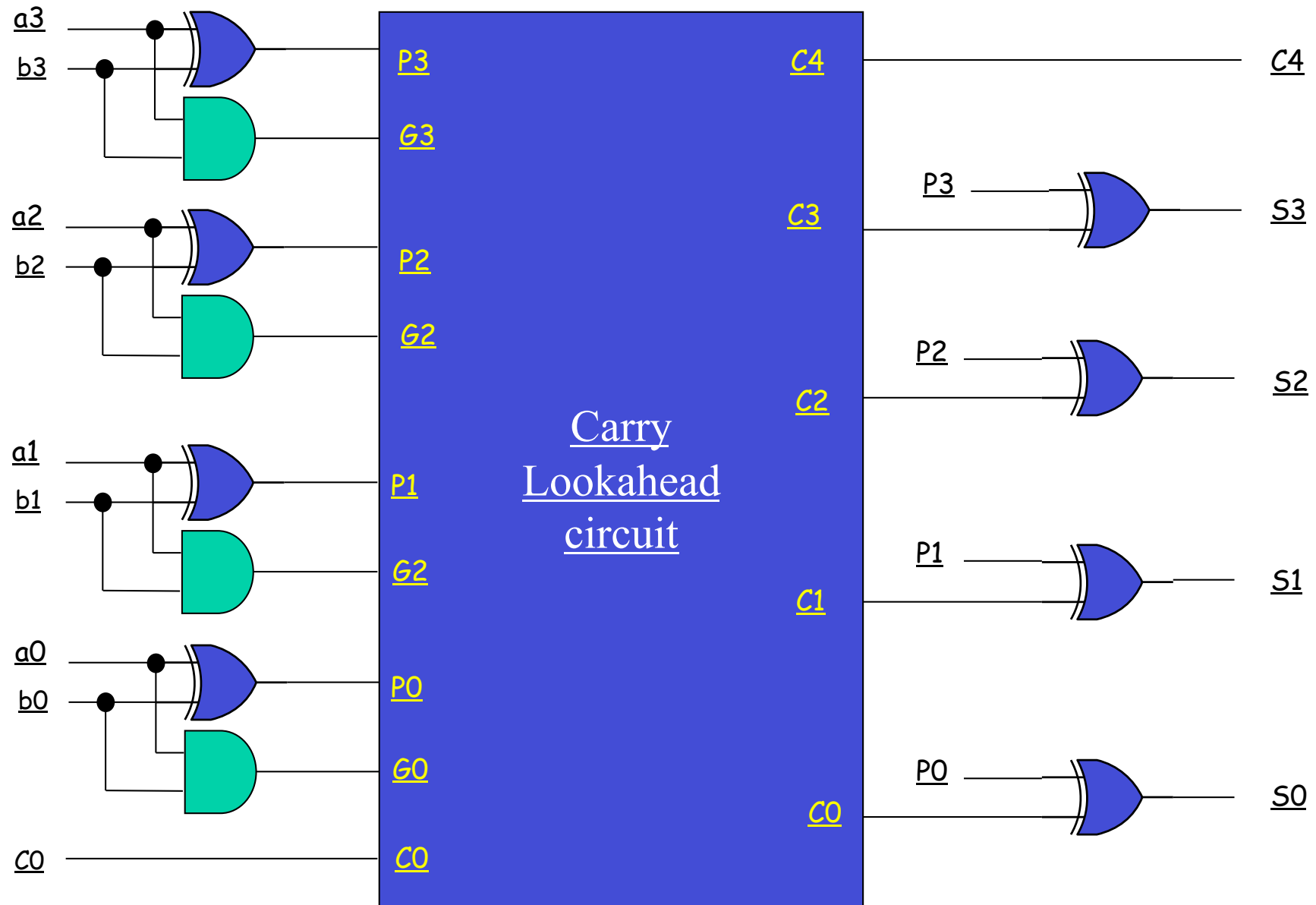


# Hybrid Approach for 16-bit Adder

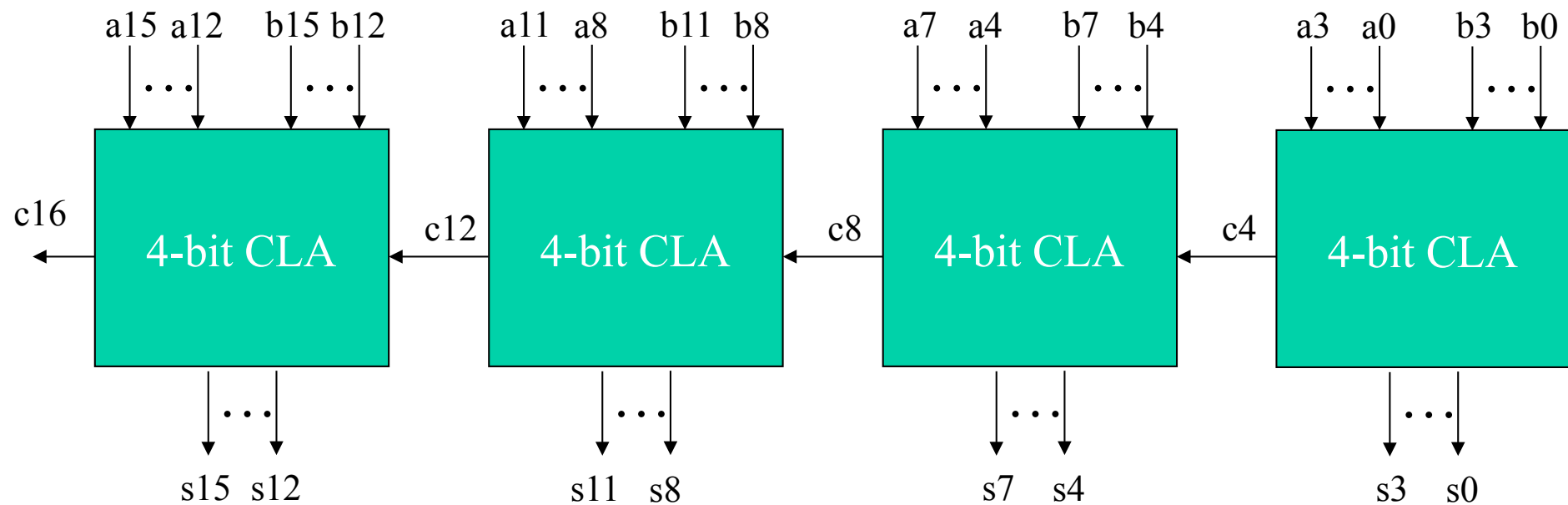
 
# Subtractor


- Recall how we do subtraction (2's complement)
  - $X - Y = X + (2^n - Y) = X + \sim Y + 1$



# Binary Multipliers
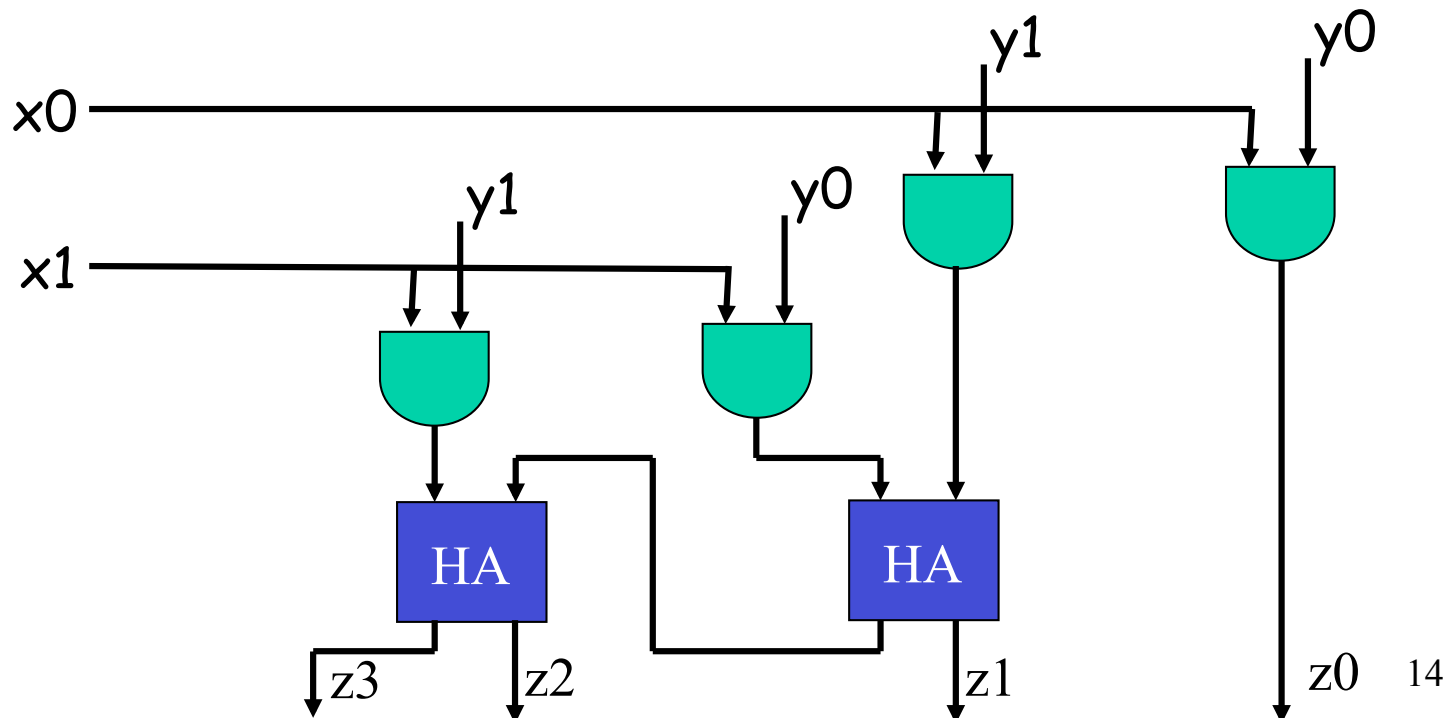
## ■ Two-bit multiplier


$$\begin{array}{r}
 \phantom{+} \phantom{x_1} \phantom{x_0} Y_1 \phantom{Y_0} \phantom{Y} \\
 \times \phantom{+} \phantom{x_1} \phantom{x_0} x_1 \phantom{x_0} \phantom{Y} \\
 \hline
 \phantom{+} \phantom{x_1} \phantom{x_0} x_0 Y_1 \phantom{x_0} Y_0 \\
 + \phantom{x_1} \phantom{x_0} \phantom{x_0} x_1 Y_1 \phantom{x_0} Y_0 \\
 \hline
 z_3 \phantom{z_2} \phantom{z_1} \phantom{z_0} \phantom{z}
 \end{array}$$



# (3x4)-bit Multiplier: Method

				$Y_3$	$Y_2$	$Y_1$	$Y_0$	$Y$
		$\times$			$x_2$	$x_1$	$x_0$	$X$
				$x_0 Y_3$	$x_0 Y_2$	$x_0 Y_1$	$x_0 Y_0$	
			$x_1 Y_3$	$x_1 Y_2$	$x_1 Y_1$	$x_1 Y_0$		
$+$		$x_2 Y_3$	$x_2 Y_2$	$x_2 Y_1$	$x_2 Y_0$			
	$Z_6$	$Z_5$	$Z_4$	$Z_3$	$Z_2$	$Z_1$	$Z_0$	

# 4-bit Multiplier: Circuit

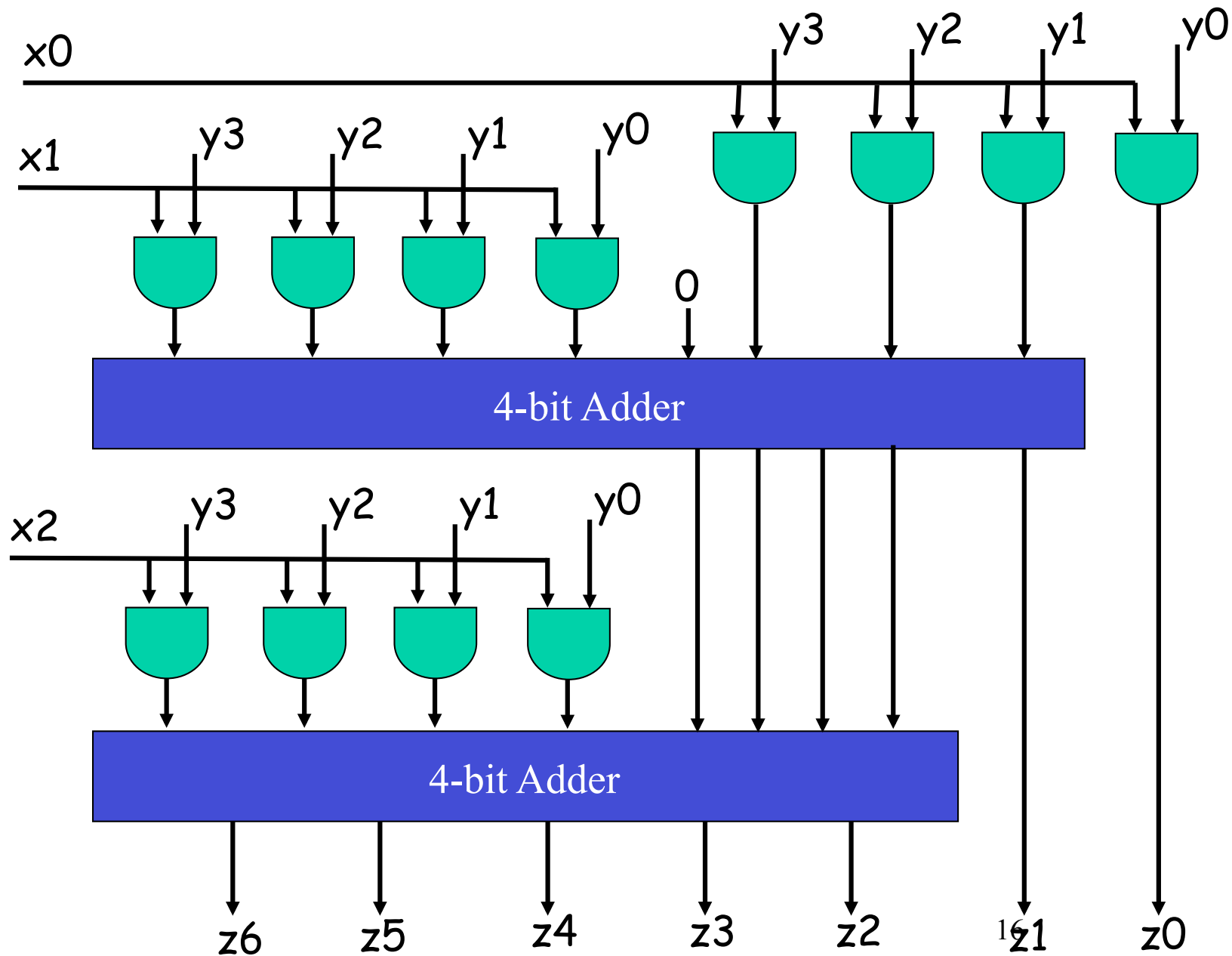



# **$m \times n$ -bit Multipliers**

- **Generalization:**
- **multiplier:  $m$ -bit integer**
- **multiplicand:  $n$ -bit integers**
- **$m \times n$  AND gates**
- **$(m-1)$  adders**
  - **each adder is  $n$ -bit**

# Magnitude Comparator

- **Comparison of two integers: A and B.**
  - $A > B \rightarrow (1, 0, 0) = (x, y, z)$
  - $A = B \rightarrow (0, 1, 0) = (x, y, z)$
  - $A < B \rightarrow (0, 0, 1) = (x, y, z)$
- **Example: 4-bit magnitude comparator**
  - $A = (a_3, a_2, a_1, a_0)$  and  $B = (b_3, b_2, b_1, b_0)$
- 1. **(A = B) case**
  - they are equal if and only if  $a_i = b_i \quad 0 \leq i \leq 3$
  - $t_i = (a_i \oplus b_i)' \quad 0 \leq i \leq 3$
  - $y = (A=B) = t_3 t_2 t_1 t_0$

# 4-bit Magnitude Comparator

## 2. (A > B) and (A < B) cases

- We compare the most significant bits of A and B first.
  - if ( $a_3 = 1$  and  $b_3 = 0$ )  $\rightarrow A > B$
  - else if ( $a_3 = 0$  and  $b_3 = 1$ )  $\rightarrow A < B$
  - else (i.e.  $a_3 = b_3$ ) compare  $a_2$  and  $b_2$ .

$$x = (A > B) = a_3 b_3' + t_3 a_2 b_2' + t_3 t_2 a_1 b_1' + t_3 t_2 t_1 a_0 b_0'$$

$$z = (A < B) = a_3' b_3 + t_3 a_2' b_2 + t_3 t_2 a_1' b_1 + t_3 t_2 t_1 a_0' b_0$$

$$y = (A = B) = t_3 t_2 t_1 t_0$$

# 4-bit Magnitude Comparator: Circuit


 


Fig. 4-17 4-Bit Magnitude Comparator
 
# Decoders

- A binary code of  $n$  bits
  - capable of representing  $2^n$  distinct elements of coded information
  - A decoder is a combinational circuit that converts binary information from  $n$  binary inputs to a maximum of  $2^n$  unique output lines



$x$	$y$	$d_0$	$d_1$	$d_2$	$d_3$
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

- $d_0 =$
- $d_1 =$
- $d_2 =$
- $d_3 =$

## 2-to-4 Decoder

- Some decoders are constructed with NAND gates.
  - Thus, active output will be logic-0
  - They also include an “enable” input to control the circuit operation

$e$	$x$	$y$	$d_0$	$d_1$	$d_2$	$d_3$
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

- $d_0 = e + x + y =$

- $d_1 = e + x + y' =$

- $d_2 = e + x' + y =$

- $d_3 = e + x' + y' =$


## 2-to-4-Line Decoder with Enable

$$d_0 = e + x + y =$$

$$d_1 = e + x + y' =$$


$$d_2 = e + x' + y =$$

$$d_3 = e + x' + y' =$$

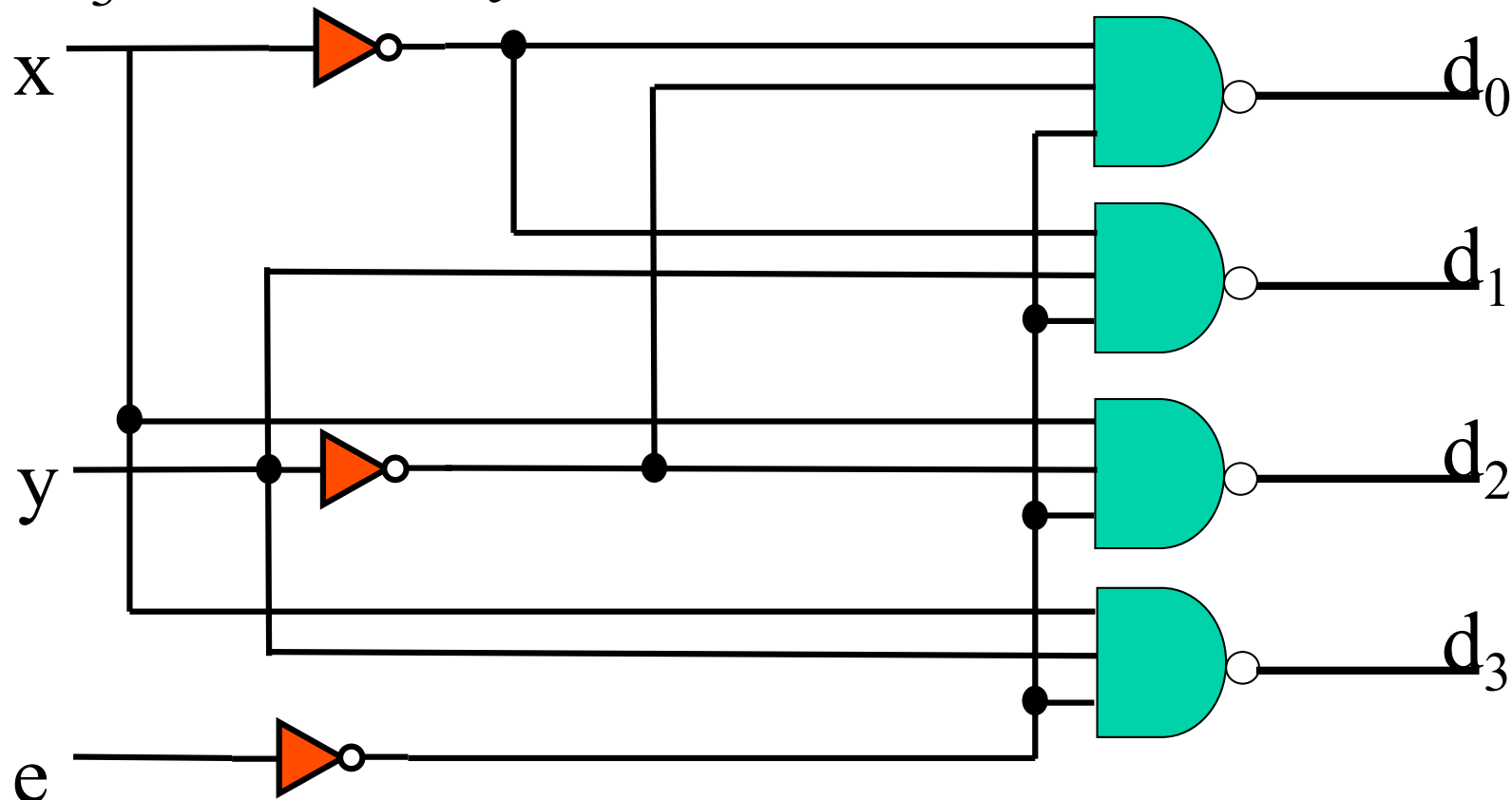
 
# Decoder/Demultiplexer


- A demultiplexer is a combinational circuit
  - it receives information from a single line and directs it one of  $2^n$  output lines
  - It has  $n$  selection lines as to which output will get the input




 
# Decoder as a Building Block

- A decoder provides the  $2^n$  minterms of  $n$  input variable




- We can use a decoder and OR gates to realize any Boolean function expressed as sum of minterms
  - Any circuit with  $n$  inputs and  $m$  outputs can be realized using an  $n$ -to- $2^n$  decoder and  $m$  OR gates.

# Example: Decoder as a Building Block
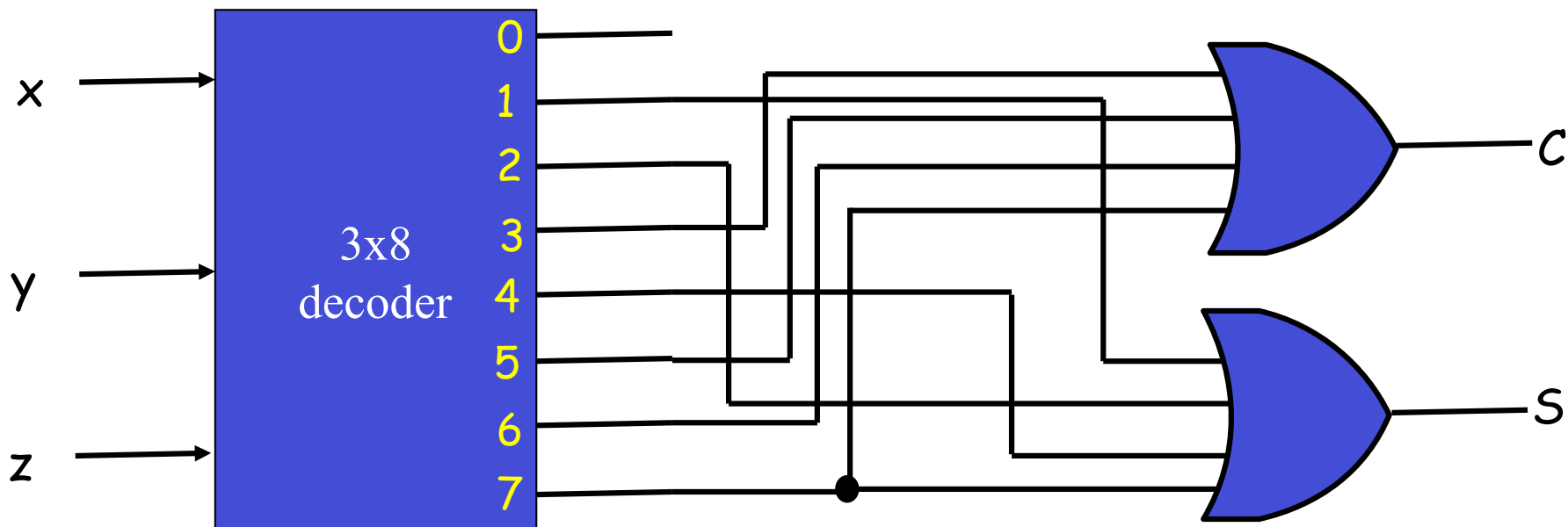
## ■ Full adder

- $C = xy + xz + yz = \Sigma(3, 5, 6, 7)$
- $S = x \oplus y \oplus z = \Sigma(1, 2, 4, 7)$



# Encoders

- **An encoder is a combinational circuit that performs the inverse operation of a decoder**
  - number of inputs:  $2^n$
  - number of outputs:  $n$
  - the output lines generate the binary code corresponding to the input value

- **Example:  $n = 2$**

$d_0$	$d_1$	$d_2$	$d_3$	$x$	$y$
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1

# Priority Encoder

- **Problem with a regular encoder:**
  - only one input can be active at any given time
  - the output is undefined for the case when more than one input is active simultaneously.
- **Priority encoder:**
  - there is a priority among the inputs

$d_0$	$d_1$	$d_2$	$d_3$	x	y	V
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

# 4-bit Priority Encoder

- In the truth table
  - X for input variables represents both 0 and 1.
  - Good for condensing the truth table
  - Example:  $X100 \rightarrow (0100, 1100)$ 
    - This means  $d_1$  has priority over  $d_0$
    - $d_3$  has the highest priority
    - $d_2$  has the next
    - $d_0$  has the lowest priority
- $V = ?$

# Maps for 4-bit Priority Encoder

$d_2d_3$ $d_0d_1$		00	01	11	10
		00	01	11	10
00		X	1	1	1
01		0	1	1	1
11		0	1	1	1
10		0	1	1	1

– X =

$d_2d_3$ $d_0d_1$		00	01	11	10
		00	01	11	10
00		X	1	1	0
01		1	1	1	0
11		1	1	1	0
10		0	1	1	0


– y =

# 4-bit Priority Encoder: Circuit

–  $x = d_2 + d_3$

–  $y = d_1 d_2' + d_3$

–  $V = d_0 + d_1 + d_2 + d_3$

 

# Multiplexers

## ■ A combinational circuit

- It selects binary information from one of the many input lines and directs it to a single output line.
- Many inputs –  $m$
- One output line
- selection lines  $n \rightarrow n = ?$

## ■ Example: 2-to-1-line multiplexer

- 2 input lines  $I_0, I_1$
- 1 output line  $Y$
- 1 select line  $S$

$$Y = ?$$


$S$	$Y$
0	$I_0$
1	$I_1$

Function Table




# 2-to-1-Line Multiplexer

$y = ?$

 

## ■ Special Symbol

 

# 4-to-1-Line Multiplexer

- 4 input lines:  $I_0, I_1, I_2, I_3$
- 1 output line:  $Y$
- 2 select lines:  $S_1, S_0$ .


$S_1$	$S_0$	$Y$
0	0	?
0	1	?
1	0	?
1	1	?

$Y = ?$

Interpretation:


- In case  $S_1 = 0$  and  $S_0 = 0$ ,  $Y$  selects  $I_0$
- In case  $S_1 = 0$  and  $S_0 = 1$ ,  $Y$  selects  $I_1$
- In case  $S_1 = 1$  and  $S_0 = 0$ ,  $Y$  selects  $I_2$
- In case  $S_1 = 1$  and  $S_0 = 1$ ,  $Y$  selects  $I_3$

# 4-to-1-Line Multiplexer: Circuit

 
 
# Multiplexer with Enable Input

- To select a certain building block we use enable inputs



E	S	y
1	XX	
0	00	
0	01	
0	10	
0	11	


# Design with Multiplexers 1/2

- **Reminder: design with decoders**

- Half adder

- $C = xy = \Sigma$


- $S = x \oplus y = x'y + xy' = \Sigma$

 

- A closer look will reveal that a multiplexer is nothing but a decoder with OR gates

# Design with Multiplexers 2/2

## ■ 4-to-1-line multiplexer

 


- $S_1 \rightarrow x$
- $S_0 \rightarrow y$
- $S_1'S_0' = x'y'$ ,
- $S_1'S_0 = x'y$ ,
- $S_1S_0' = xy'$ ,
- $S_1S_0 = xy$

- $Y = S_1'S_0' I_0 + S_1'S_0 I_1 + S_1S_0' I_2 + S_1S_0 I_3.$
- $Y = x'y' I_0 + x'y I_1 + xy' I_2 + xyI_3$
- $Y =$


# Example: Design with Multiplexers

- Example:  $S = \Sigma(1, 2)$

 
 
# Design with Multiplexers Efficiently

- More efficient way to implement an n-variable Boolean function
  1. Use a multiplexer with n-1 selection inputs
  2. First (n-1) variables are connected to the selection inputs
  3. The remaining variable is connected to data inputs
- Example:  $Y = \Sigma(1, 2)$





# Example: Design with Multiplexers

- $F(x, y, z) = \Sigma(1, 2, 6, 7)$ 
  - $F = x'y'z + x'yz' + xyz' + xyz$
  - $Y = S_1'S_0' I_0 + S_1'S_0 I_1 + S_1S_0 I_2 + S_1S_0 I_3$
  - $I_0 = z, I_1 = z', I_2 = 0, I_3 = z \text{ or } z'.$

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$F =$

$F =$

$F =$

$F =$

# Example: Design with Multiplexers


$$F = x'y'z + x'yz' + xyz' + xyz$$

$$F = z \text{ when } x = 0 \text{ and } y = 0$$

$$F = z' \text{ when } x = 0 \text{ and } y = 1$$

$$F = 0 \text{ when } x = 1 \text{ and } y = 0$$
 
$$F = 1 \text{ when } x = 1 \text{ and } y = 1$$






# Design with Multiplexers

- **General procedure for n-variable Boolean function**
  - $F(x_1, x_2, \dots, x_n)$
- 1. The Boolean function is expressed in a truth table
- 2. The first (n-1) variables are applied to the selection inputs of the multiplexer ( $x_1, x_2, \dots, x_{n-1}$ )
- 3. For each combination of these (n-1) variables, evaluate the value of the output as a function of the last variable,  $x_n$ .
  - $0, 1, x_n, x_n'$
- 4. These values are applied to the data inputs in the proper order.

# **Programmable Logic Devices (PLD's)**


- **Programmable Logic Devices are formed by AND and OR arrays. The gate arrays are programmed by using switches in order implement a special Boolean function.**
- **We will discuss three PLDs in this course.**
  - 1. Programmable Read Only Memory (PROM)**
  - 2. Programmable Logic Array (PLA)**
  - 3. Programmable Array Logic (PAL)**

# Programmable Logic Devices

   
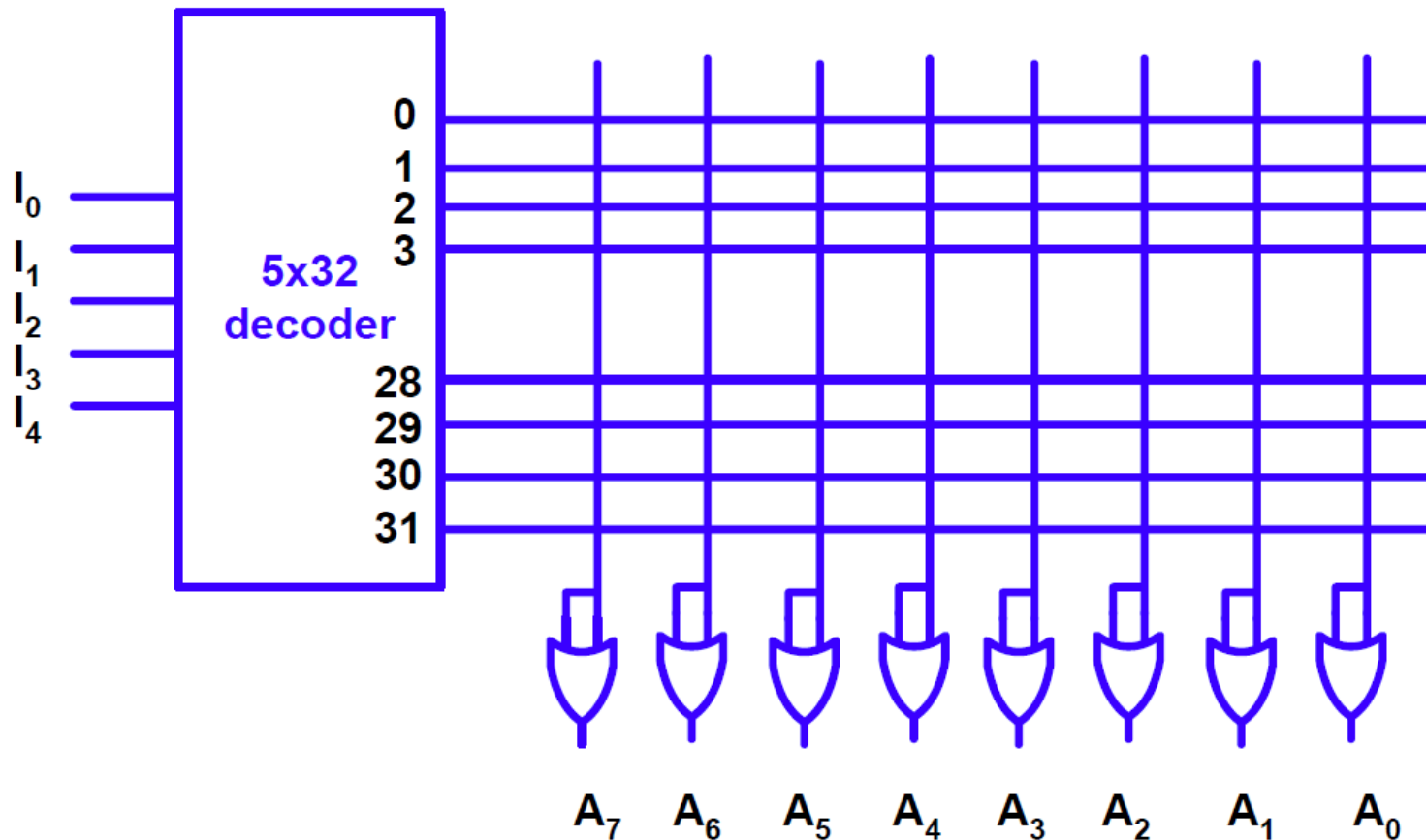
## Read Only Memory (ROM)

- ROM is a device which can store binary information and keep it even when the power is cut.
- ROM contains a decoder and a fixed OR array.



Architecture of a 32x8-bit ROM

# **Combinational Circuit Design by Using ROM**

- **It is direct implementation of a Boolean function.**
  - **There is no need to optimize the Boolean function. It produces all the minterms.**
- **Reprogramme gives the chance to implement different Boolean functions on the same device.**

# Design with ROM


- The truth table of the Boolean function shows the positions of the switches that are closed.

Inputs					Outputs							
I <sub>4</sub>	I <sub>3</sub>	I <sub>2</sub>	I <sub>1</sub>	I <sub>0</sub>	A <sub>7</sub>	A <sub>6</sub>	A <sub>5</sub>	A <sub>4</sub>	A <sub>3</sub>	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>
0	0	0	0	0	1	0	1	1	0	1	1	0
0	0	0	0	1	0	0	0	1	1	1	0	1
0	0	0	1	0	1	1	0	0	0	1	0	1
0	0	0	1	1	1	0	1	1	0	0	1	0
...					...							
1	1	1	0	0	0	0	0	0	1	0	0	1
1	1	1	0	1	1	1	1	0	0	0	1	0
1	1	1	1	0	0	1	0	0	1	0	1	0
1	1	1	1	1	0	0	1	1	0	0	1	1


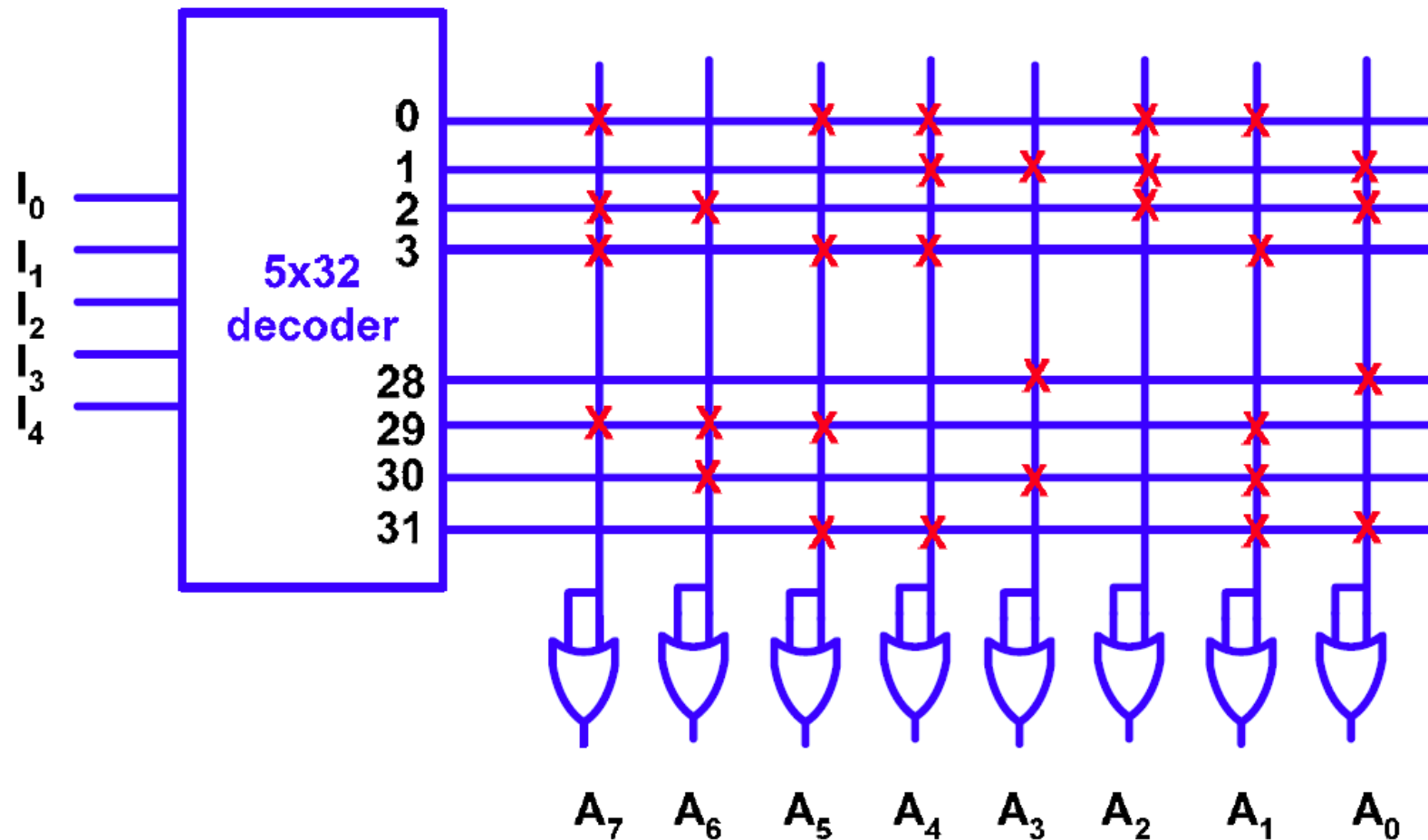
# Design with ROM

- X shows that there is connection. Hence X shows logic-1.
- If there is no X, then there is no connection. Hence absence of X means logic-0.




# Example

- Design a circuit which calculates the square of the 3-bit input with ROM.
- We have to find the input and output bit length.
  - The input bit length is 3. The output bit length is 6.  $72 = 49 = 1100012$ .
- We have to produce the truth table.
  - Doğruluk Tablosu:

$x_2$	$x_1$	$x_0$	$y_5$	$y_4$	$y_3$	$y_2$	$y_1$	$y_0$
0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1
0	1	0	0	0	0	1	0	0
0	1	1	0	0	1	0	0	1
1	0	0	0	1	0	0	0	0
1	0	1	0	1	1	0	0	1
1	1	0	1	0	0	1	0	0
1	1	1	1	1	0	0	0	1

 
# Example

- We decide that  $y_0 = x_0$  and  $y_1 = 0$  from the truth table.
- We need a  $8 \times 4$  ROM.




# Programmable Array Logic (PAL)

Minterms AND Gate Inputs

 

# Design with PAL

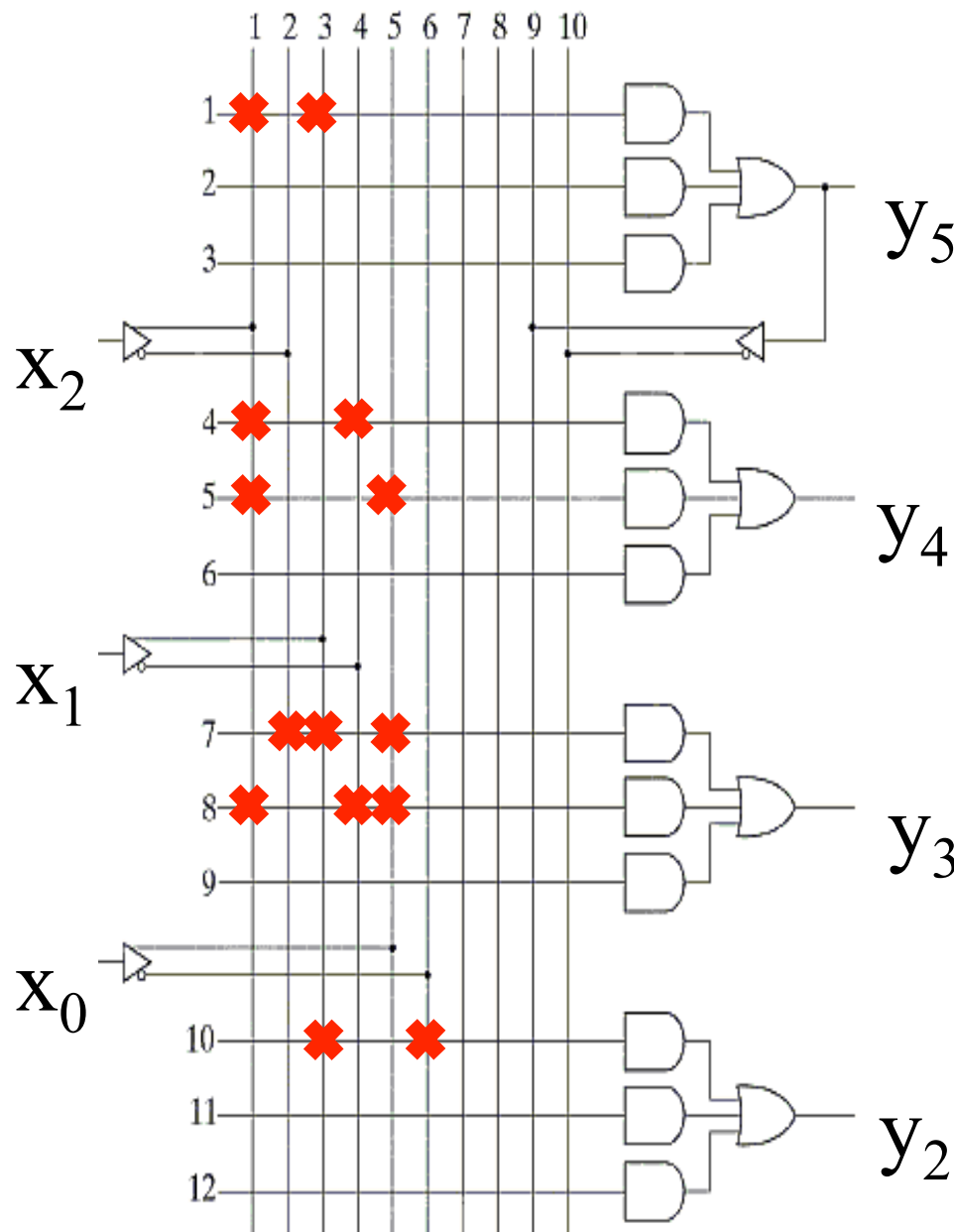

$$y_5 = x_2x_1$$


		$x_2x_1$			
		00	01	11	10
$x_0$	0				1
	1			1	1

$$y_4 = x_2x_1' + x_2x_0$$

$$y_3 = x_2'x_1x_0 + x_2x_1'x_0$$

$$y_2 = x_1x_0'$$

# Programmable Logic Array (PLA)

 

$$F1 = AB' + AC + A'BC'$$

$$F2 = (AC + BC)'$$